

# MODULE 4 : OPERATIONAL AMPLIFIER

- Preview : Basic amplifier concepts & Terminology
- Operational Amplifier (= Op-amp) is a circuit building block of universal importance.
- Op-amps are used for long-time

## Initial Applications

- Analog computation
- Instrumentation

## Later Applications

- Communication
- Instrumentation
- Computing System

→ Early Op-amp construction : 10s of \$

Discrete components : vacuum tubes → Transistors + Resistors

→ Mid - 1960 : First IC Op-amp produced (μA-709)

- Large No of Transistors & Resistors
- single silicon chip.
- Price = High
- characteristics = poor

Dramatically, usage ↑

price ↓

Demand for better quality op-amp ↑

→ Amplifier circuits :

$$\left. \begin{aligned} v_o(t) &\propto v_i(t) \\ v_o(t) &= \underline{A} v_i(t) \end{aligned} \right\} \text{Linear Amplifier}$$

→ Magnitude of amplification (= Gain)  
→ Also called as proportionality constant

→ Shortcomings of amplifier circuits

Input Impedance,  $Z_i$  = Low

Gain,  $A$  = Moderate

Bandwidth, BW = Limited

"Limitations of Basic Amplifier"

Amplifiers Noise present at the input

- Environmental Noise
- Thermal Noise
- other noise

Solution : Operational Amplifiers

Op-amp is popular for its

- Versatility
- characteristics  $\approx$  ideal
- Easy to design circuits
- Performance levels : Theoretically predicted

→ Integrated circuit (IC) version of op-amp components :


- Transistors (Large Numbers = 10)
- Resistors
- Capacitor (usually one)

In this chapter,

- op-amp is treated as a circuit building block
- op-amp is studied with
  - Terminal characteristics
  - Applications



### 5.1 The Ideal op-amp

#### 5.1.1 The Op-amp Terminals

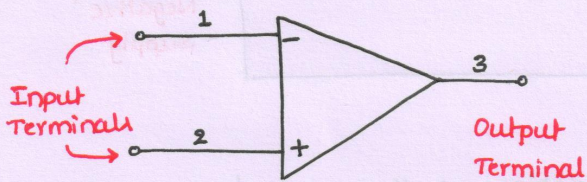


- Op-amp: Three terminals (From signal point of view)
- IC op-amps require two DC power supplies

#### (a) Op-amp circuit symbol

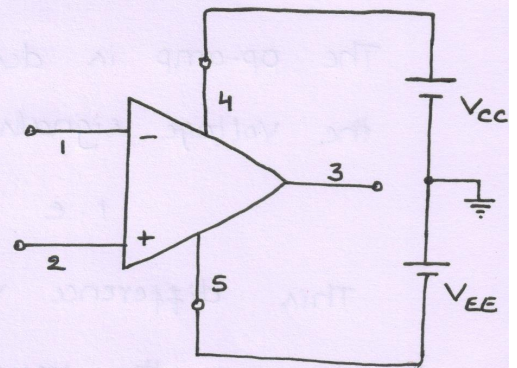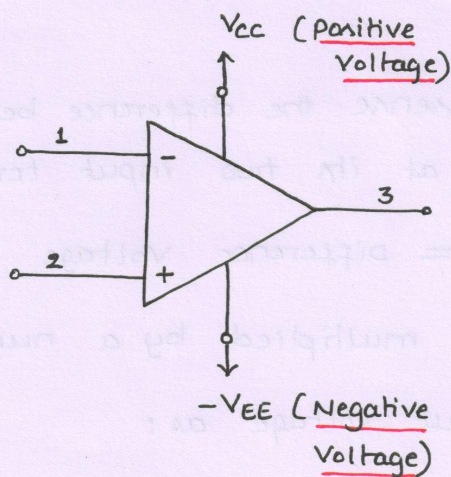
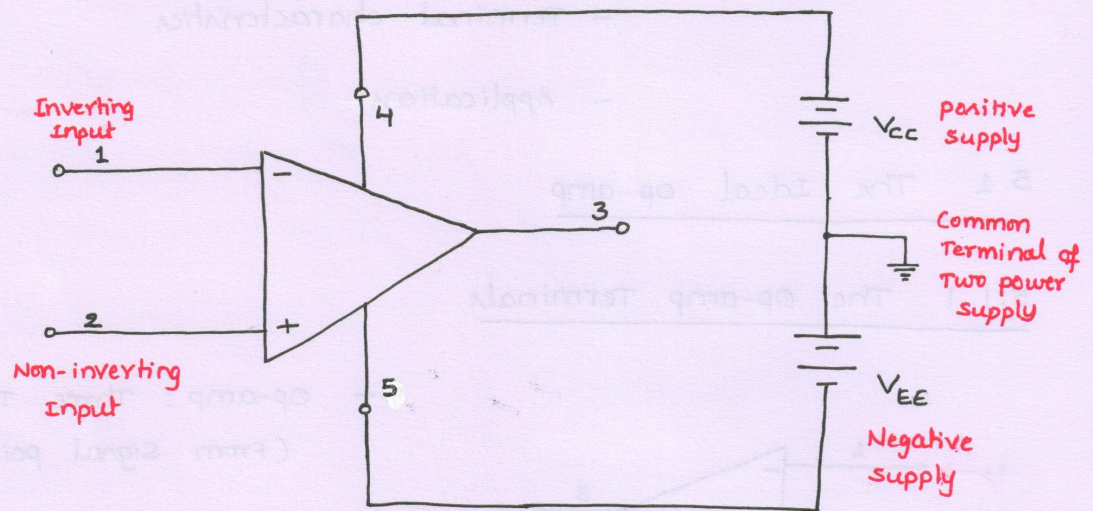
#### (b) Op-amp with DC power supplies

- op-amp have terminals for
  - Frequency compensation
  - offset Nulling



### 5.1.2 Function and characteristics of the Ideal op-amp

#### 3 Op-amp Circuit Function


##### 1. Gain

The op-amp is designed to sense the difference between the voltage signals applied at its two input terminals.

$$\text{i.e. } (V_2 - V_1) = \text{Difference Voltage}$$


This difference voltage is multiplied by a number,  $A$  causing the resultant output voltage as:

$$V_o = A (V_2 - V_1)$$

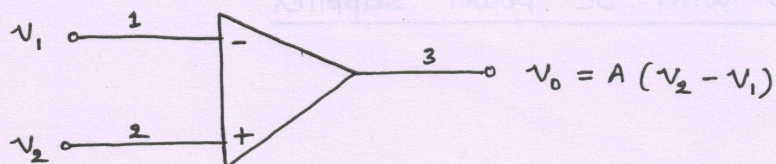

**Note:** All terminal voltages are measured w.r. to ground.

## 2. Input current and Input Impedance

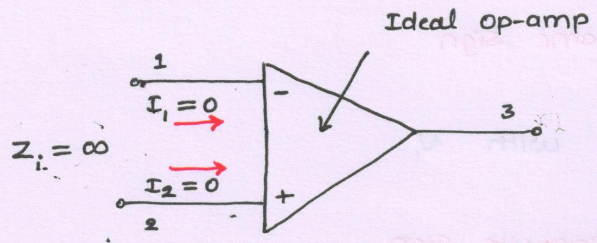

- op-amp is not supposed to draw any input current
- Signal current into terminal-1, is zero  $I_1 = 0$
- Signal current into terminal-2, is zero  $I_2 = 0$

$\Rightarrow Z_i = \infty$

## 3. Output Impedance


Output terminal = output terminal of an ideal voltage source.

i.e  $V_o = A (V_2 - V_1)$

$\Rightarrow$  Output Impedance of an ideal op-amp = zero

$Z_o = 0$

## Equivalent circuit Model

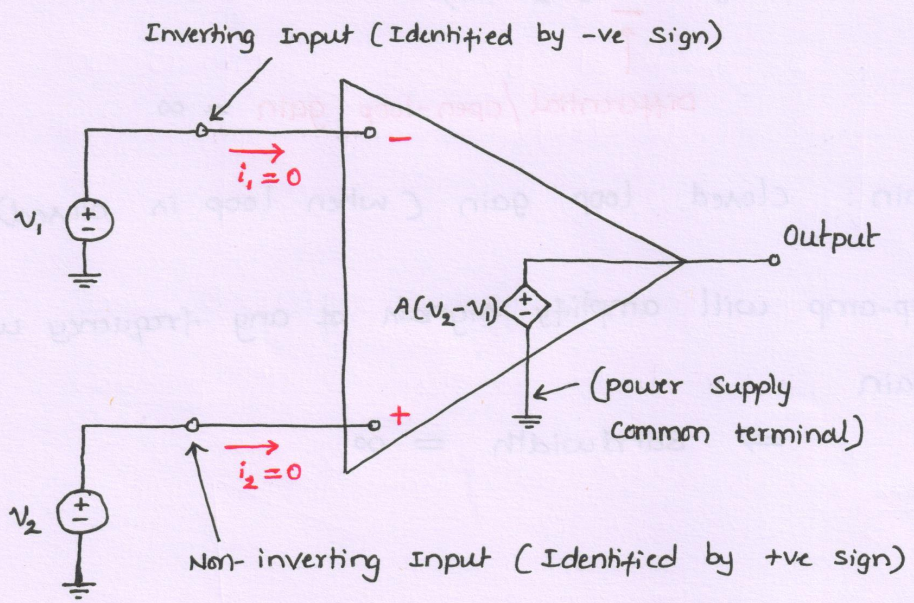

(c) Equivalent circuit of the Ideal - Op-amp

→ Output is in phase with  $v_2$

$$\left. \begin{array}{l} v_o = +ve \\ v_2 = +ve \end{array} \right\} \text{Same sign}$$

→ Output is in out-of-phase with  $v_1$

$$\left. \begin{array}{l} v_o = +ve \\ v_1 = -ve \end{array} \right\} \text{Opposite sign}$$

→ Op-amp responds only to the difference signal

$$\text{i.e. } v_2 - v_1$$

ignores any common signal to both inputs

Example: if  $v_1 = v_2 = 1V$ , then

$$v_o = 0 \text{ (Ideally)}$$

The property is referred as Common Mode Rejection

$$\text{Common mode gain} = 0$$

$$\text{Common mode rejection} = \infty$$

} Ideal op-amp

→ Op-amp is a differential input, single ended output amplifier

$$\text{since, } v_o = A (v_2 - v_1)$$

↑  
Differential/open-loop gain =  $\infty$


→ Another gain: closed loop gain (when loop is closed)

→ Ideal op-amp will amplify signals of any frequency with equal gain

$$\Rightarrow \text{Bandwidth} = \infty$$

Summarizing characteristics of an Ideal Op-amp

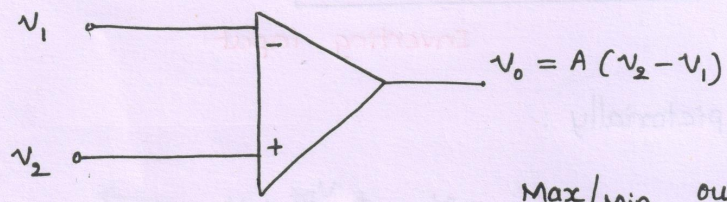
- ①  $z_i = \infty, i_1 = 0, i_2 = 0$
- ②  $z_o = 0$
- ③  $A_{CM} = 0 \Rightarrow$  Common Mode Rejection  $= \infty$
- ④  $A_{OL} = \infty$
- ⑤  $BW = \infty$



Max/min output = 10V =  $v_0$   
 $A = 10^5$

$$(v_2 - v_1) = \frac{v_0}{A} = \frac{10}{10^5} = 0.1 \text{ mV}$$

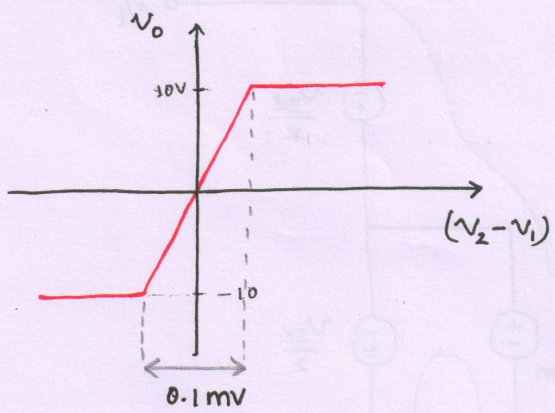$(v_2 - v_1) < 0.1 \text{ mV}$  for linear operation



5.1.3 Differential and Common Mode signals

→ Differential input signal :  $v_{Id} = v_2 - v_1$  — (a)

→ Common mode input signal :  $v_{Icm} = \frac{1}{2}(v_1 + v_2)$

$$2v_{Icm} = v_2 + v_1 \text{ — (b)}$$

Adding (a) and (b)

$$\begin{aligned} v_2 - v_1 &= v_{Id} \\ v_2 + v_1 &= 2v_{Icm} \\ \hline 2v_2 &= v_{Id} + 2v_{Icm} \end{aligned}$$

$$v_2 = v_{icm} + \frac{v_{id}}{2} \quad \text{--- (c)}$$

Non-inverting input

subtracting (a) and (b)

$$v_2 + v_1 = 2v_{icm}$$

$$v_2 - v_1 = v_{id}$$

$$2v_1 = 2v_{icm} - v_{id}$$

$$v_1 = v_{icm} - \frac{v_{id}}{2} \quad \text{--- (d)}$$

Inverting input

Representing pictorially :

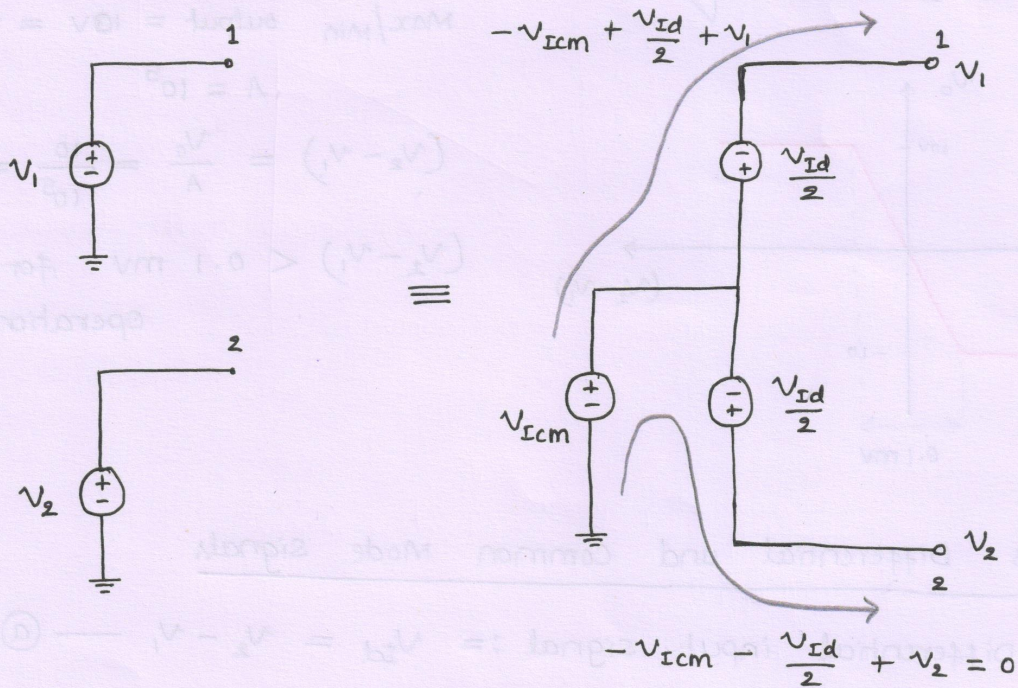


Fig. (d) Representing  $v_1$  &  $v_2$  in terms of

$v_{icm}$  and  $v_{id}$




## 5.2 The Inverting Configuration

(5)

The two basic closed loop op-amp configurations are:

1. Inverting configuration
  2. Non-inverting configuration
- } Employ op-amp & Resistors
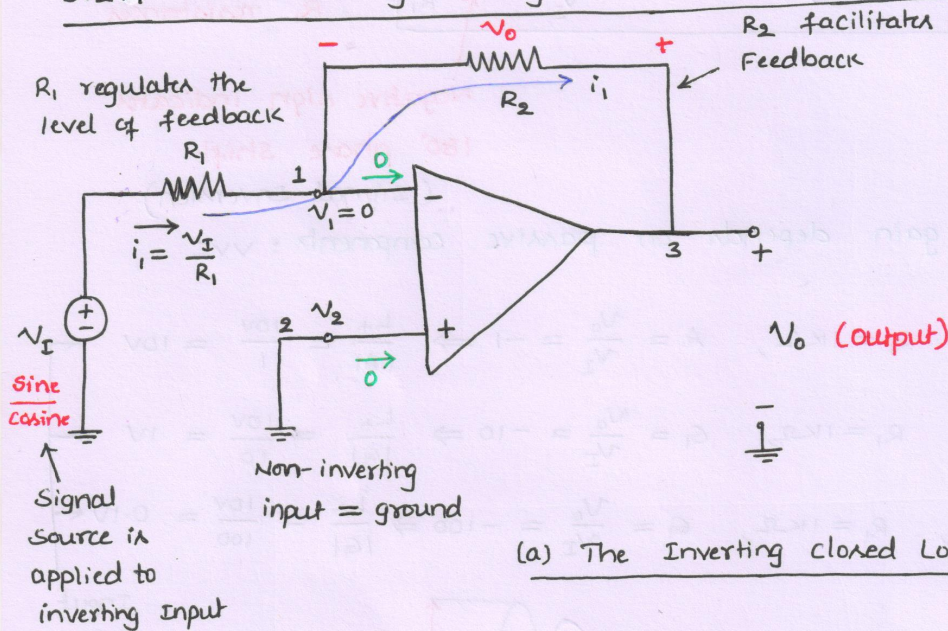
### 5.2.1 The Inverting Configuration: The closed loop gain



(a) The Inverting closed Loop Configuration

$$V_o = A (V_2 - V_1) \longrightarrow \text{For Ideal op-amp}$$

↑  
Very large, Ideally =  $\infty$

$$\frac{V_o}{A} = V_2 - V_1 \cong 0 \Rightarrow V_1 = V_2$$

A =  $\infty$

Voltage at inverting input =  $V_1 = V_2 = 0$

↑                      ↑  
Virtual ground      ground

As  $A \rightarrow \infty$ ,  $V_1 \cong V_2$

(Do not physically short, terminals 1 and 2)

$V_1 = V_2 = 0 \Rightarrow$  virtual short circuit between the two input terminals

virtual short circuit : The voltage that exist at  $v_2$  appears at  $v_1$

$$v_o = -i_1 R_2 = -\frac{v_I}{R_1} \times R_2$$

The closed loop gain =  $G_1 = \frac{v_o}{v_I} = -\frac{R_2}{R_1} \Rightarrow$  Ratio between  $R_2$  &  $R_1$  resistances


Negative sign indicates 180° phase shift (Signal Inversion)

closed loop gain depends on passive components :  $v_I$


if  $R_2 = 1k\Omega$ ,  $R_1 = 1k\Omega$ ,  $G_1 = \frac{v_o}{v_I} = -1 \Rightarrow \frac{L+}{|G_1|} = \frac{10V}{1} = 10V$

if  $R_2 = 10k\Omega$ ,  $R_1 = 1k\Omega$ ,  $G_1 = \frac{v_o}{v_I} = -10 \Rightarrow \frac{L+}{|G_1|} = \frac{10V}{10} = 1V$

if  $R_2 = 100k\Omega$ ,  $R_1 = 1k\Omega$ ,  $G_1 = \frac{v_o}{v_I} = -100 \Rightarrow \frac{L+}{|G_1|} = \frac{10V}{100} = 0.1V$

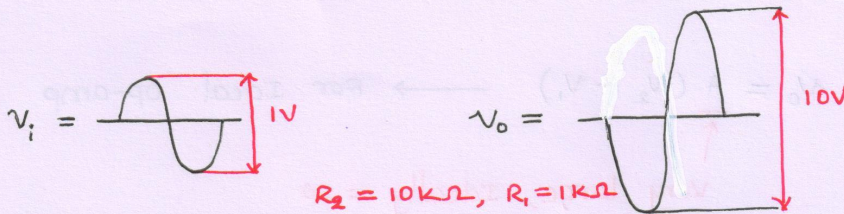

Input voltages required

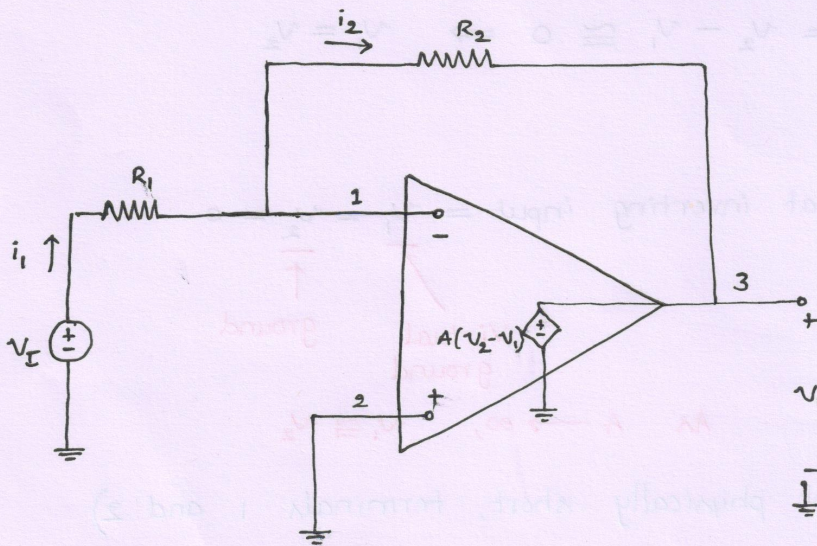


Assumption: Ideal op-amp

$A \rightarrow$  very large, Ideally =  $\infty$   
↑  
Open loop gain

$G_1 = \frac{v_o}{v_I}$   
↑  
closed loop gain

(a) Analysis of Inverting configuration

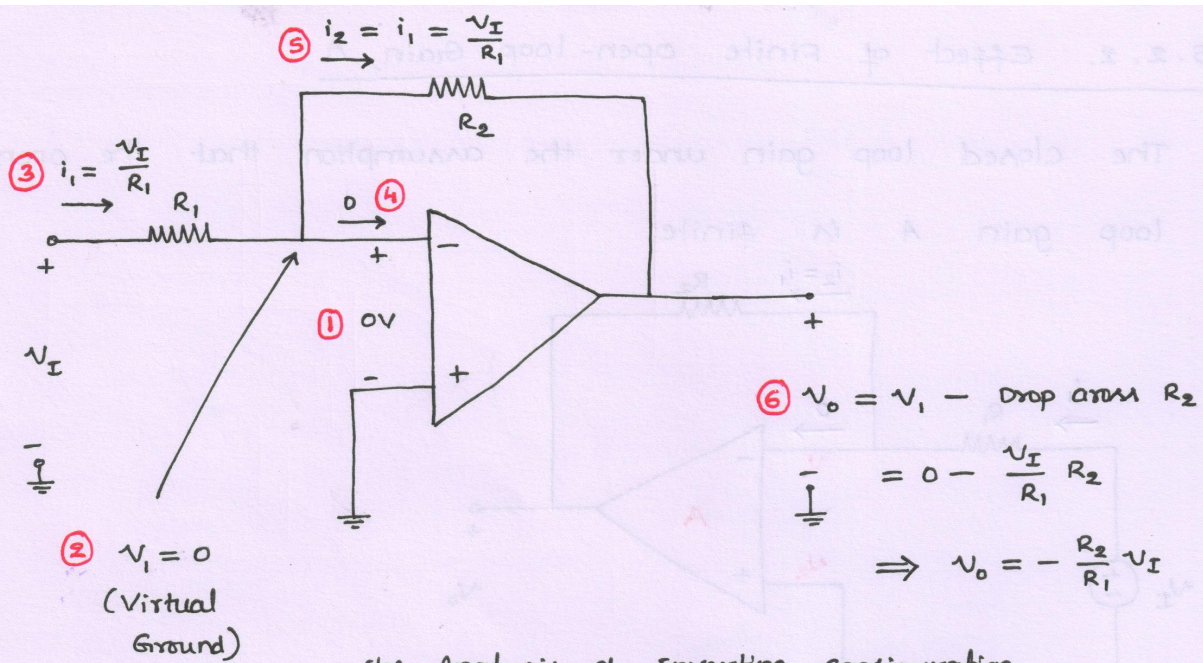

(b) Analysis of Inverting Configuration

Note: circled numbers indicate the order of the analysis steps


### § Observations

1. closed loop gain:  $G_1 = \frac{V_o}{V_I} = -\frac{R_2}{R_1}$

- $G_1$  depends on external passive components,  $R_1$  and  $R_2$
- Negative sign in the  $G_1$  eqn. indicates  $180^\circ$  phase shift w.r.t input.

$\Rightarrow$  Inverting Configuration.

- $G_1$  is independent of the op-amp gain,  $A$
- $G_1 < A$ , due to negative feedback  
 |  
 stable & predictable

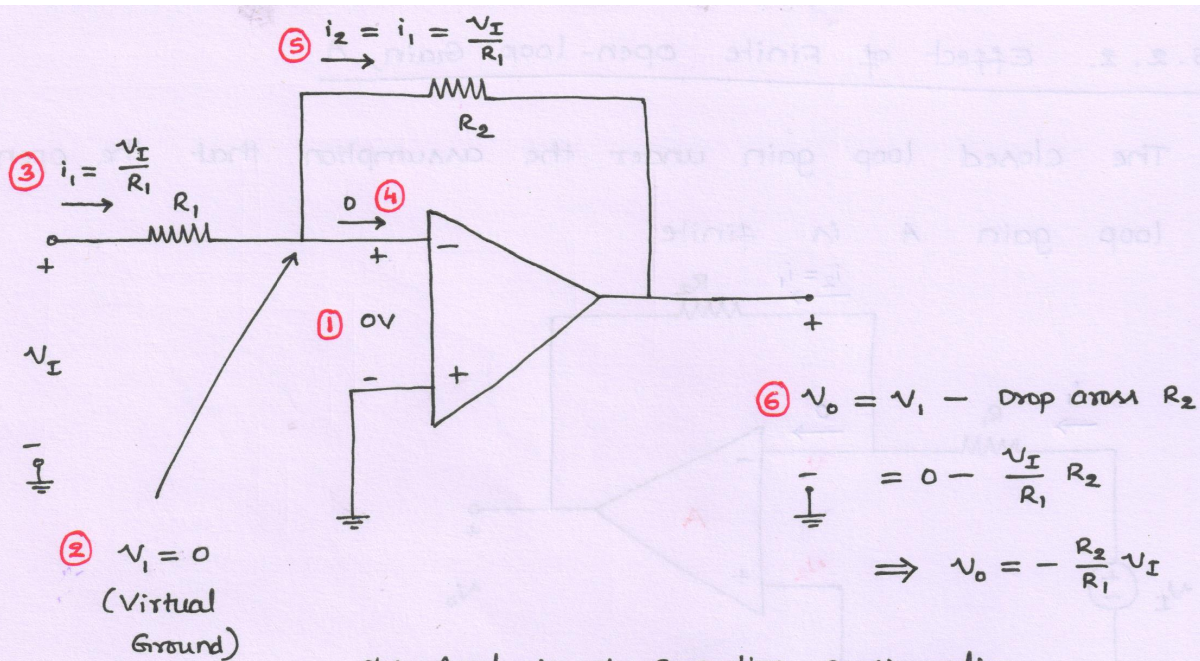

Note: circled numbers indicate the order of the analysis steps

### § Observations

1. closed loop gain:  $G_1 = \frac{V_o}{V_I} = -\frac{R_2}{R_1}$


- $G_1$  depends on external passive components,  $R_1$  and  $R_2$
- Negative sign in the  $G_1$  eqn. indicates  $180^\circ$  phase shift w.r.t input.

$\Rightarrow$  Inverting Configuration.

- $G_1$  is independent of the op-amp gain,  $A$
- $\frac{G_1}{A} < 1$ , due to negative feedback  
|  
stable & predictable
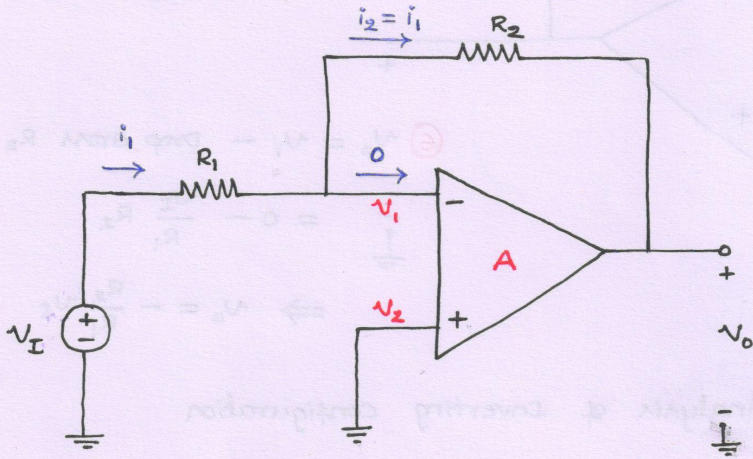
### 5.2.2. Effect of Finite open-loop Gain, $A$

The closed loop gain under the assumption that the open loop gain  $A$  is finite.



(a) Analysis of the inverting configuration with  $A = \text{finite}$


Recall,  $G = -\frac{R_2}{R_1}$  for  $A = \infty$

$$V_o = A (v_2 - v_1)$$

$v_2 = 0\text{V (ground)}$

$$V_o = A (0 - v_1)$$
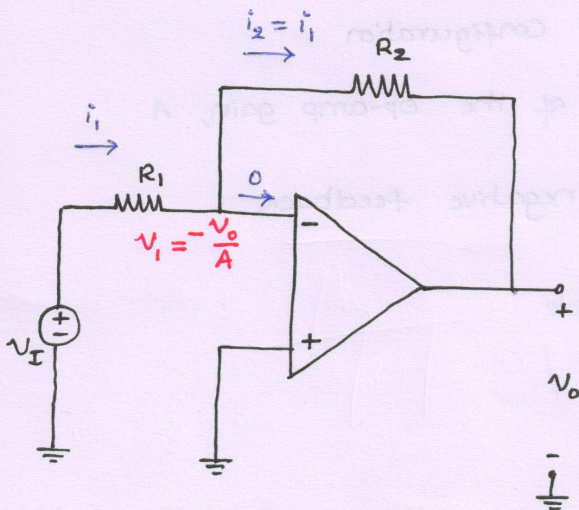
$$\Rightarrow v_1 = -\frac{V_o}{A} = \text{voltage at inverting input}$$



The current  $i_1$  through  $R_1$  is given by

$$i_1 = \frac{V_I - v_1}{R_1} = \frac{V_I - (-\frac{V_o}{A})}{R_1}$$

$$\text{Therefore, } i_1 = \frac{V_I + \frac{V_o}{A}}{R_1}$$

since  $R_i = \infty$ , current through

$$R_2, i_2 = i_1$$

The output voltage,  $V_o$  is given by

$$V_o = V_i - \text{Drop across } R_2$$

$$V_o = V_i - i_2 R_2$$

$$V_o = V_i - i_1 R_2$$

$$-\frac{V_o}{A} = \left( V_i + \frac{V_o}{A} \right) \frac{R_2}{R_1}$$

Therefore, 
$$V_o = -\frac{V_o}{A} - \frac{V_i + \frac{V_o}{A}}{R_1} R_2$$

$$V_o = -\frac{V_o}{A} - V_i \frac{R_2}{R_1} - \frac{V_o}{A} \frac{R_2}{R_1}$$

$$V_o + \frac{V_o}{A} + \frac{V_o}{A} \frac{R_2}{R_1} = -V_i \frac{R_2}{R_1}$$

$$V_o \left[ 1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right) \right] = -V_i \frac{R_2}{R_1}$$

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + \frac{(1 + R_2/R_1)}{A}}$$

Therefore, closed loop gain

$$G_1 = \frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}}{1 + \frac{(1 + \frac{R_2}{R_1})}{A}}$$

Non-ideal gain

①

Observations :

1. If  $A \rightarrow \infty$ , then  $G_1 = -\frac{R_2}{R_1}$  (Ideal value)

Also, as  $A \rightarrow \infty$ ,  $V_i = -\frac{V_o}{A} \rightarrow 0$  (virtual ground assumption)

2. To minimize, dependance  $G_1$  on  $A$ , we should make


$$1 + \frac{R_2}{R_1} \ll A$$

in eqn. ①

Alternatively,  $\frac{(1 + \frac{R_2}{R_1})}{A} \ll 1$ , Therefore,  $G \approx -\frac{R_2}{R_1}$

Typically,  $A = 10^5$

### 5.2.3 Input and Output Resistances

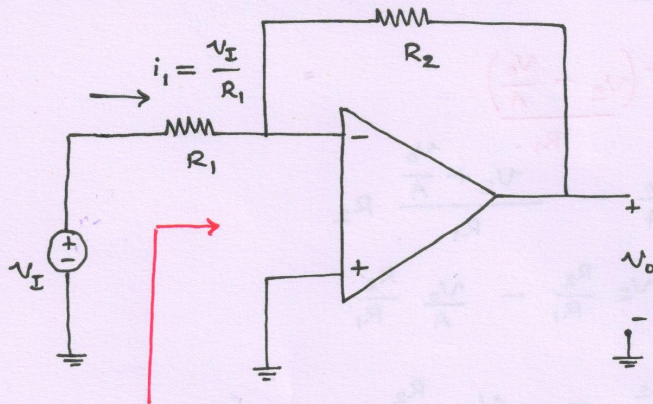


$$R_i \equiv \frac{V_I}{i_i} = \frac{V_I}{V_I/R_1}$$

$$\Rightarrow R_i = R_1$$

$R_i$  (Input Resistance of closed-loop inverting amplifier)


### Voltage Amplifier Model of Inverting Configuration

\* Input Resistance:

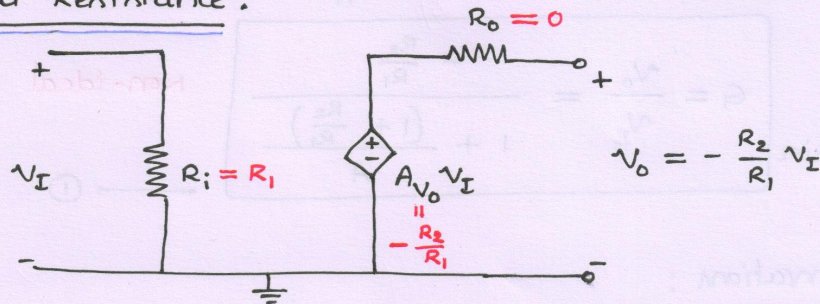

$R_i = \infty$  (perfect Voltage Amplifier)

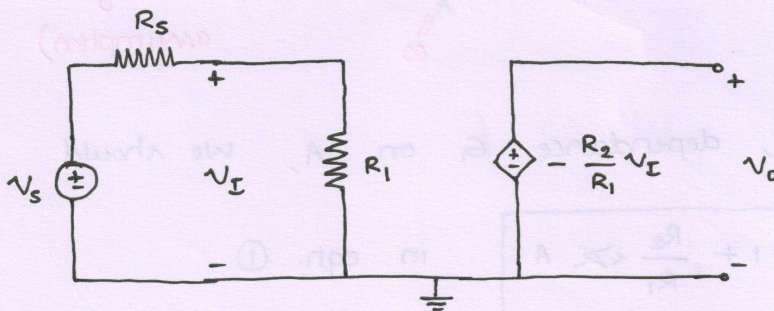(a) Voltage Amplifier Model: Inverting Configuration



$$V_I = V_s \frac{R_1}{R_1 + R_s}$$

$$V_I = V_s \frac{1}{1 + \frac{R_s}{R_1}}$$

$$V_I = V_s \frac{1}{1 + \frac{R_s}{R_i}}$$

⇒ Amplifier input resistance forms a voltage divider with source resistance,  $R_s$  that feeds the amplifier

⇒ For  $V_I = V_s$ ,  $R_i = \text{High}$

To avoid the loss of signal strength, voltage amplifiers are required to have high input resistance

→ For Inverting Configuration,

$$R_i = R_1$$

To avoid loss of signal strength of voltage amplifier

$$R_i = R_1 = \text{Large} \quad \text{Ideally, } R_i = \infty$$

①

However,

$$\text{closed-loop gain, } G = -\frac{R_2}{R_1}$$

To obtain larger closed loop gain,  $G$

$$R_2 = \text{Large, and } R_1 = \text{small} \quad \text{②}$$

Further, to avoid the loss of signal strength


↑  $R_1$ ,  $R_2$  becomes impractically large ( $> \text{M}\Omega$ )

⇒ Inverting configuration suffers from a low input resistance.
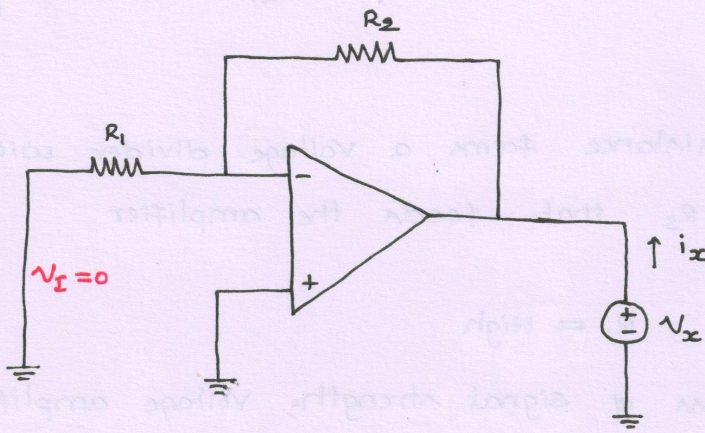
### \* Output Resistance:

The Inverting configuration to determine output resistance is shown in Fig. (b)






$$V_o = - \frac{R_2}{R_1} \frac{V_I}{0} \quad (\text{Input = short circuit})$$

$$V_o = 0$$

$$i_x \rightarrow \infty$$

$$\Rightarrow R_o = 0$$

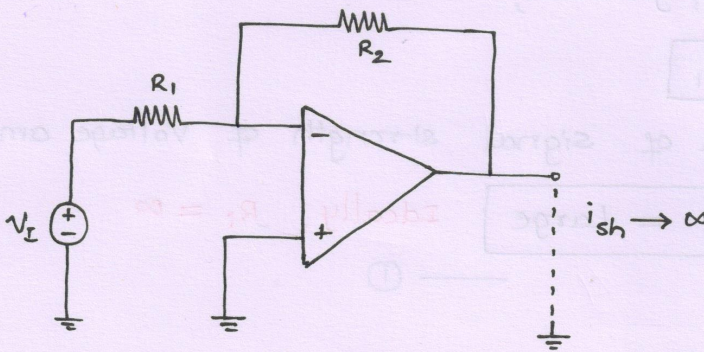(b) Inverting Configuration circuit to Determine  $R_o$



$$i_{sh} \rightarrow \infty$$

$R_2 = \text{large}$ , and  $R_1 = \text{small}$

Output Resistance:

The inverting configuration to determine output resistance is shown in fig. (b)

Example 5.2

Assuming op-amp to be ideal, derive an expression for the closed loop gain,  $\frac{V_o}{V_i}$  of the circuit shown below. Use this circuit to design an inverting amplifier with a gain of 100 and an input resistance of  $1\text{M}\Omega$ . Assume that for practical reasons it is required not to use resistors greater than  $1\text{M}\Omega$ . Compare your design with that based on the inverting configuration.

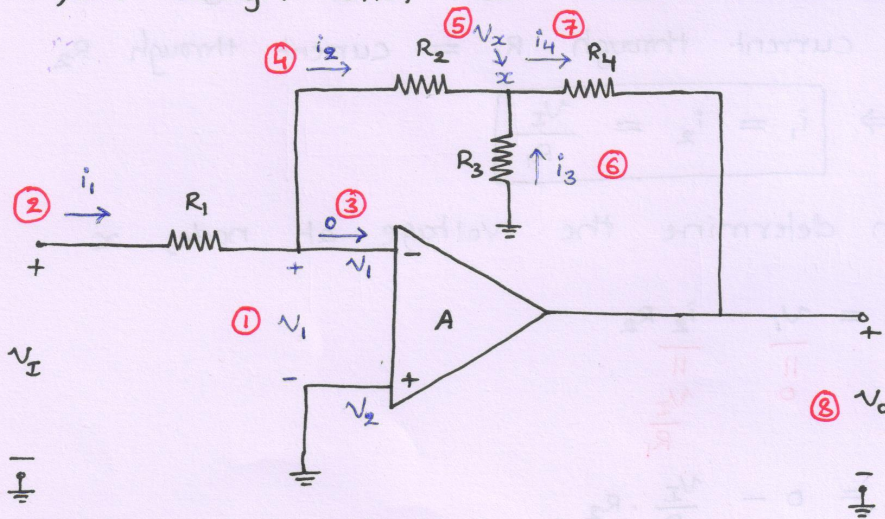


Fig. (a)

Note: circled numbers, indicate the sequence of steps in the analysis

Solution

→ op-amp is assumed to be ideal

⇒  $A = \infty$

We know that  $V_o = A (V_2 - V_1)$

$V_2 = 0$  (ground)

$V_o = A (0 - V_1)$

$V_1 = -\frac{V_o}{A} = 0$

Therefore, voltage at inverting input,  $V_1 = 0$

→ knowing  $v_1$ , we can determine the current  $i_1$  as follows:

$$i_1 = \frac{v_I - v_1}{R_1}$$

$$i_1 = \frac{v_I - 0}{R_1}$$

$$i_1 = \frac{v_I}{R_1}$$

→ For an op-amp,  $R_i = \infty$

⇒ Zero current flows into the inverting input

Therefore, current through  $R_1 =$  current through  $R_2$

$$\Rightarrow i_1 = i_2 = \frac{v_I}{R_1}$$

→ Now, we can determine the voltage at node  $x$

$$v_x = v_1 - i_2 R_2$$

$$v_x = 0 - \frac{v_I}{R_1} \cdot R_2$$

Therefore, 
$$v_x = -\frac{R_2}{R_1} v_I$$

→ This in turn enables us to find  $i_3$

$$i_3 = \frac{0 - v_x}{R_3} = -\frac{R_2}{R_1} \frac{v_I}{R_3}$$

$$i_3 = -\frac{v_x}{R_3} = -\frac{1}{R_3} \left( -\frac{R_2}{R_1} v_I \right)$$

$$i_3 = \frac{R_2}{R_1 R_3} v_I$$

→ Applying KCL at node  $x$  yields  $i_4$ :

$$i_4 = i_2 + i_3$$

$$i_4 = \frac{V_I}{R_1} + \frac{R_2}{R_1 R_3} V_I$$

→ Finally, we can determine  $v_o$  as follows:

$$V_o = \frac{V_I}{R_1} - i_4 \cdot R_4$$
  
$$= -\frac{R_2}{R_1} V_I - \left( \frac{V_I}{R_1} + \frac{R_2}{R_1 R_3} V_I \right) R_4$$

$$V_o = -\frac{R_2}{R_1} V_I - \left( \frac{V_I}{R_1} + \frac{R_2}{R_1 R_3} V_I \right) R_4$$

$$V_o = -V_I \left[ \frac{R_2}{R_1} + \frac{R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right]$$

$$\frac{V_o}{V_I} = - \left[ \frac{R_2}{R_1} + \frac{R_4}{R_1} + \frac{R_2 R_4}{R_1 R_3} \right]$$

$$\frac{V_o}{V_I} = - \frac{R_2}{R_1} \left[ 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$

$$\frac{V_o}{V_I} = - \frac{R_2}{R_1} \left[ 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$

→  $R_1 = \text{Input resistance} = 1\text{M}\Omega$  (required)

if we choose  $R_2 = R_3 = R_4 = 1\text{M}\Omega$ , then  $\frac{V_o}{V_I} \neq -100$

let  $R_2 = 1\text{M}\Omega$ , and  $R_3$  and  $R_4$  are selected

so that  $\frac{V_o}{V_I} = -100$

$$\text{i.e. } \left( \frac{V_o}{V_I} \right) = - \frac{R_2}{R_1} \left[ 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right]$$
  
$$\underset{-100}{=} \left( \frac{V_o}{V_I} \right) = - \frac{\overset{1\text{M}\Omega}{R_2}}{\underset{1\text{M}\Omega}{R_1}} \left[ 1 + \frac{\underset{1\text{M}\Omega}{R_4}}{\underset{1\text{M}\Omega}{R_2}} + \frac{R_4}{R_3} \right]$$

$$-100 = - \frac{1\text{M}\Omega}{1\text{M}\Omega} \left[ 1 + \frac{R_4}{1\text{M}\Omega} + \frac{R_4}{R_3} \right]$$

$$-100 = -1 \left[ 1 + \frac{R_4}{1\text{M}\Omega} + \frac{R_4}{R_3} \right]$$

if we choose,  $R_4 = 1\text{M}\Omega$ , then 2<sup>nd</sup> factor = 1

Therefore, to have a total gain of 100,  $R_3$  required is

$$-100 = -1 \left[ 1 + 1 + \frac{1M\Omega}{R_3} \right]$$

$$98 = \frac{1M\Omega}{R_3}$$

$$\Rightarrow R_3 = \frac{1M\Omega}{98} = 10.2 \text{ k}\Omega$$

$$\boxed{R_3 = 10.2 \text{ k}\Omega}$$

Comparison : Considering basic inverting configuration

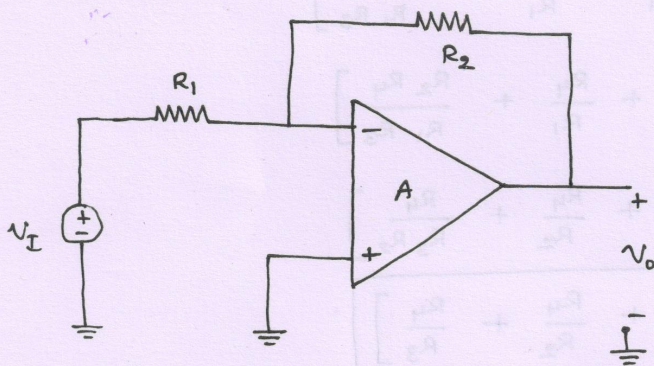


Fig. (b)

w. k. t  $G = - \frac{R_2}{R_1}$

↑

closed loop gain

$$R_1 = 1M\Omega \text{ (required)}$$

Therefore, to have a gain of -100,  $R_2$  required is

calculated as follows

$$-100 = - \frac{R_2}{1M\Omega}$$

$$\Rightarrow \boxed{R_2 = 100 \text{ M}\Omega} \text{ (very large value)}$$

conclusion : The circuit shown in Fig. (a) is able to realize a large voltage gain without using large resistors in the feedback path.

§ Current Amplifier

A circuit shown in Fig. (a) is modified as a current amplifier

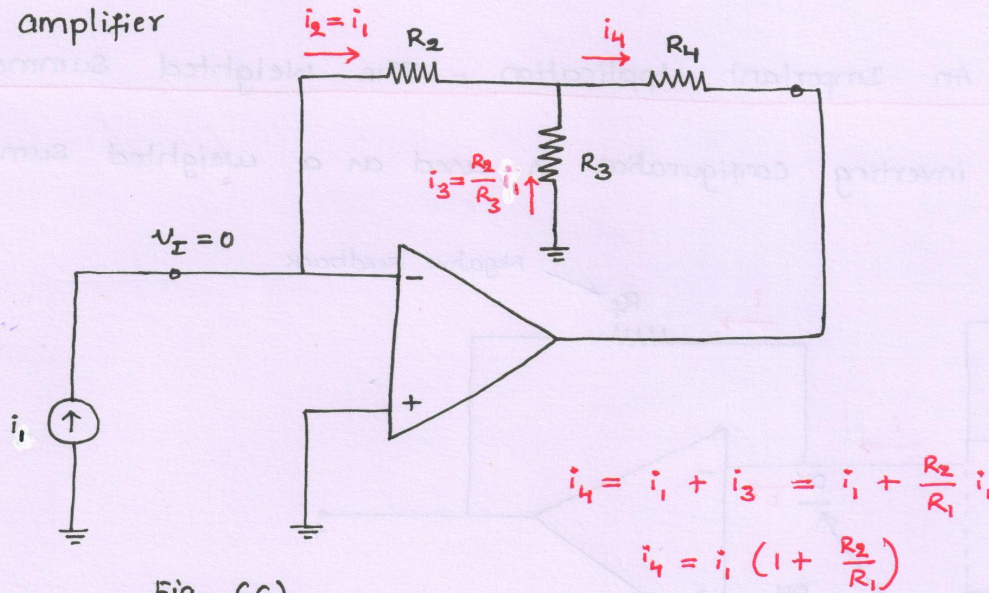


Fig. (c)

→  $R_2$  and  $R_3$  are in effect parallel

→ By making  $R_3$  lower than  $R_2$  by a factor,  $K$

i.e.  $R_3 = \frac{R_2}{K}$ , where  $K > 1$

→  $R_3$  is forced to carry a current  $K$ -times that in  $R_2$

→  $i_2 = i_1$

$i_3 = K i_1$

$i_4 = \underline{(K+1) i_1}$ , since  $i_4 = i_2 + i_3$

↑  
current multiplication

⇒ The current multiplication enables a large voltage drop across  $R_4$


$\Rightarrow V_o = \text{large}$ , without using large value for  $R_4$

Also,  $i_4$  is independent of the value of  $R_4$

Therefore, Fig. (c) can be used as a current amplifier.
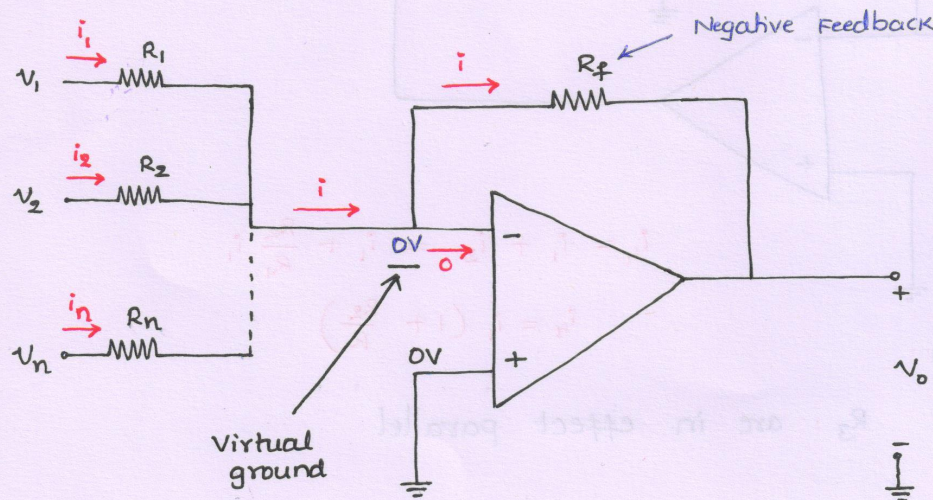
#### 5.2.4 An Important Application - The Weighted Summer

$\rightarrow$  An inverting configuration is used as a weighted summer



(a) A Weighted Summer

$\rightarrow$  A weighted summer circuit is shown in Fig. (a)

$\rightarrow R_f$  : Resistor in negative feedback path

$V_1, V_2, \dots, V_n$  : Input signals applied to inverting input

$R_1, R_2, \dots, R_n$  : Resistors of corresponding input signals

$\rightarrow$  The ideal op-amp will have a virtual ground appearing at its negative input terminal

Therefore, the currents  $i_1, i_2, \dots, i_n$  are given by

$$i_1 = \frac{V_1}{R_1}, \quad i_2 = \frac{V_2}{R_2}, \quad \dots, \quad i_n = \frac{V_n}{R_n}$$

All these currents sum together to produce the current  $i$ ; i.e. (12)

$$i = i_1 + i_2 + \dots + i_n$$

→ This  $i$  is forced to flow through  $R_f$ , since no current flows into the input terminals of an ideal op-amp.

→ The output voltage,  $V_o$  can be determined by ohm's Law,

$$V_o = \underbrace{V_1}_{\substack{\parallel \\ 0V \\ \text{(Virtual Ground)}}} - \underbrace{\text{Drop across } R_f}_{\substack{\parallel \\ i R_f}}$$

$$V_o = 0 - i R_f = -i R_f \quad \text{where } i = (i_1 + i_2 + \dots + i_n)$$

$$V_o = - \left( \underbrace{i_1}_{\substack{\parallel \\ \frac{V_1}{R_1}}} + \underbrace{i_2}_{\substack{\parallel \\ \frac{V_2}{R_2}}} + \dots + \underbrace{i_n}_{\substack{\parallel \\ \frac{V_n}{R_n}}} \right) R_f$$

$$V_o = - \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right) R_f$$

$$V_o = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \dots + \frac{R_f}{R_n} V_n \right) \quad \text{--- (1)}$$

Weights

⇒ The output voltage is weighted sum of the input signals  $V_1, V_2, \dots, V_n$

The circuit is referred to as a "Weighted Summer"

→ The summing coefficients may be independently adjusted by adjusting the corresponding "feed-in" resistor ( $R_1$  to  $R_n$ )

Disadvantage:

→ All summing co-efficients are of the same sign (see eqn. (1))

→ The need may arise for summing signals with opposite signs



9 Weighted Summer : summing signals with opposite sign

The weighted summer for summing signals with opposite signs can be implemented using two op-amps shown in Fig. (a)

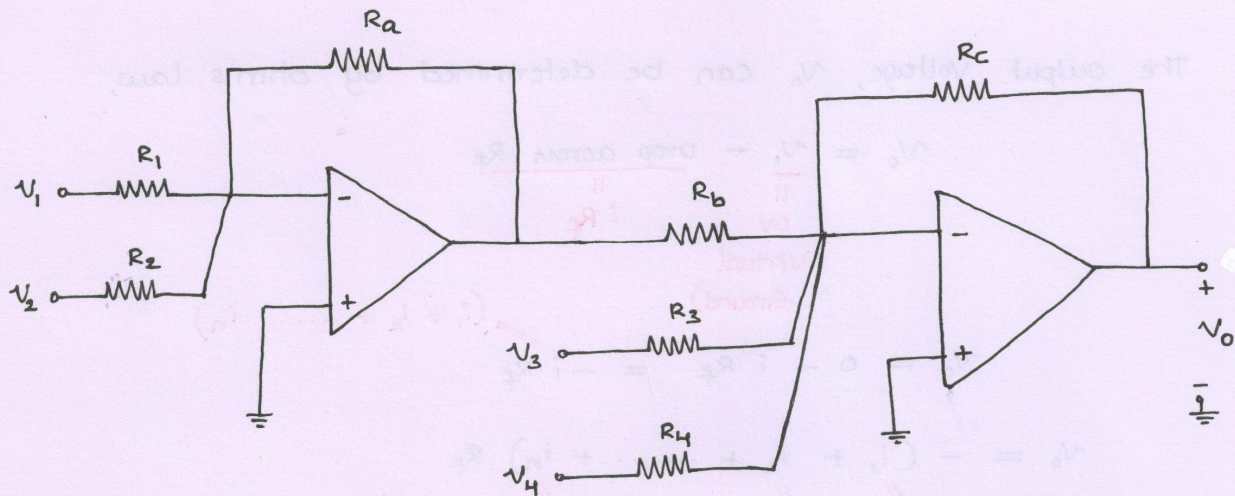



Fig. (a) : Weighted Summer Implementation for summing coefficients of both signs

→ Assume op-amps are ideal

→ Apply superposition principle to obtain the expression for output voltage,  $V_o$

$$V_o = A V_1 + B V_2 + C V_3 + D V_4 \quad : \text{Linear circuit}$$

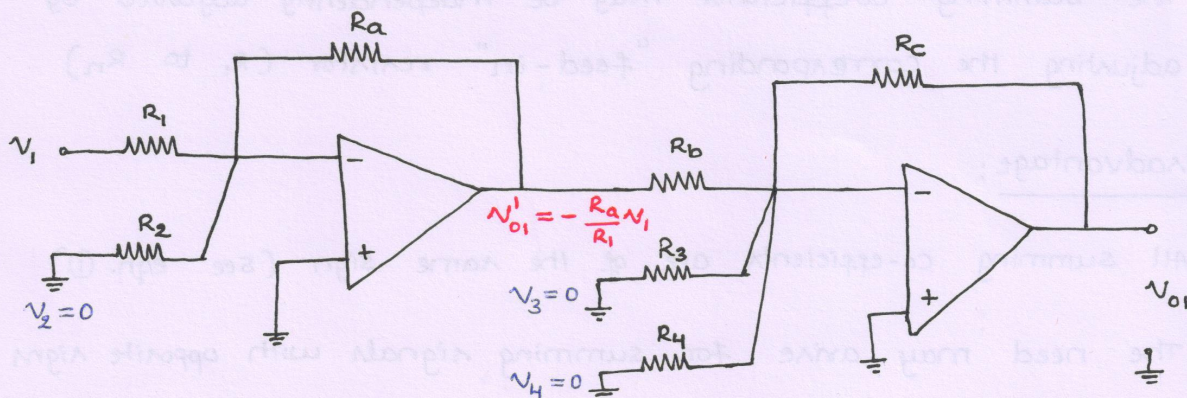→ Considering  $V_1$  alone and assuming  $V_2 = V_3 = V_4 = 0$




Output of 1<sup>st</sup> op-amp :  $V_{o1}' = - \frac{R_a}{R_1} V_1$  (Inverting configuration)

output of 2<sup>nd</sup> op-amp :  $V_{o1} = - \frac{R_c}{R_b} V_{o1}'$   
 $= - \frac{R_c}{R_b} \left( - \frac{R_a}{R_1} V_1 \right)$

$V_{o1} = + \frac{R_a R_c}{R_b R_1} V_1$

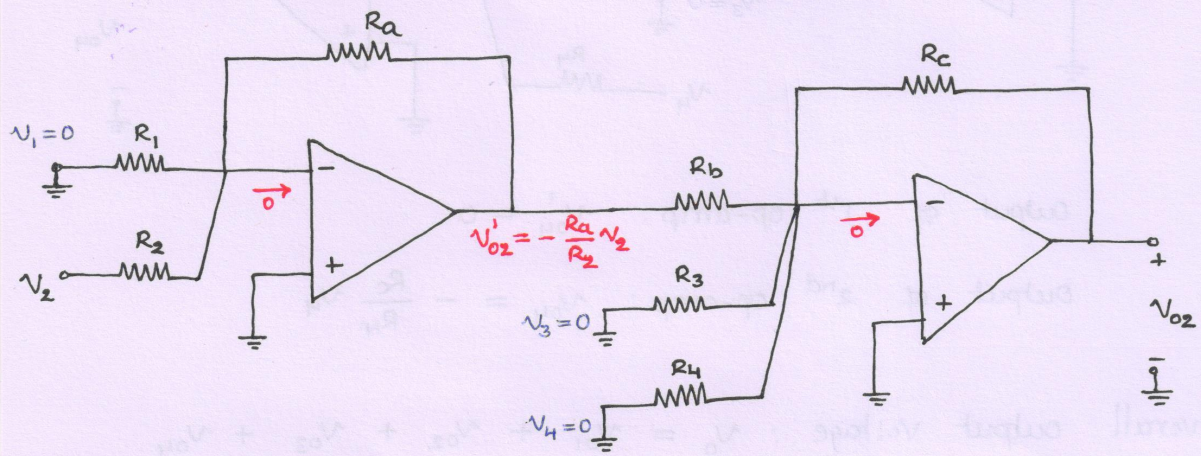→ considering  $V_2$  alone and assuming  $V_1 = V_3 = V_4 = 0$




Output of 1<sup>st</sup> op-amp :  $V_{o2}' = - \frac{R_a}{R_2} V_2$

Output of 2<sup>nd</sup> op-amp :  $V_{o2} = - \frac{R_c}{R_b} V_{o2}'$   
 $= - \frac{R_c}{R_b} \left( - \frac{R_a}{R_2} V_2 \right)$

$V_{o2} = + \frac{R_a R_c}{R_b R_2} V_2$

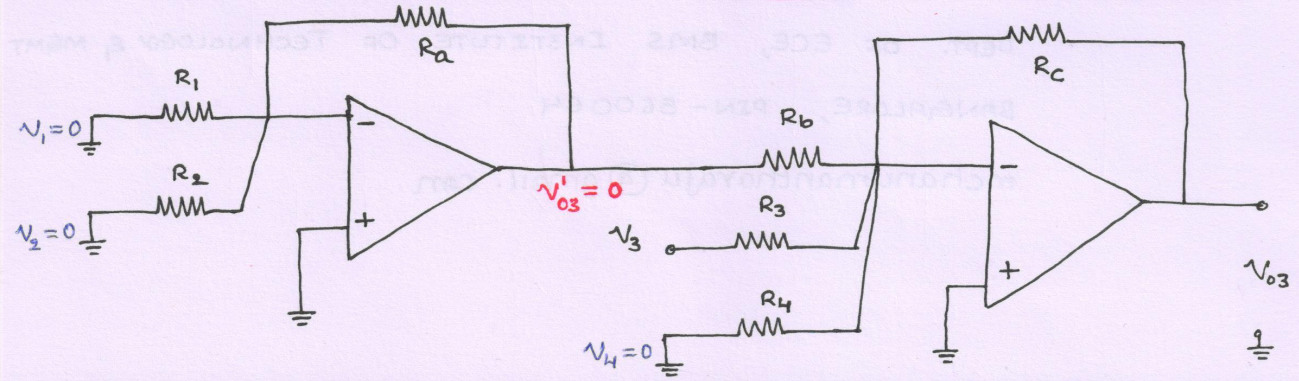
→ considering  $V_3$  alone and assuming  $V_1 = V_2 = V_4 = 0$



output of 1<sup>st</sup> op-amp :  $V_{03}^1 = 0$

output of 2<sup>nd</sup> op-amp :  $V_{03} = -\frac{R_c}{R_3} V_3$

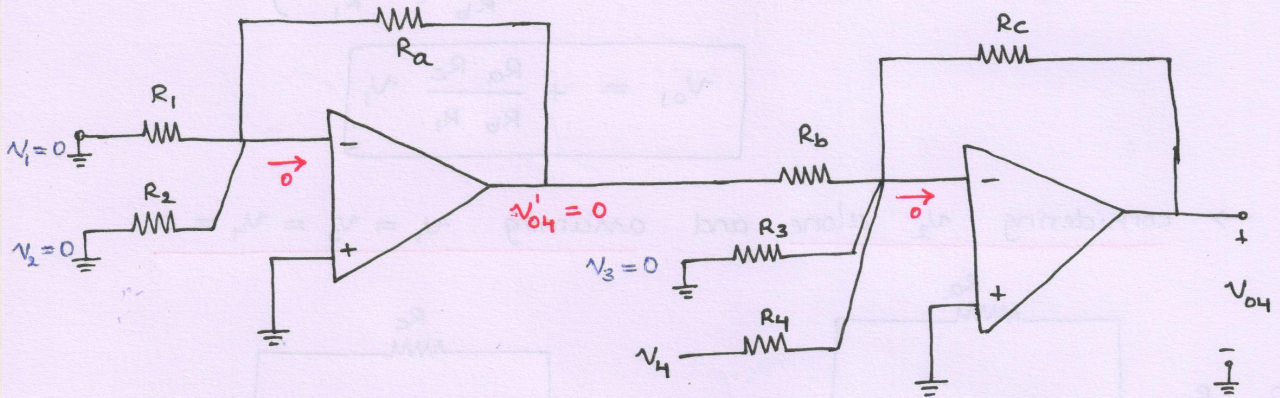→ considering  $V_4$  alone and assuming  $V_1 = V_2 = V_3 = 0$



output of 1<sup>st</sup> op-amp :  $V'_{04} = 0$


output of 2<sup>nd</sup> op-amp :  $V_{04} = -\frac{R_c}{R_4} V_4$

Overall output voltage :  $V_o = V_{01} + V_{02} + V_{03} + V_{04}$

$$V_o = V_1 \left( \frac{R_a}{R_1} \right) \left( \frac{R_c}{R_b} \right) + V_2 \left( \frac{R_a}{R_2} \right) \left( \frac{R_c}{R_b} \right) - V_3 \left( \frac{R_c}{R_3} \right) - V_4 \left( \frac{R_c}{R_4} \right)$$

Exercise D5.7: Design an inverting amplifier to form the weighted sum  $v_o$  of two inputs  $v_1$  and  $v_2$ . It is required that  $v_o = -(v_1 + 5v_2)$ . choose values for  $R_1$ ,  $R_2$ , and  $R_f$  so that for a maximum output voltage of 10V the current in the feedback resistor will not exceed 1mA.

Solution:

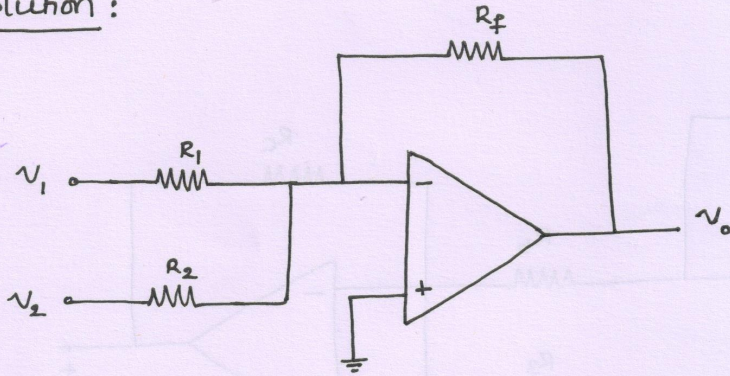

For the circuit shown, applying superposition principle

$$v_o = - \left( \frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 \right)$$

since it is required that  $v_o = -(v_1 + 5v_2)$ ,

we want to have

$$\frac{R_f}{R_1} = 1 \quad \text{and} \quad \frac{R_f}{R_2} = 5$$

It is also desired that for a maximum output voltage of 10V, the current in the feedback resistor does not exceed 1 mA.

Therefore,  $\frac{10V}{R_f} \leq 1 \text{ mA}$

$$\Rightarrow R_f \geq \frac{10V}{1 \text{ mA}}$$

$$\boxed{R_f \geq 10 \text{ k}\Omega}$$

Let us choose  $R_f$  to be  $10k\Omega$ , then  $R_1 = R_f = 10k\Omega$


$$R_2 = \frac{R_f}{5} = \frac{10k\Omega}{5} = 2k\Omega$$

$$R_2 = 2k\Omega$$

Exercise D5.8: Design a weighted summer that provides

$$V_o = 2V_1 + V_2 - 4V_3$$

Solution

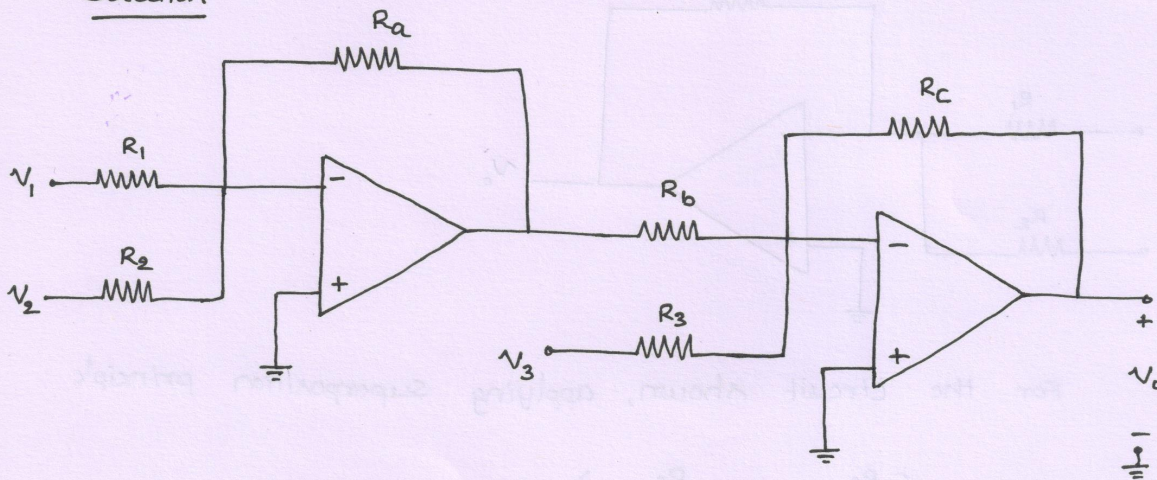

(a) Weighted Summer: Coefficients of both signs

Applying superposition principle, we get

$$V_o = \left(\frac{R_a}{R_1}\right)\left(\frac{R_c}{R_b}\right)V_1 + \left(\frac{R_a}{R_2}\right)\left(\frac{R_c}{R_b}\right)V_2 - \frac{R_c}{R_3}V_3$$

We want to design the circuit such that:  $V_o = 2V_1 + V_2 - 4V_3$

Thus, we need to have:  $\left(\frac{R_a}{R_1}\right)\left(\frac{R_c}{R_b}\right) = 2$ ,  $\left(\frac{R_a}{R_2}\right)\left(\frac{R_c}{R_b}\right) = 1$ , &  $\frac{R_c}{R_3} = 4$

We have three equations & we have to find six unknowns

Let us choose:  $R_a = R_b = R_c = 10k\Omega$

then we have,  $R_3 = \frac{R_c}{4} = \frac{10}{4} = 2.5k\Omega$


$$\left(\frac{R_a}{R_1}\right)\left(\frac{R_c}{R_b}\right) = 2 \Rightarrow \frac{10}{R_1} \times \frac{10}{10} = 2 \Rightarrow R_1 = 5k\Omega$$

$$\left(\frac{R_a}{R_2}\right)\left(\frac{R_c}{R_b}\right) = 1 \Rightarrow \frac{10}{R_2} \times \frac{10}{10} = 1 \Rightarrow R_2 = 10k\Omega$$

5.3 The Non-Inverting Configuration


- Second closed loop configuration
- The input signal,  $V_I$  is applied directly to the positive input terminal of the op-amp, while one terminal of  $R_1$  is connected to ground.

5.3.1 The closed-Loop Gain

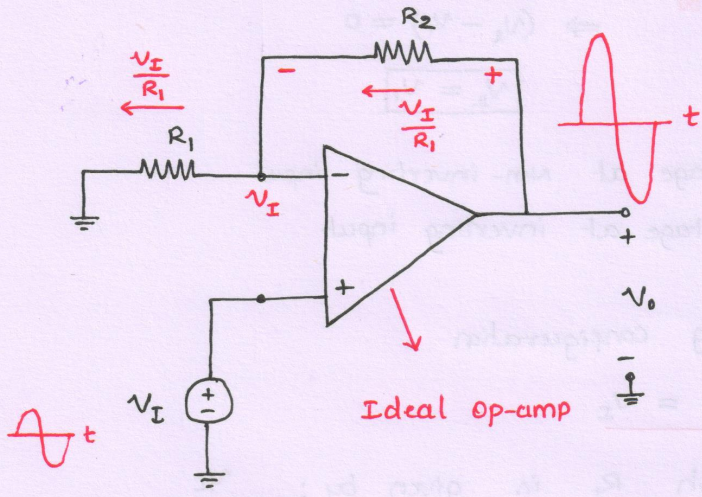

- External components  $R_1$  &  $R_2$  form a closed loop
- Output is fed back to the inverting input terminal.
- Input signal is applied to the non-inverting input terminal

(a) The Non-inverting Configuration

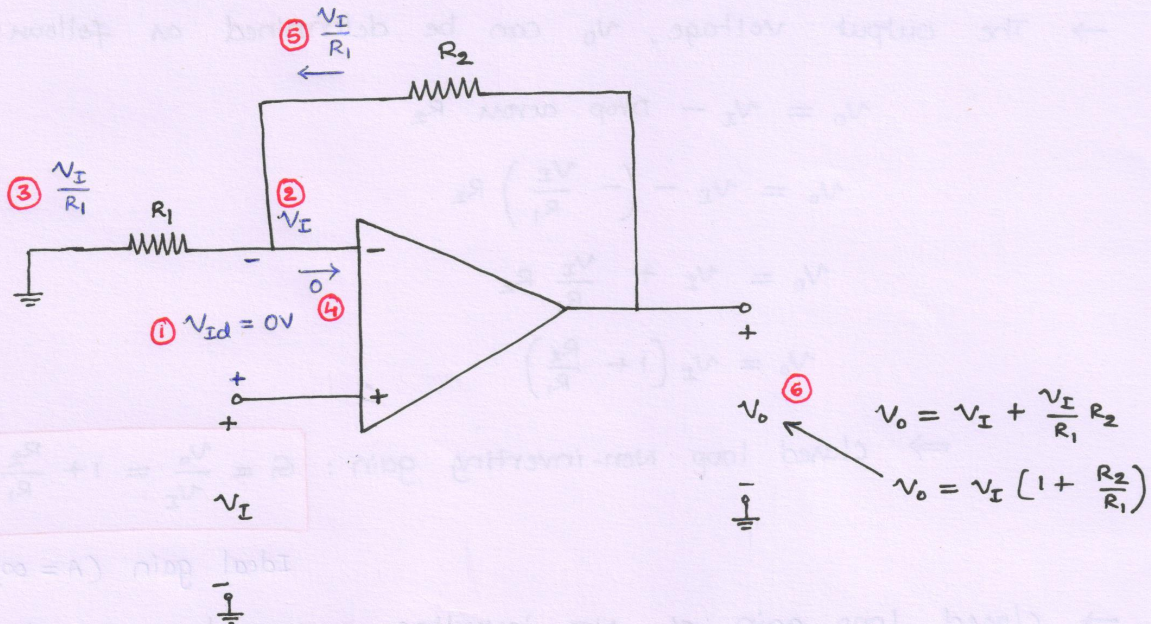

$$V_o = V_I + \frac{V_I}{R_1} R_2$$

$$V_o = V_I \left( 1 + \frac{R_2}{R_1} \right)$$

(b) Analysis of Non-inverting Amplifier circuit

§ To determine closed loop gain:  $G_1$

Assumption: - op-amp is ideal with  $A = \infty$

- virtual short circuit exists between its two input terminals

$$V_o = A (V_2 - V_1)$$

$$\frac{V_o}{A} = (V_2 - V_1) \quad V_{Id}$$

$$\Rightarrow (V_2 - V_1) = 0$$

$$\boxed{V_2 = V_1}$$

$V_2$  = voltage at non-inverting input

$V_1$  = voltage at inverting input

→ For the non-inverting configuration

$$\underline{V_2 = V_1 = V_I}$$

→ The current through  $R_1$  is given by:  $\frac{V_I}{R_1}$

This current will flow through  $R_2$

→ The output voltage,  $V_o$  can be determined as follows:

$$V_o = V_I - \text{Drop across } R_2$$

$$V_o = V_I - \left(-\frac{V_I}{R_1}\right) R_2$$


$$V_o = V_I + \frac{V_I}{R_1} R_2$$

$$V_o = V_I \left(1 + \frac{R_2}{R_1}\right)$$

$$\Rightarrow \text{closed loop non-inverting gain: } \boxed{G_1 = \frac{V_o}{V_I} = 1 + \frac{R_2}{R_1}}$$

Ideal gain ( $A = \infty$ )

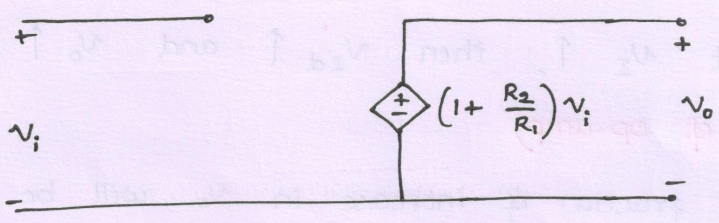
→ closed loop gain of non-inverting configuration depends entirely on external passive components (independent of  $A$ )



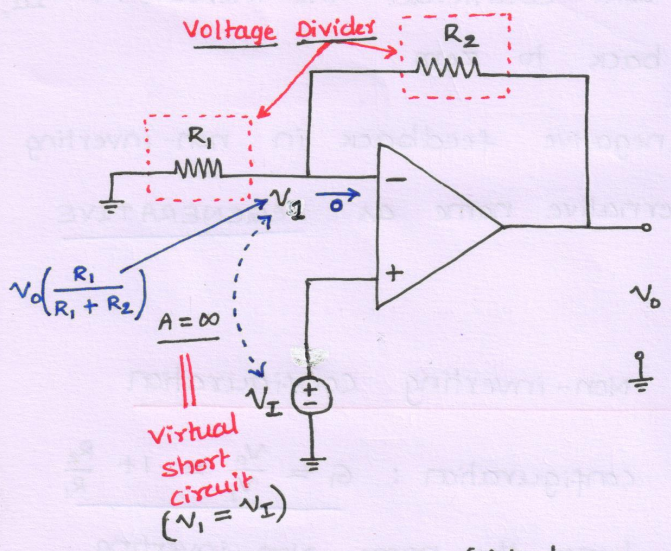(c) Equivalent circuit model for the non-inverting configuration

- Input impedance :  $R_i = \infty$
- Output impedance :  $R_o = 0$
- Voltage gain :  $A_{V_o} = 1 + \frac{R_2}{R_1}$

§ Degenerative Feedback : An insight into the operation of Non-inverting Configuration



→  $R_1$  and  $R_2$  act as a voltage divider feeding a fraction of output voltage,  $V_o$  back to the inverting input of the op-amp (since current into the op-amp inverting input = zero)

$$i.e. \quad V_1 = V_o \left( \frac{R_1}{R_1 + R_2} \right) \quad \text{--- ①}$$

→ Since  $A = \infty$  (ideal op-amp)

⇒ There is a virtual short circuit between the two input terminals of the op-amp

Therefore, the virtual short circuit forces the voltage at the inverting input to be equal to the voltage applied at positive input.

Thus,  $V_o \left( \frac{R_1}{R_1 + R_2} \right) = V_i \Rightarrow$  yields gain  $G_1$  ②

where  $G_1 = \frac{V_o}{V_i} = \left( 1 + \frac{R_2}{R_1} \right)$  (derived earlier)




### 5.3.3 Effect of Finite Open-Loop Gain

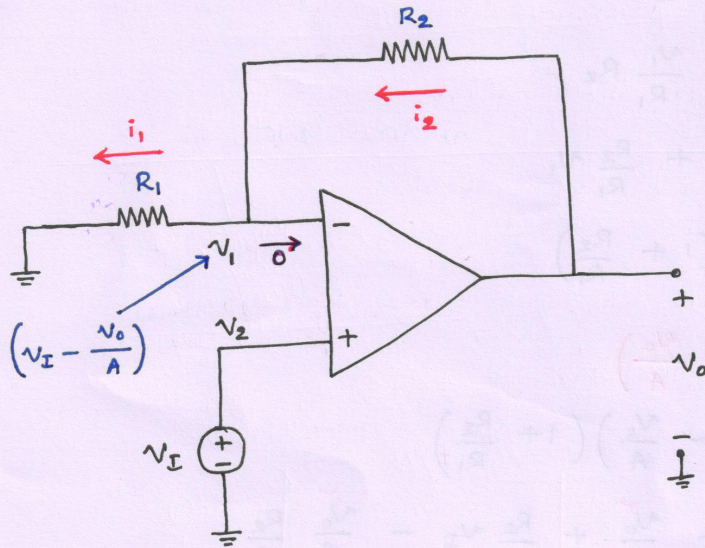(16)

The effect of finite open-loop gain of the op-amp non-inverting configuration is derived as follows:

Assumption: op-amp is ideal, except for open loop gain,  $A$  (i.e.  $A \neq \infty$ )



→ Voltage at inverting input:  $V_1$

$$V_o = A (V_2 - V_1)$$

$$V_o = A (V_I - V_1)$$

$$V_o = A V_I - A V_1$$

$$A V_1 = A V_I - V_o$$

$$V_1 = V_I - \frac{V_o}{A}$$

$$\rightarrow i_1 = \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1}$$

$$i_1 = \frac{V_1}{R_1}$$

$$\rightarrow i_2 = \frac{V_o - V_1}{R_2}$$

→ The op-amp has its input impedance,  $R_i = \infty$ , Therefore

current draw by the op-amp is zero

$$\Rightarrow i_1 = i_2$$
$$\frac{V_1}{R_1} = \frac{V_o - V_1}{R_2}$$

$$\frac{V_1}{R_1} = \frac{V_o - V_1}{R_2}$$

$$V_o - V_1 = \frac{V_1}{R_1} R_2$$

$$V_o = V_1 + \frac{R_2}{R_1} V_1$$

$$V_o = \frac{V_1}{1} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\parallel \left( V_I - \frac{V_o}{A} \right)$$

$$V_o = \left( V_I - \frac{V_o}{A} \right) \left( 1 + \frac{R_2}{R_1} \right)$$

$$V_o = V_I - \frac{V_o}{A} + \frac{R_2}{R_1} V_I - \frac{V_o}{A} \frac{R_2}{R_1}$$

$$V_o \left[ 1 + \frac{1}{A} + \frac{1}{A} \frac{R_2}{R_1} \right] = V_I \left[ 1 + \frac{R_2}{R_1} \right]$$

$$V_o \left[ 1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right) \right] = V_I \left[ 1 + \frac{R_2}{R_1} \right]$$

$$G = \frac{V_o}{V_I} = \frac{\left( 1 + \frac{R_2}{R_1} \right)}{\left[ 1 + \frac{\left( 1 + \frac{R_2}{R_1} \right)}{A} \right]}$$

Non-ideal gain  
( $A \neq \infty$ )

Observations:

→ The denominator of eqn. ① is similar to that of finite loop gain eqn. of inverting configuration.

⇒ Feedback loop of inverting configuration

|| Equal

Feedback loop of Non-inverting configuration

→ The numerator of eqn. ① is :  $1 + \frac{R_2}{R_1}$  (17)

whereas numerator of finite loop gain equation of inverting configuration is :  $-\frac{R_2}{R_1}$

→ For  $A = \infty$ , in eqn. ①,

$$G = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1}\right) : \text{Ideal \& Non-inverting gain}$$

→ For  $A \gg 1 + \frac{R_2}{R_1}$

$$\text{OR} \quad 1 \gg \frac{\left(1 + \frac{R_2}{R_1}\right)}{A}$$

then  $G = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1}\right) : \text{Ideal non-inverting gain}$

### 5.3.4 The Voltage Follower

→ Comparison of Ideal vs Non-ideal gain of Non-inv. Amplifier

Let  $\frac{R_2}{R_1} = 9$

→ if  $A = \infty$ , Ideal closed loop gain,  $G = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$

$$G = 1 + 9 = 10$$

$$\boxed{G = 10}$$

→ if  $A = 10^5$ , Non-ideal closed loop gain,  $G = \frac{V_o}{V_i} =$

$$G = \frac{\left(1 + \frac{R_2}{R_1}\right)}{\left[1 + \frac{1 + \frac{R_2}{R_1}}{A}\right]} = \frac{1 + 9}{\left[1 + \frac{1 + 9}{10^5}\right]}$$

$$G = \frac{10}{1 + 10 \times 10^{-5}} = 9.999$$

Error is 1-part in 10,000 which is 0.01%

### 5.3.4 The Voltage Follower

→  $R_i = \text{High}$  for non-inverting configuration

→ This property enables us to use non-inverting configuration as a buffer amplifier

||  
connects a source with a high-impedance  
to a low-impedance load

→ Buffer amplifier : Do not provide gain  
but

It is a impedance transformer

→ For non-inverting configuration :


setting,  $R_2 = 0$  (short circuit)

$R_1 = \infty$  (open circuit)


} unity-gain Amplifier

||  
Voltage follower

(commonly referred)

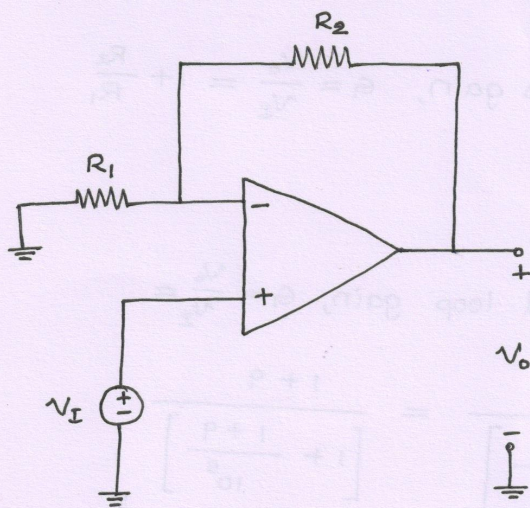

(a) non-inverting configuration

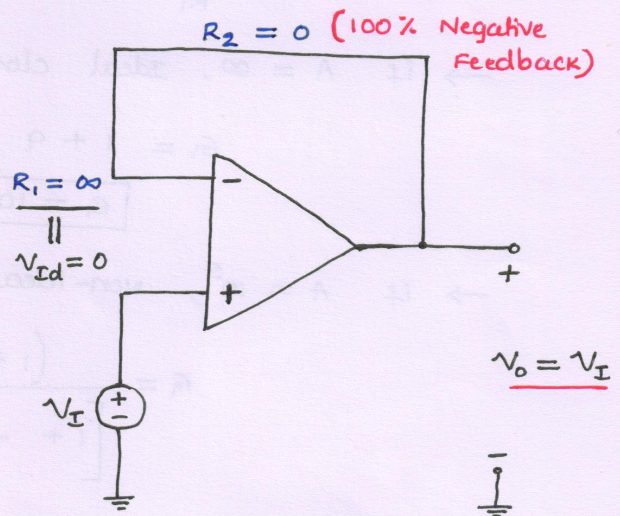

(b) voltage follower

→ For the unity-gain buffer or follower amplifier, the output follows the input.

→ For the non-inverting configuration, the ideal closed loop

gain is:  $G = \frac{V_o}{V_I} = \left(1 + \frac{R_2}{R_1}\right)$  — ①

if we make,  $R_2 = 0$  and  $R_1 = \infty$  then

eqn. ① changes to:  $G = \frac{V_o}{V_I} = \left(1 + \frac{0}{\infty}\right)$

$\Rightarrow G = \frac{V_o}{V_I} = 1$

Unity gain


$V_o = V_I$

→ In ideal case, the voltage follower as:

$V_o = V_I$


$R_{in} = \infty$

$R_{out} = 0$

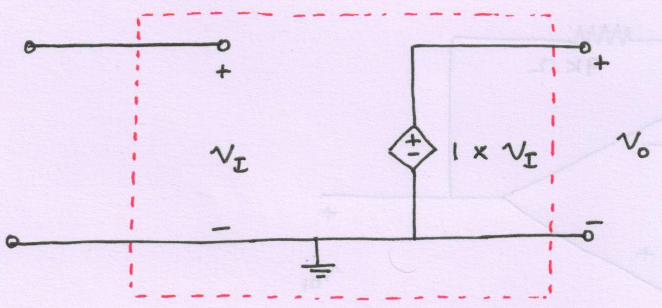


Voltage Follower Equivalent circuit Model

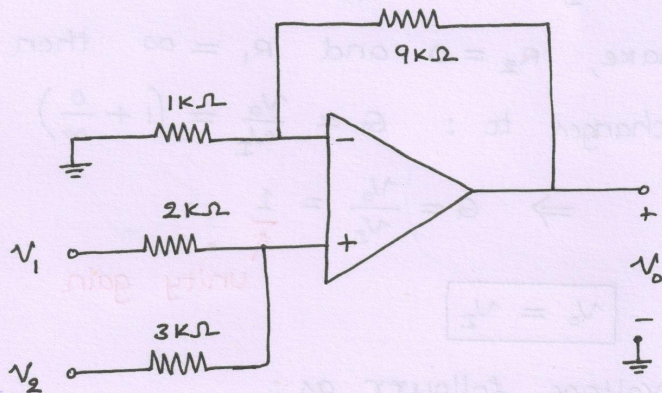Exercise 5.9: using the superposition principle, find the output voltage for the circuit shown.



Solution: using the principle of superposition, we find the output voltage as follows:

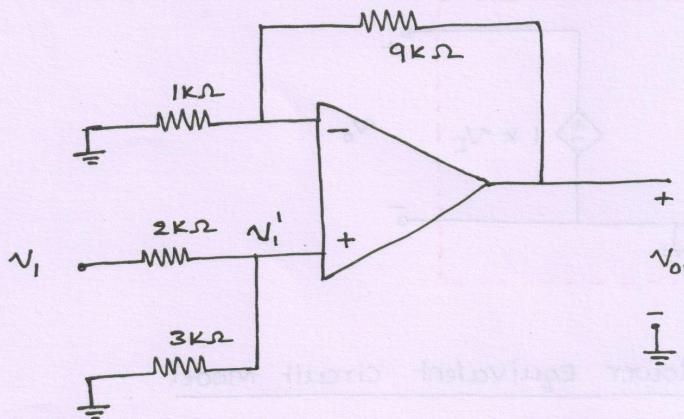⊗ contribution of  $V_1$  to  $V_0$ , set  $V_2 = 0$



$$V_1' = V_1 \frac{3}{3+2} = 0.6 V_1$$


$$\text{Thus } V_{o1} = \left(1 + \frac{9k}{1k}\right) \times 0.6 V_1$$

$$V_{o1} = 10 \times 0.6 V_1 = 6 V_1 \Rightarrow \boxed{V_{o1} = 6 V_1}$$

⊗ contribution of  $V_2$  to  $V_0$ , set  $V_1 = 0$

$$V_2' = \frac{2}{2+3} V_2 = 0.4 V_2$$
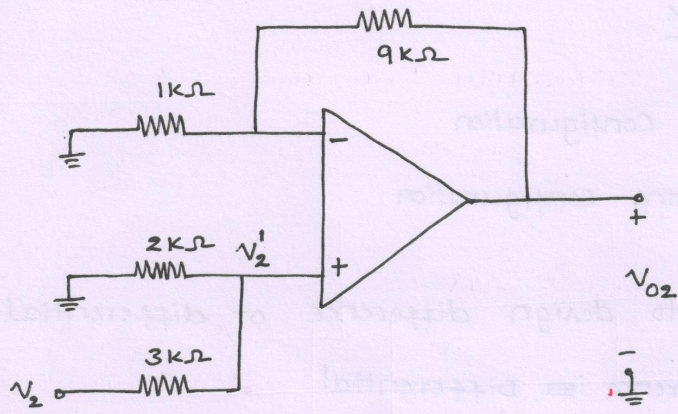
$$\text{Thus, } V_{o2} = \left(1 + \frac{9k}{1k}\right) V_2' = 10 \times 0.4 V_2 \Rightarrow \boxed{V_{o2} = 4 V_2}$$



Thus, overall output voltage,  $V_o = V_{o1} + V_{o2}$

$$V_o = 6V_1 + 4V_2$$


Exercise D5.11: Design a non-inverting amplifier with a gain of 2. At the maximum output voltage of 10V, the current in the voltage divider is to be 10μA.

Solution:  $G = 2$

We know that,  $G = 1 + \frac{R_2}{R_1}$  for non-inverting config<sup>n</sup>

$$2 = 1 + \frac{R_2}{R_1}$$
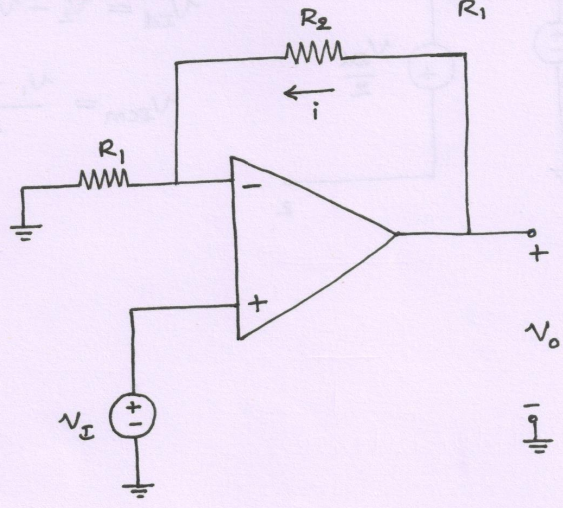
$$\frac{R_2}{R_1} = 1 \Rightarrow R_2 = R_1$$



if  $V_o = 10V$ , then it is desired that  $i = 10\mu A$

$$\text{Thus, } i = \frac{10V}{R_1 + R_2} = 10\mu A$$

$$\Rightarrow R_1 + R_2 = \frac{10V}{10\mu A}$$

$$R_1 + R_2 = 1M\Omega$$

since  $R_1 = R_2$

$$\Rightarrow R_1 = 0.5M\Omega \quad \text{and} \quad R_2 = 0.5M\Omega$$

## 5.4 Difference Amplifiers



Preview: Inverting Configuration

Non-inverting Configuration


→ Op-amps are used to design difference or differential amplifier      **difference  $\equiv$  Differential**

→ A differential amplifier is one that responds to the difference between the two input signals applied at its input and ideally rejects signals that are common to the two inputs.

→ Recall

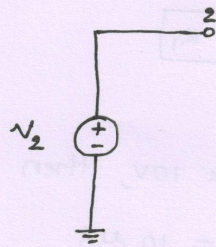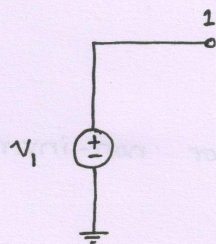

$\equiv$

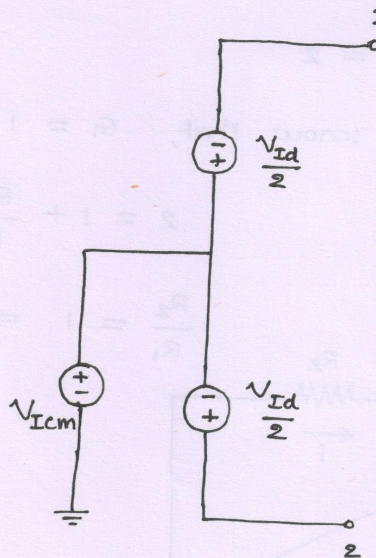


$$V_1 = V_{Icm} - \frac{V_{Id}}{2}$$

$$V_2 = V_{Icm} + \frac{V_{Id}}{2}$$

$$V_{Id} = V_2 - V_1$$

$$V_{Icm} = \frac{V_1 + V_2}{2}$$



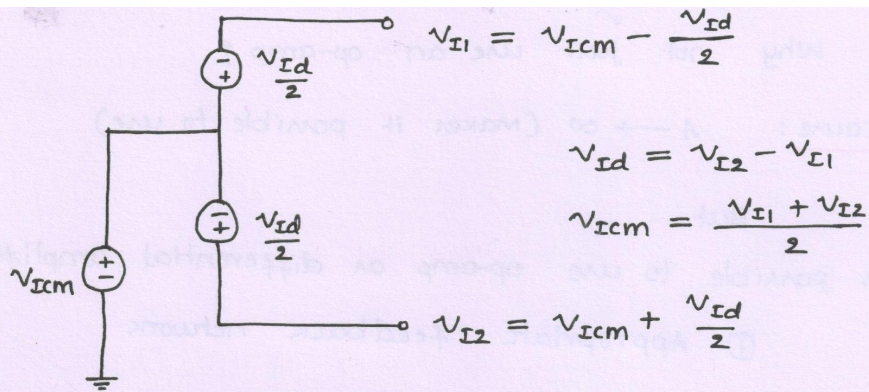

(b) Representation of the input signals in terms of their differential and common mode components

Difference amplifier :

Amplifies  $\longrightarrow$  differential input signal ( $V_{Id}$ )

Rejects  $\longrightarrow$  common mode input signal ( $V_{Icm}$ )

$$V_o = \underbrace{A_d}_{\substack{\uparrow \\ \text{Differential} \\ \text{gain}}} V_{Id} + \underbrace{A_{cm}}_{\substack{\uparrow \\ \text{common mode} \\ \text{gain (Ideally, zero)}}} V_{Icm}$$

Efficiency of differential amplifier is measured by

- ① Degree of rejection of  $V_{Icm}$
- ② preference to  $V_{Id}$

This is usually quantified by a measure known as:

Common Mode Rejection Ratio (CMRR)

$$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|}$$

by default op-amp : Differential Amplifier

Why not just use an op-amp?

Because:  $A \rightarrow \infty$  (Makes it possible to use)

But

It is possible to use op-amp as differential amplifier by

① Appropriate feedback network

② Finite closed loop gain,  $G_f$

↑ predictable & stable

### 5.4.1 A Single op-amp Difference Amplifier


Non-inverting configuration  $\rightarrow \left(\frac{V_o}{V_i}\right) = 1 + \frac{R_2}{R_1} \rightarrow$  positive

Inverting configuration  $\rightarrow \left(\frac{V_o}{V_i}\right) = -\frac{R_2}{R_1} \rightarrow$  Negative

combining two configurations



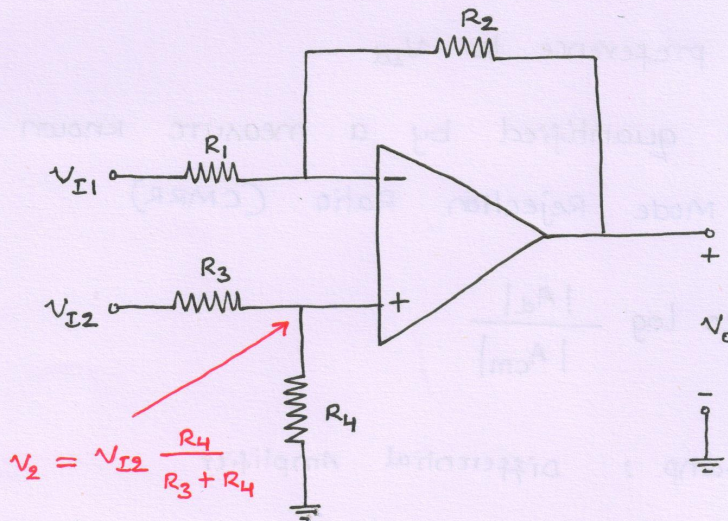
step in right direction to  
get the difference between  
two input signals



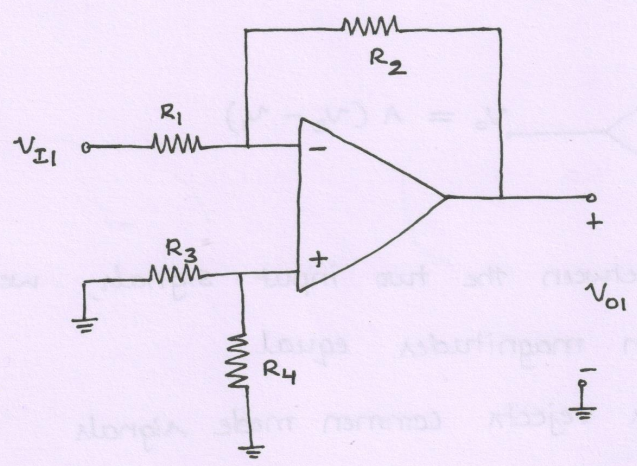(a) A Difference Amplifier

Applying superposition principle :


⊗ Contribution of  $V_{I1}$  to output,  $V_o$  : Assume  $V_{I2} = 0$



The equivalent circuit is an "Inverting configuration"

Therefore, 
$$V_{o1} = - \frac{R_2}{R_1} V_{I1}$$

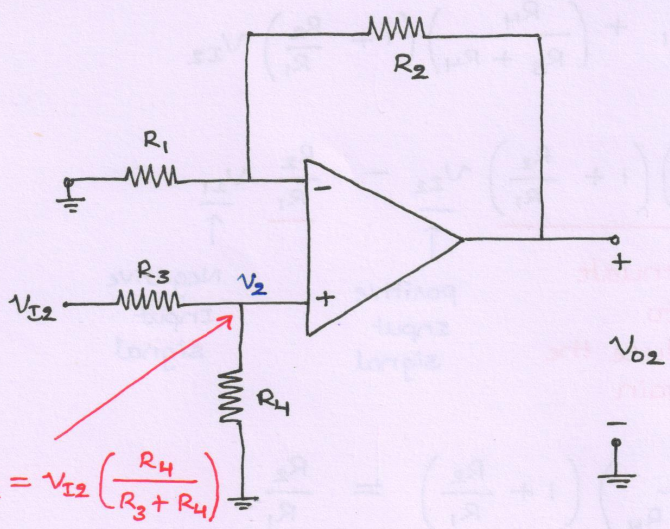⊗ Contribution of  $V_{I2}$  to output,  $V_o$  : Assume  $V_{I1} = 0$



The equivalent circuit is a "Non-inverting configuration"

Therefore,

$$V_{o2} = V_2 \left( 1 + \frac{R_2}{R_1} \right)$$

$$V_2 = V_{I2} \left( \frac{R_4}{R_3 + R_4} \right)$$

$$V_{o2} = V_{I2} \left( \frac{R_4}{R_3 + R_4} \right) \left( 1 + \frac{R_2}{R_1} \right)$$


⊗ Overall output voltage,  $V_o$  of the difference amplifier is the sum of  $V_{o1}$  and  $V_{o2}$

Thus we have,  $V_o = V_{o1} + V_{o2}$

$$V_o = - \frac{R_2}{R_1} V_{I1} + V_{I2} \left( \frac{R_4}{R_4 + R_3} \right) \left( 1 + \frac{R_2}{R_1} \right)$$

§ The output voltage of op-amp in open-loop mode is

$$V_o = A (V_2 - V_1)$$

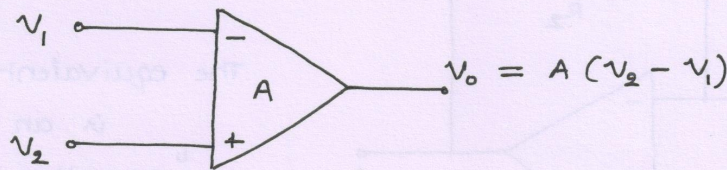

§ To get the difference between the two input signals, we have to make the two gain magnitudes equal

⇒ This rejects common mode signals

consider output voltage,  $V_o$  of difference amplifier

$$V_o = -\frac{R_2}{R_1} V_{I1} + \left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) V_{I2}$$

or

$$V_o = \underbrace{\left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right)}_{\text{Attenuate to reduce the gain}} V_{I2} - \frac{R_2}{R_1} V_{I1}$$

↑ positive input signal
↑ Negative input signal

Therefore,  $\left(\frac{R_4}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) = \frac{R_2}{R_1}$

$$\frac{1}{\left(1 + \frac{R_3}{R_4}\right)} \left(1 + \frac{R_2}{R_1}\right) = \frac{R_2}{R_1}$$

$$1 + \frac{R_2}{R_1} = \frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4}\right)$$

$$1 + \frac{R_2}{R_1} = \frac{R_2}{R_1} + \frac{R_2 R_3}{R_1 R_4}$$

||

1 (For LHS = RHS)

$$1 + \frac{R_2}{R_1} = \frac{R_2}{R_1} + \frac{R_2}{R_1}$$

$$R_3 = R_1 \text{ and } R_2 = R_4$$

condition to work as a difference amplifier

$$\Rightarrow \text{LHS} = \text{RHS}$$

Therefore, eqn. ① changes to

$$V_o = \left( \frac{R_4}{R_3 + R_4} \right) \left( 1 + \frac{R_2}{R_1} \right) V_{I2} - \frac{R_2}{R_1} V_{I1}$$

Applying matching condition for the 1<sup>st</sup> term


$$\parallel \frac{R_2}{R_1}$$

$$V_o = \frac{R_2}{R_1} V_{I2} - \frac{R_2}{R_1} V_{I1}$$

$$V_o = \frac{R_2}{R_1} (V_{I2} - V_{I1})$$

$$\text{Differential Gain : } A_d = \frac{V_o}{V_{I2} - V_{I1}} = \frac{R_2}{R_1}$$

Common Mode Gain :  $A_{cm}$

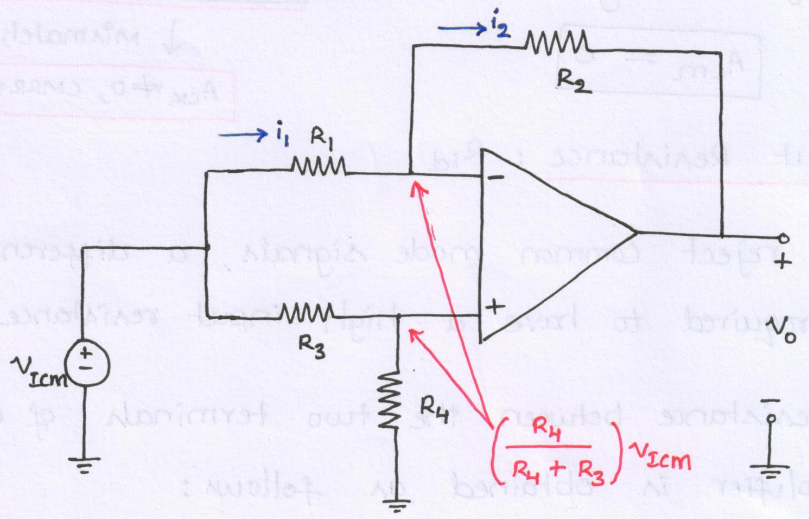

$$i_1 = \frac{V_{ICM} - \frac{R_4}{R_4 + R_3} V_{ICM}}{R_1}$$

$$i_1 = \frac{V_{ICM}}{R_1} \left[ \frac{R_4 + R_3 - R_4}{R_4 + R_3} \right]$$

$$i_1 = V_{ICM} \frac{R_3}{R_4 + R_3} \frac{1}{R_1}$$

The output voltage,  $V_o$  is given by

$$V_o = \frac{R_4}{R_4 + R_3} V_{ICM} - \frac{i_2 R_2}{\parallel}$$

Drop across  
 $R_2$

Substituting  $i_2 = i_1$ , since op-amp do not draw current

$$V_o = \frac{R_4}{R_4 + R_3} V_{ICM} - V_{ICM} \frac{R_3}{R_4 + R_3} \frac{1}{R_1} R_2$$

$$V_o = \frac{R_4}{R_4 + R_3} V_{ICM} - \frac{R_2}{R_1} \frac{R_3}{R_4 + R_3} V_{ICM}$$

$$V_o = \frac{R_4}{R_4 + R_3} V_{ICM} \left[ 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right]$$

$$\text{Common Mode Gain (A}_{cm}) = \frac{V_o}{V_{ICM}} = \left( \frac{R_4}{R_4 + R_3} \right) \left[ 1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right]$$

if we apply matching condition :  $R_1 = R_3$  &  $R_2 = R_4$

then  $A_{cm} = 0$


↓ mismatch

$$A_{cm} \neq 0, CMRR \neq \infty$$

§ Differential Input Resistance :  $R_{id}$

→ In addition to reject common mode signals, a difference amplifier is required to have a high input resistance.

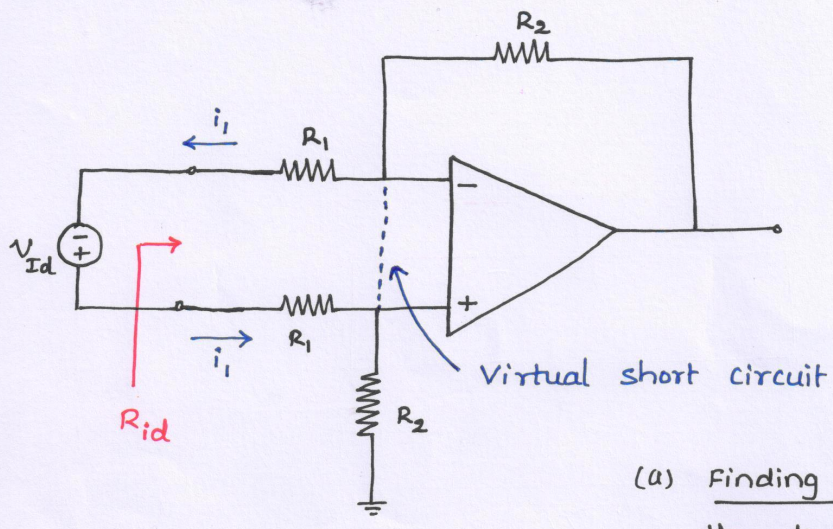→ The input resistance between the two terminals of a difference amplifier is obtained as follows:



$$\left. \begin{aligned} R_3 &= R_1 \\ R_4 &= R_2 \end{aligned} \right\} \text{Assumption}$$

(a) Finding the input resistance of the difference amplifier

Now  $R_{id} \equiv \frac{V_{Id}}{i_1}$

The two input terminals of the op-amp track each other in potential. Therefore, we may write loop equation as

$$-V_{Id} + i_1 R_1 + \overbrace{0}^{\substack{\uparrow \\ \text{Virtual short} \\ \text{circuit}}} + i_1 R_1 = 0$$

$$V_{Id} = 2 i_1 R_1$$

$$R_{id} = \frac{V_{Id}}{i_1} = 2 R_1$$

→ If differential amplifier is required to have large differential gain, then  $R_1 = \text{small}$

i.e.  $A_d = \frac{R_2}{R_1}$  ; for large  $A_d$ ,  $R_1 = \text{small}$   
 Not easy to vary (Drawback)

⇒  $R_{id} = \text{Input resistance} = 2 R_1$  (small)

⇒ Drawback of the differential amplifier