

Introduction \Rightarrow (In 1 ϕ s/m 2 wires are supply for transmission voltage to load is motor (P-n)

Any electrical equipment such as generator, transformer, & receptor having only one winding is called a 1 ϕ system

\rightarrow if no of ϕ armature windings are increased it becomes polyphase system it

\rightarrow A two phase generator has two windings displaced by 90° & produces 2-phase voltage means 2-phase means equal voltage

\rightarrow Similarly 3-phase generator has 3 windings carries equal voltage & displaced by 120° & it is popularly used,

\rightarrow The generation, transmission & utilization of electric power are carried out by 3- ϕ system.

Advantages of 3 ϕ system:

- 1) 3- ϕ apparatus is more efficient than a 1 ϕ phase apparatus
(*) 3 ϕ machine gives a higher output than 1 ϕ machine
- 2) For the same capacity, 3 ϕ apparatus costs less than 1 ϕ apparatus.
(*) voltage regulation in 3 ϕ system is better than that in 1 ϕ supply
- 3) Size of 3 ϕ apparatus is smaller in size than the size of 1 ϕ apparatus of same capacity & hence requires less material for construction
- 4) 3 ϕ motors produce uniform torque whereas the torque produced by 1 ϕ motor is pulsating
- 5) 3 ϕ motors are self starting whereas 1 ϕ phase motors are not self starting.
- 6) Power factor of 1 ϕ motors is poor than of motors of same ratings
- 7) Instantaneous power of 3 ϕ is constant whereas it is fluctuating in 1 ϕ . this fluctuating power causes vibration in wind.

①



8) In case of star system 2-different voltages can be obtained, one b/w lines & other b/w line & phase whereas in Δ only one voltage can be obtained.

Generation of 3 ϕ AC - ~~supply~~ voltage : \rightarrow

In 3 ϕ system there are ~~3~~ 3-equal voltages of same frequency ^{but phase} displaced from one another by 120° electrical.

These voltages are produced by 3 ϕ generator which has 3-identical windings. When these windings are rotated in a magnetic field, emf induced in winding, or phase

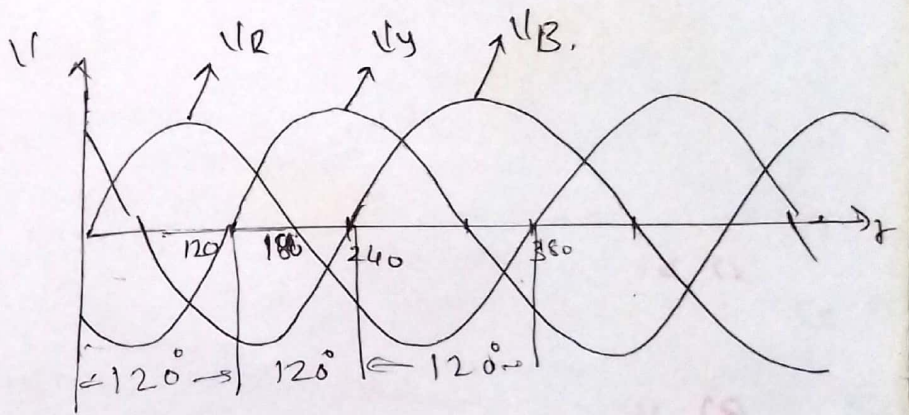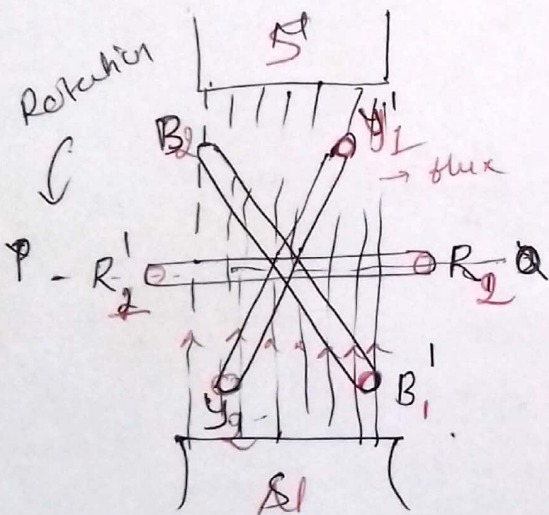These emf are same magnitude & frequency but phase displacement will be 120°



3- ϕ waveform

V_B lags

V_B lags V_Y by 120°

V_Y lags V_R by 120°

Phase Diagram for induced emf

(*) Let V_R, V_Y, V_B are 3 independent voltages induced in

as $R_1, R_2, Y_1, Y_2, B_1, B_2$

→ when coils R_1, R_2 are in the position PQ as shown below & is increases in +ve direction ωt is indicated by V_R as shown in waveform.

→ coils Y_1, Y_2 is 120° electrically behind R_1, R_2 . The emf induced in this coil is -ve & is approximately -ve value as shown in V_Y waveform

→ Similarly coil B_1, B_2 is electrically 240° behind R_1, R_2 or 120° behind Y_1, Y_2

→ Therefore emf induced in 3-coils are of same magnitude & frequency but 120° electrically from each other

Q) From the phasor diagram V_R is assumed to be reference voltage & is zero for the instant as shown. At same instant V_Y is displaced by 120° & will follow V_R , while V_B is ahead of V_R by 120°

$$V_R = V_m \sin \omega t$$

$$V_Y = V_m \sin(\omega t - 120^\circ)$$

$$V_B = V_m \sin(\omega t - 240^\circ)$$

$$= V_m \sin(\omega t + 120^\circ)$$

∴ Sum of all 3-voltage at a instant is zero

$$V_R + V_Y + V_B = 0.$$

It can be proved mathematically also


$$\text{Let } V_R + V_Y + V_B = 0$$

$$= V_m [\sin \omega t + \sin(\omega t - 120^\circ) + \sin(\omega t + 120^\circ)]$$

$$= V_m \left[\sin \omega t + \sin \omega t \cdot \cos 120^\circ - \cos \omega t \cdot \sin 120^\circ + \sin \omega t \cdot \cos 120^\circ + \cos \omega t \cdot \sin 120^\circ \right]$$

$$= V_m [\sin \omega t + 2 \sin \omega t \cdot \cos 120^\circ] = V_m \left[\sin \omega t + 2 \sin \omega t \left(-\frac{1}{2}\right) \right] = 0 \quad (3)$$

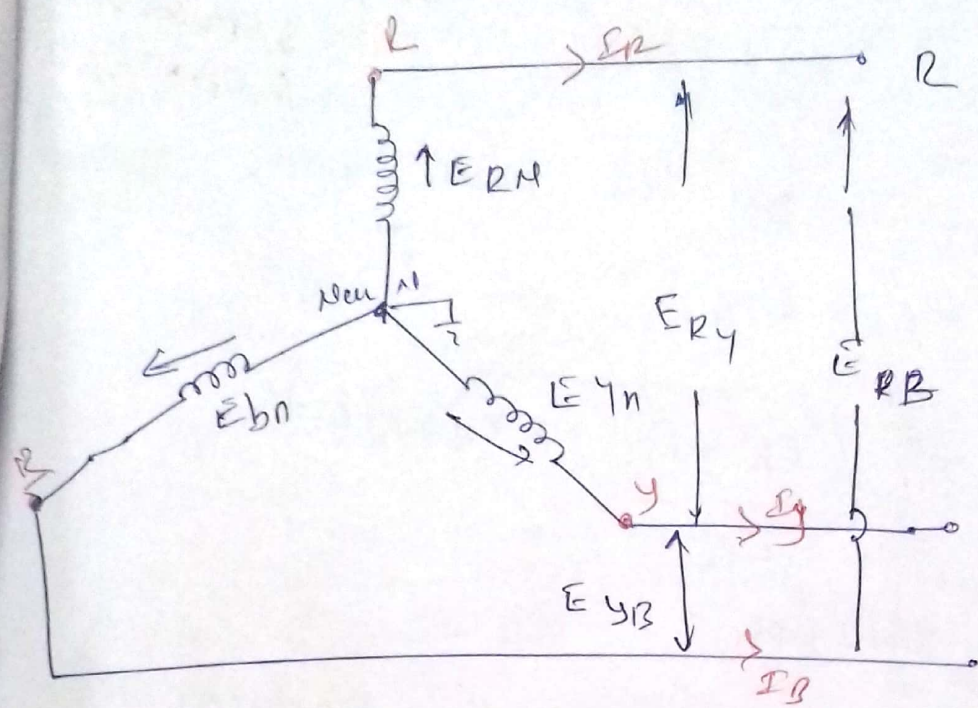Relation B/w line & phase values for star connection



(*) * Starting end (connection) finishing terminal


end of the 3 coils are connected to point N as known as neutral pt

(*) E_{RN} , E_{YN} & E_{BN} are the phase voltages & each one of them equal to E_{ph}

(*) E_{RY} , E_{YB} , E_{RB} are line voltages & each one of them E_L

(*) Line Voltage : potential difference b/w any 2-line's supply is called line voltage & current passing through any line is called line current

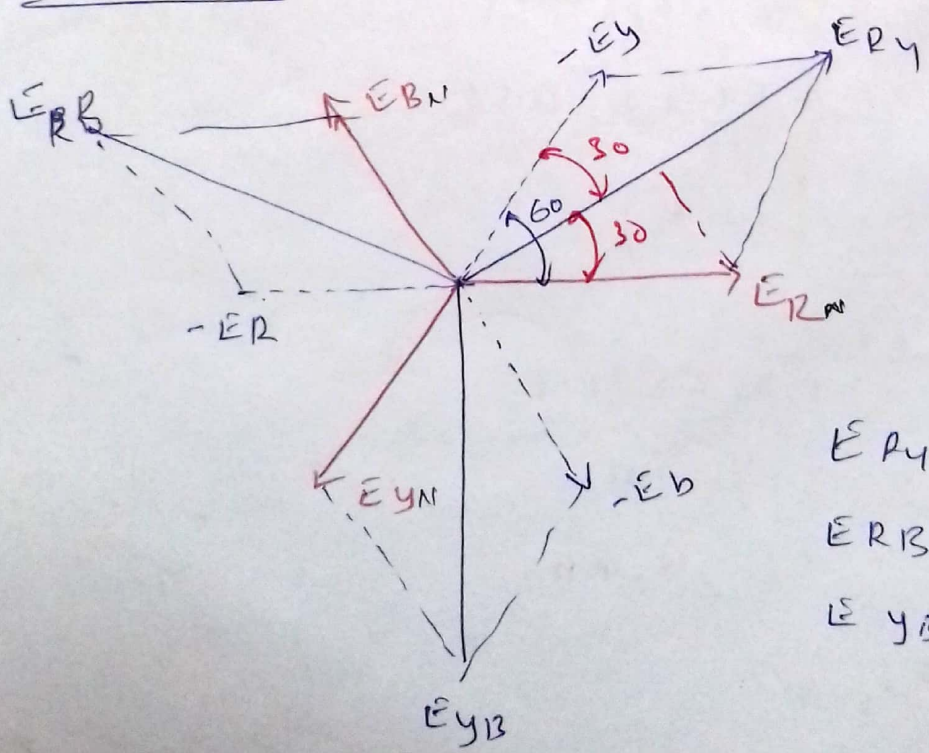(*) Phase Voltage : potential difference b/w line & neutral



vector sum of E_R & $-E_Y$ give E_{RY}
angle b/w E_R & $-E_Y = 60^\circ$

$$E_{RY} = E_R - E_Y$$

$$E_{RB} = E_R - E_B$$

$$E_{YB} = E_Y - E_B$$

$$E_{RY} = E_R - E_Y \quad (\text{vector difference})$$

$$= E_R + (-E_Y) \quad (\text{vector sum})$$

from the vector dia

$$E_{RY} = \sqrt{E_R^2 + E_Y^2 + 2E_R E_Y \cos 60^\circ} \quad (\text{Law's of parallelogram})$$

$$E_R = E_Y = E_{ph}$$

$$E_{RY} = 2 E_{ph} \cdot \cos 30^\circ$$

$$= \frac{3}{2} E_{ph} \cos 30^\circ$$

$$= \frac{3}{2} E_{ph} \times \frac{\sqrt{3}}{2}$$

let $E_R + E_Y + E_B$ are the phase voltages

$$E_R = E_Y = E_B = E_{ph}$$

line voltage $E_{RY} = \sqrt{E_{ph}^2 + E_{ph}^2 + 2E_{ph} E_{ph} \cos 60^\circ}$

$$= \sqrt{3 E_{ph}^2}$$

$$E_L = \sqrt{3} E_{ph}$$

(*) In star connected system each line conductor is connected to separate phase, hence line & phase currents are same

(*) Current flows through the lines are equal in magnitude.

$$I_L = I_{ph}$$

$$\text{Total power} = 3 E_{ph} \cdot I_{ph} \cdot \cos \phi$$

$$= 3 \frac{E_L}{\sqrt{3}} \times I_L \cos \phi$$

$$\boxed{\text{Power} = \sqrt{3} E_L I_L \cos \phi}$$


$$\text{Apparent power} = \sqrt{3} E_L I_L = \text{VA}$$

$$= 3 E_{ph} \cdot I_{ph}$$

h / 01 $\cos \phi = \frac{1}{2}$

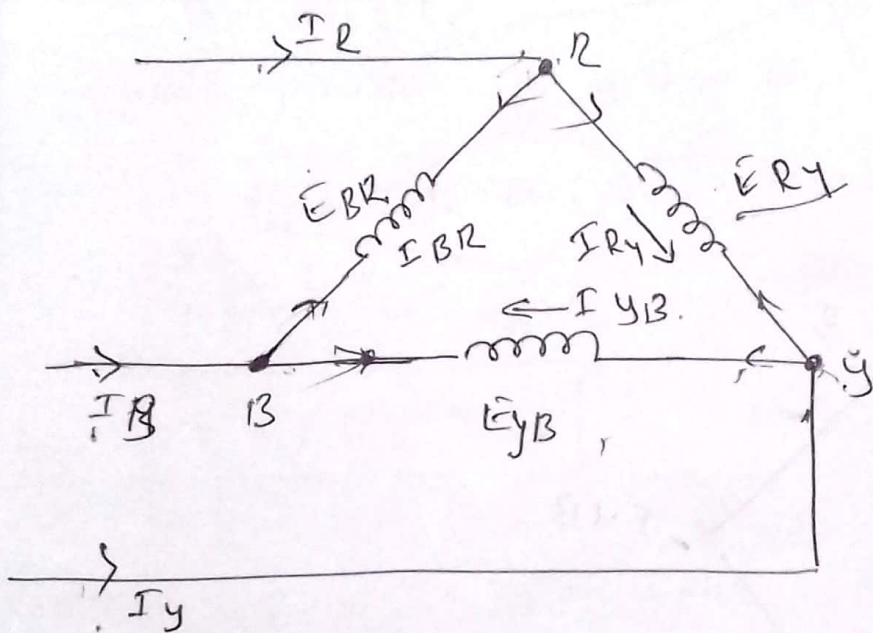1) Relation B/w line & phase values for Delta connected load : \rightarrow

Delta connection is formed when one end of the winding connected to starting end of other & connections are continued to form a closed loop.



~~Line voltage $E_{RY} = E_{YB} = E_{BR} = V_L$~~

~~Phase voltage $= V_{ph} = E_{RY} = E_{BR} = V_{BR} =$~~


Line voltage $= E_{RY} = E_{YB} = E_{BR} = E_L$

Phase voltage $= E_{RY} = E_{YB} = E_{BR} = E_{ph}$.

$\therefore E_L = E_{ph}$.

Line current $= I_R = I_Y = I_B = I_L$

$I_{ph} = I_{RY} = I_{YB} = I_{BR}$

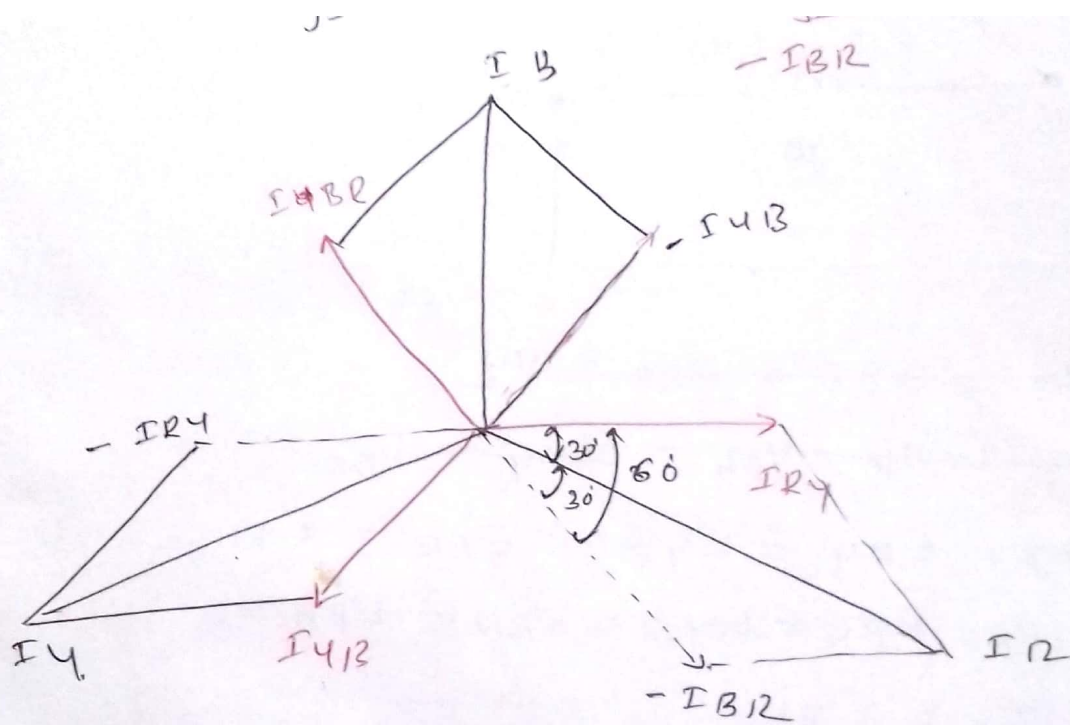

$$\left. \begin{aligned} I_R &= I_{RY} - I_{BR} \\ I_Y &= I_{YB} - I_{RY} \end{aligned} \right\}$$

$$I_B = I_{BR} - I_{YB}$$

$$I_R = I_{RY} - I_{BR} \quad (\text{vector diff.})$$

$$I_R = I_{RY} - (+I_{BR}) \quad (\text{vector sum})$$

$$I_R = \sqrt{I_{RY}^2 + I_{BR}^2 + 2I_{RY} \cdot I_{BR} \cdot \cos 60^\circ}$$

(7)

$$I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + I_{ph}^2}$$

$$= \sqrt{3} I_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

for star connection

$$E_L = \sqrt{3} E_{ph}$$

$$I_L = I_{ph}$$

for Delta connection

$$E_L = E_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

3-phase power is given by

$$P = 3 E_{ph} \cdot I_{ph} \cdot \cos \phi \rightarrow \text{Power}$$

$$= 3 E_L \cdot \frac{I_L}{\sqrt{3}} \cdot \cos \phi$$

$$P = \sqrt{3} E_L I_L \cos \phi$$

per phase

$$P_{\text{phase}} = E_{ph} I_{ph} \cos \phi$$


Q1) apparent power = $3 E_{ph} \cdot I_{ph}$

$$3 \cdot E_L \times \frac{I_L}{\sqrt{3}}$$

$$= \sqrt{3} E_L \cdot I_L$$

Q2) A balanced 3 ϕ - star connected load of $(8+j6)$ per phase is connected to a 3- ϕ 230V supply, find line current, power factor, power, reactive power, ~~power~~ & voltage drop.

5

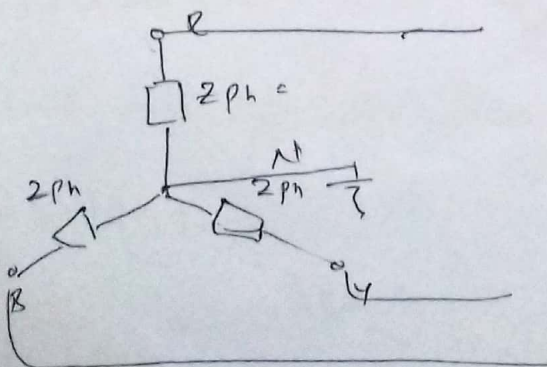

$$Z = (8+j6) = 10 \angle 36.86^\circ$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = 132.79 \text{ V}$$

$$\text{Phase current } (I_p) = \frac{132.79}{10} = 13.27$$

$$I_L = I_{ph} = 13.27 \text{ A}$$

$$\phi = \cos^{-1}(0.8) = 36.86$$

$$\therefore \text{Power factor} = \frac{R}{Z} = \frac{8}{10} = 0.8$$

$$P = \sqrt{3} I_L V_L \cos \phi = \sqrt{3} \times 13.27 \times 230 \times 0.8 = 4231.98 \text{ W}$$

$$Q = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} \times 230 \times 13.27 \times 0.6 = 3173.98 \text{ VAR}$$

$$S = \sqrt{3} V_L I_L = \sqrt{3} \times 230 \times 13.27 = 5289.97 \text{ VA}$$

8

Q1) calculate the active & reactive power of each phase of star connected 10KV Δ generator supply by ~~5 MW~~ at 0.8 p.f. If the total current remains same, when load p.f. raised to 0.9 calculate new o/p & its active & reactive component per phase

$$\Rightarrow P = 5\text{ MW} = 3\text{ phases} \times 0.8 \quad \text{p.f. } V_L = 10\text{KV star}$$

$$P = \sqrt{3} V_L I_L \cos\phi$$

$$5 \times 10^6 = \sqrt{3} \times 10 \times 10^3 \times I_L \times 0.8$$

$$I_L = 360.84 \text{ A} = I_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = 5773.50 \text{ V.}$$

(*) Active component of each phase = $V_{ph} \cdot I_{ph} \cdot \cos\phi$
 $= 1.666 \text{ MW}$

(*) reactive " " " = $V_{ph} \cdot I_{ph} \sin\phi = 2.5 \text{ MVAR}$

Now current remains but $\cos\phi_2 = 0.9$

$$P_T = \sqrt{3} V_L I_L \cos\phi = \sqrt{3} \times 10 \times 10^3 \times 360.84 \times 0.9$$

$$= 5.625 \text{ MW}$$

Now Active component of each phase = $V_{ph} \cdot I_{ph} \cdot \cos\phi$
 $= 1.875 \text{ MW}$

reactive " " " = $V_{ph} \cdot I_{ph} \cdot \sin\phi_2$
 $= 0.9081 \text{ MVAR}$

(P)

(a)

A Balanced star connected load is supplied from a balanced 3 ϕ , 400V, 50Hz system. The current in each phase 30A & lags 30° behind the phase voltage. Find
 1) total power 2) phase voltage & Draw the phasor diagram


$V_L = 400V$

$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231V$

$E_{RY} = E_R + (-E_Y)$


$I_{ph} = 30A = I_L$

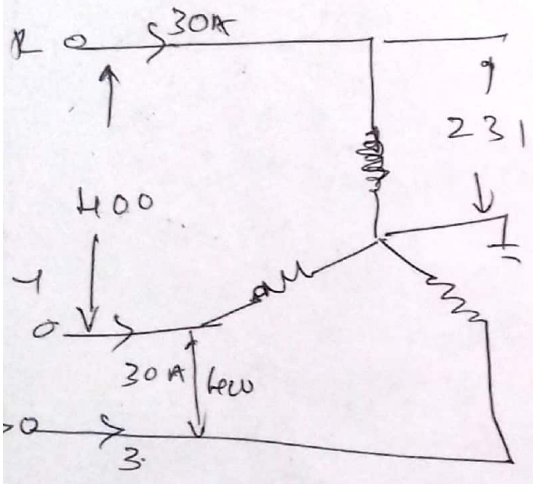Power factor = $\cos \phi = \cos 30^\circ = 0.866$



Total power = $3 E_{ph} \cdot I_{ph} \cos \phi$
 $= 3 \times 231 \cdot 30 \times 0.866$
 $= 18 kW$

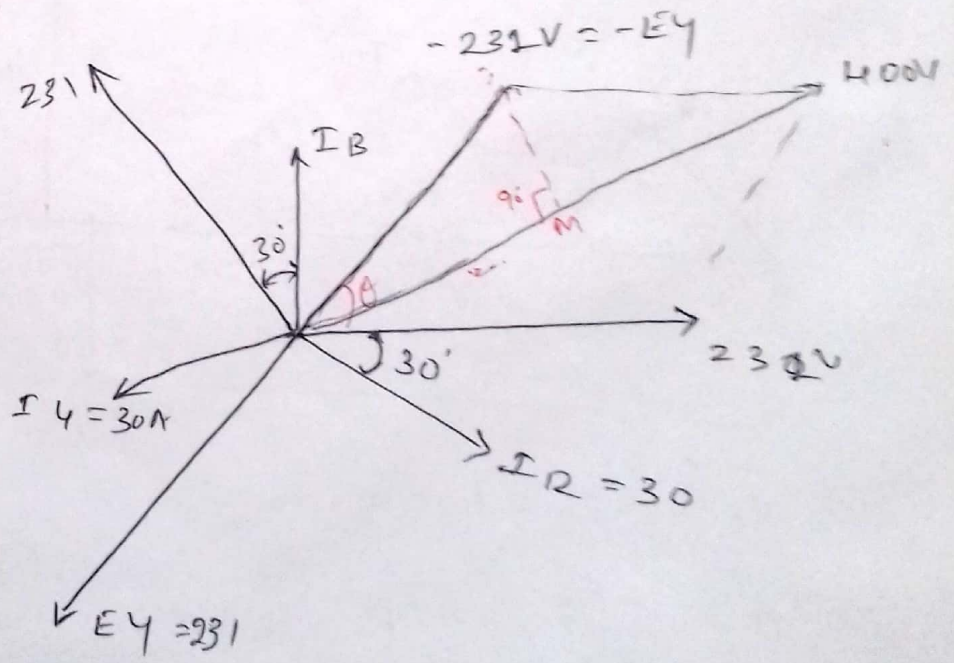$\cos 30 = \frac{OM}{231}$
 $OM = 231 \cos 30 = 231 \cdot 0.866$
 $= 200$




②

④

3-equal impedance, each having a resistance of 8 Ω & inductive reactance of 6 Ω are connected in
 1) star 2) Delta, a/c 3 ϕ 400V system Find
 Phase current 2) line current 3) total power consumed

⑩

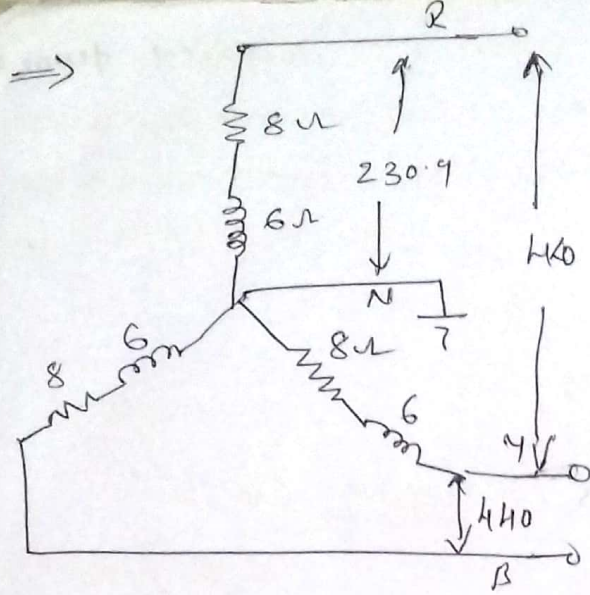

$$V_L = 400V$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.9V$$

$$Z_{ph} = \sqrt{R^2 + X_L^2} = \sqrt{8^2 + 6^2} = 10$$


$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.9}{10} = 23.09A$$

$$I_{ph} = I_L = 23.09A$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$\cos \phi = \frac{R}{Z_{ph}} = \frac{8}{10} = 0.8$$
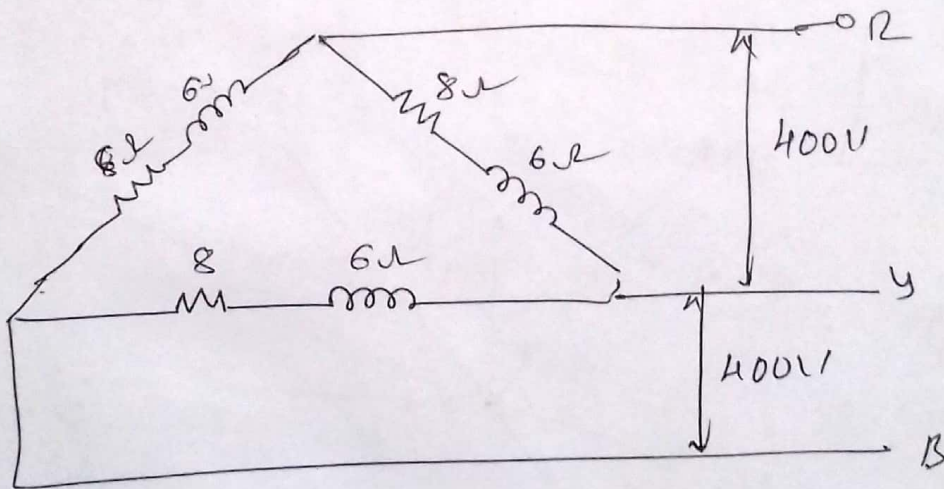
$$P = \sqrt{3} \times 400 \times 23.09 \times 0.8 = 12.79 \text{ kW}$$



$$V_L = V_{ph} = 400V$$

$$I_{ph} = \frac{400}{10} = 40A$$

$$I_L = \sqrt{3} \times 40 = 69.28A$$

$$P = \sqrt{3} E_L I_L \cos \phi$$

$$= \sqrt{3} \times 69.28 \times 400 \times 0.8 = 38.39 \text{ kW}$$

3 ϕ Delta connected load consumes a power of 60 kW taking a lagging current of 200 A at a line voltage of 400 V. Find the parameters of each phase. What would be the power consumed, if the load were connected in star?

$$\Rightarrow P = 60 \text{ kW} \quad I_L = 200 \text{ A} \quad V_L = 400 \text{ V} \quad (7)$$

$$P = \sqrt{3} V_L I_L \cos \phi = 60 \times 10^3 = \sqrt{3} \times 400 \times 200 \cos \phi$$

$$\cos \phi = 0.433 \quad \text{i.e.} \quad \phi = \cos^{-1}(0.433) = 64.34$$

(I_{ph} lags V_{ph})

for Delta $V_L = V_{ph} = 400 \text{ V}$ $I_{ph} = \frac{I_L}{\sqrt{3}} = 115.47$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{115.47} = 3.464 \Omega$$

$$Z_{ph} = 3.464 \angle 64.34^\circ \Omega = 1.5 + j3.1225$$

$$R_{ph} = 1.5 \Omega \quad X_{L_{ph}} = 3.1225$$

$$X_{L_{ph}} = 2\pi f L_{ph} = L_{ph} = \frac{3.1225}{2\pi \times 50} = 9.939 \text{ mH}$$

~~for~~ star connected

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 \text{ V} \quad (6)$$


$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{3.464} = 66.67 = I_L$$

$$\cos \phi = 0.433$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 66.67 \times 0.433 = 20 \text{ kW}$$

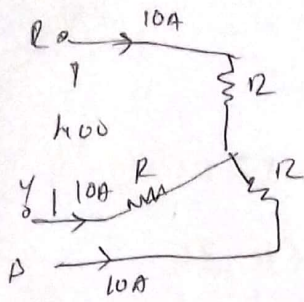- ③ 3-similar resistors are connected in star all across 3- ϕ supply. The line current is 10A. calculate
 (1) value of each resistor (2) line voltage required to give the same line current if the resistors are connected in




$$I_L = I_{ph} = 10A$$

$$V_L = 400$$

$$V_{ph} = \frac{400}{\sqrt{3}} = 230.91$$

$$R = \frac{230.91}{10} = 23.09\Omega$$

Delta \rightarrow

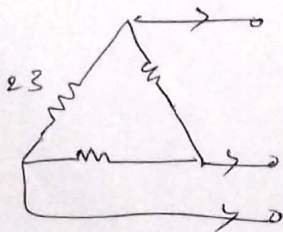

$$I_L = 10A$$

$$I_{ph} = \frac{10}{\sqrt{3}} = 5.77$$

$$R = 23.09$$

$$V_{ph} = I_{ph} \cdot R \\ = 5.77 \times 23.09 \\ = 133.3V$$

$$V_L = V_{ph} = 133.3V$$


(*) while solving 3 ϕ problem

- (1) given supply voltages are line voltage
- (2) determine phase voltage depending on whether load is \star or Delta
- (3) determine phase current

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$
- (4) determine line current depending whether load is Δ or Star
- (5) ϕ is angle b/w V_{ph} & I_{ph} value can be obtained from given Z_{ph}
- (6) Total power consumed = $\sqrt{3} V_L I_L \cos \phi$

$$= 3 V_{ph} I_{ph} \cos \phi$$

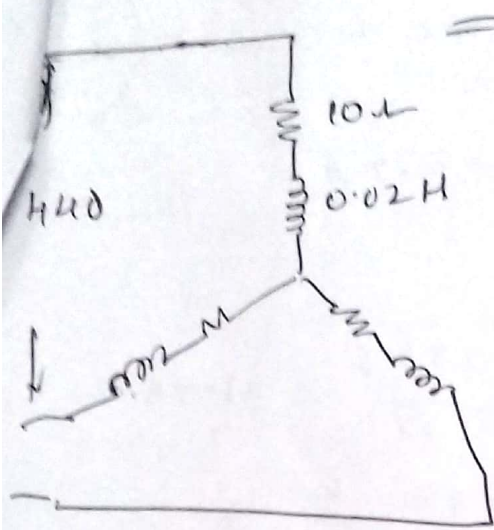3-coils each having resistance of 10Ω & inductance of $0.02H$ are connected in star to a $440V, 50Hz, 3\phi$ supply. Calculate the line current & total power consumed.



$$\Rightarrow X_L = 2\pi fL = 2\pi \times 50 \times 0.02 = 6.28\Omega$$

$$R = 10\Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 6.28^2} = 11.81\Omega$$

$$V_L = 440$$

$$V_{ph} = \frac{440}{\sqrt{3}} = 254.03V$$

$$I_{ph} = \frac{V_{ph}}{Z} = \frac{254.03}{11.81} = 21.51A = I_L$$


$$P = \sqrt{3} V_L I_L \cos\phi$$

$$= \sqrt{3} \times 440 \times 21.51 \times \frac{R}{Z}$$

$$P = 13.88 kW$$

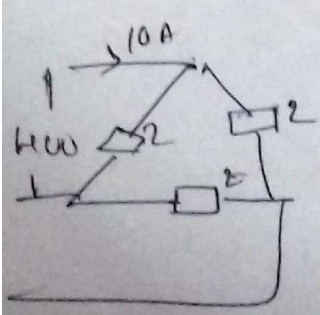(7)

(*) a 3ϕ load of 3 equal impedances connected in Δ -ac to a balanced $400V$ supply takes $10A$ at a power factor of 0.7 (lagging) calculate
 ① Phase current ② Total power ③ The total reactive kVA
 if windings are connected in star, what will be the new real & reactive power



$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{10}{\sqrt{3}} = 5.774A$$

$$Z = \frac{V_{ph}}{I_{ph}} = \frac{400}{5.774} = 69.27\Omega$$

$$P = \sqrt{3} V_L I_L \cos\phi$$

$$= \sqrt{3} \times 400 \times 10 \times 0.7$$


$$= 4.849 kW$$

$$\phi = \cos^{-1}(0.7) = 45.57^\circ$$

$$\text{reactive kVA} = \sqrt{3} V_L I_L \sin\phi$$

$$= \sqrt{3} \times 400 \times 10 \times \sin(45.57)$$

$$= 4.947 kVAR$$

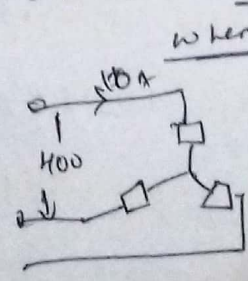

when star

$$Z = 69.27\Omega$$

$$I_{ph} = \frac{V_{ph}}{Z} = \frac{400}{69.27}$$

$$I_{ph} = 5.774 = I_L$$

$$P = \sqrt{3} \times 400 \times 5.774 \times 0.7 = 1.619 kW$$

(14)

wattmeter


It is device used to measure the power when connected in 1 ϕ & 3 ϕ system, in watts

① ~~current~~ wattmeter has 2-coils

① current coil

② potential coil & voltage coil.


① current coil

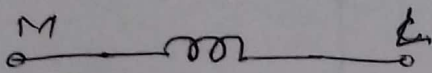

This senses the current & always connected in series with the load.


& It is similar to Ammeter. The resistance of this coil is as small as possible & hence its cross-section area is large & it has less number of turns.

② voltage coil

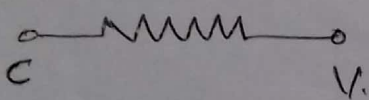


It is also called as potential coil or pressure coil. This senses the voltage & is always connected across the

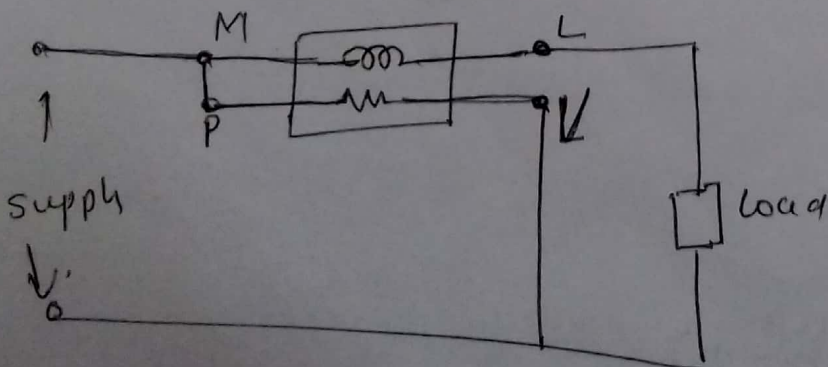
supply terminals, similar to voltmeter. Resistance of this coil is large & its cross section area is small, hence large no's of turns.



2- wattmeter method :- ?

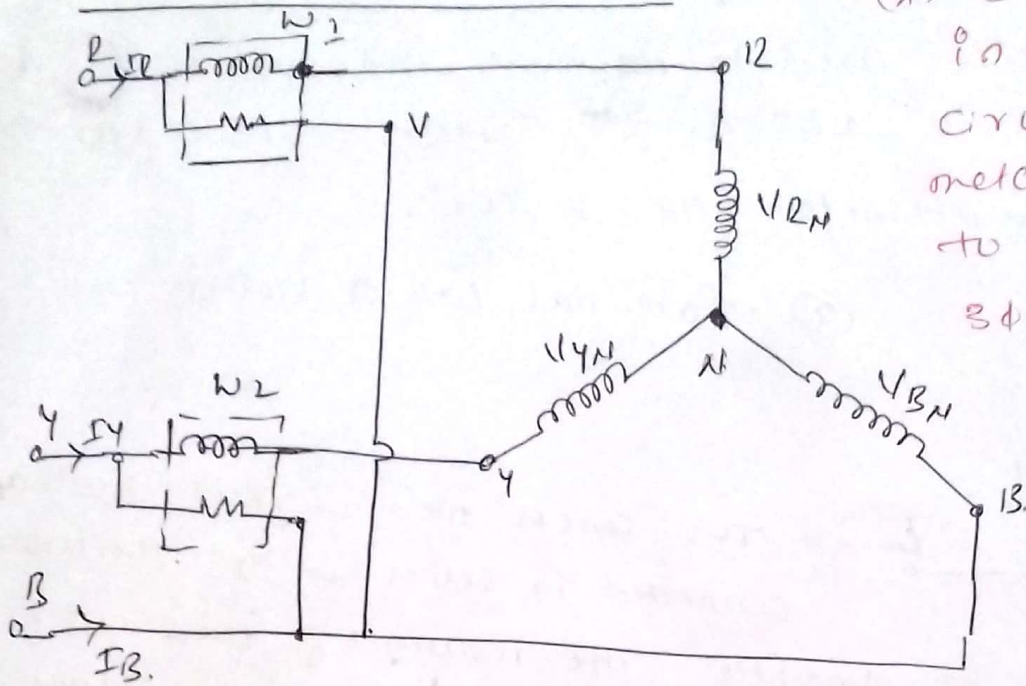

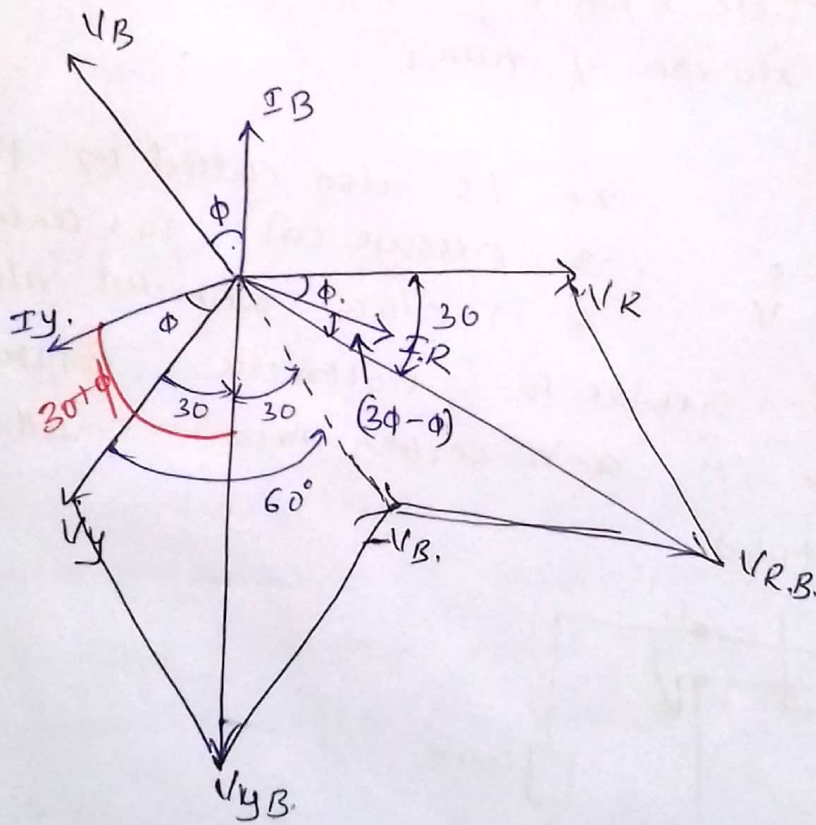(*) show that W_1 is a balanced 3 ϕ circuit two watt meters are sufficient to measure the total 3 ϕ power & power factor of the load



$$W_1 = I_R \cdot V_{RB} \cdot \cos(30 - \phi)$$

$$W_2 = I_Y \cdot V_{YB} \cdot \cos(30 + \phi)$$

$$I_R = I_Y = I_B = I_L$$

$$V_{RB} = V_{RY} = V_{YB} = V_L$$

(17)

$$\begin{aligned}
 \omega_1 + \omega_2 &= \underline{I}_R \cdot \underline{V}_{RB} \cos(30^\circ - \phi) + I_Y \cdot V_{YB} \cos(30^\circ + \phi) \\
 &= I_L V_L [\cos(30^\circ - \phi) + \cos(30^\circ + \phi)] \quad (10) \\
 &= I_L V_L \left[\cos 30^\circ \cdot \cos \phi + \sin 30^\circ \cdot \sin \phi + \cos 30^\circ \cdot \cos \phi - \sin 30^\circ \cdot \sin \phi \right] \\
 &= I_L V_L [2 \cos 30^\circ \cdot \cos \phi] \\
 &= I_L V_L \left[\cancel{2} \times \frac{\sqrt{3}}{\cancel{2}} \times \cos \phi \right] \\
 &= I_L V_L \sqrt{3} \cos \phi
 \end{aligned}$$

$$\boxed{\omega_1 + \omega_2 = \sqrt{3} V_L I_L \cos \phi} \quad \rightarrow (1)$$

Expression for P.f.:

$$\begin{aligned}
 \omega_1 - \omega_2 &= V_L I_L [\cos(30^\circ - \phi) - \cos(30^\circ + \phi)] \\
 &= V_L I_L \left[\cancel{\cos 30^\circ} \cdot \cos \phi + \sin 30^\circ \cdot \sin \phi - \cancel{\cos 30^\circ} \cdot \cos \phi + \sin 30^\circ \cdot \sin \phi \right] \\
 &= V_L I_L [2 \sin 30^\circ \cdot \sin \phi] \\
 &= V_L I_L \left[\cancel{2} \times \frac{1}{\cancel{2}} \sin \phi \right]
 \end{aligned}$$

$$\omega_1 - \omega_2 = V_L I_L \sin \phi \quad \rightarrow (2)$$

divide (2) \div (1) we get

$$\frac{\omega_1 - \omega_2}{\omega_1 + \omega_2} = \frac{V_L I_L \sin \phi}{\sqrt{3} V_L I_L \cos \phi} = \frac{1}{\sqrt{3}} \tan \phi$$

$$\tan \phi = \frac{\sqrt{3} (\omega_1 - \omega_2)}{\omega_1 + \omega_2} \quad \text{OR} \quad \phi = \tan^{-1} \left[\frac{\sqrt{3} (\omega_1 - \omega_2)}{\omega_1 + \omega_2} \right]$$

$$\text{P.f.} = \cos \phi$$

$$\text{P.f.} = \cos \left[\tan^{-1} \left\{ \frac{\sqrt{3} (\omega_1 - \omega_2)}{\omega_1 + \omega_2} \right\} \right]$$

(18)

① The power flowing in a 3 ϕ , 3 wire balanced load system is measured by 2-wattmeter method. The readings in wattmeter A is 750 watts & wattmeter B is 1500 watts. What is power factor of the system & load current per phase

$$W_1 = 750 \text{ W} \quad W_2 = 1500$$

$$\begin{aligned} \cos \phi &= \cos \left\{ \tan^{-1} \left[\frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} \right] \right\} \\ &= \cos \left\{ \tan^{-1} \left[\frac{\sqrt{3} (750 - 1500)}{750 + 1500} \right] \right\} \Rightarrow \cos \left\{ \tan^{-1} (-0.2911) \right\} \\ &= \cos (-29.11) \\ &= 0.873 \text{ (leading)} \end{aligned}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

$$(750 + 1500) = \sqrt{3} V_L I_L \cdot 0.873$$

$\sqrt{3} V_L I_L = 1500 \text{ VA}$ \rightarrow if V_L is known, I_L can be obtained, hence load current per phase can be obtained

(*) A balanced 3 ϕ , star connected load draws power from 440V supply. The 2-wattmeters connected indicate $W_1 = 5 \text{ kW}$ & $W_2 = 1.2 \text{ kW}$ calculate power, P.f, current in CA

$$\Rightarrow V_L = 440 \text{ V} \quad W_1 = 5 \text{ kW}, \quad W_2 = 1.2 \text{ kW}$$

$$P = W_1 + W_2 = 5 + 1.2 = 6.2 \text{ kW}$$

$$\begin{aligned} \cos \phi &= \cos \left\{ \tan^{-1} \left[\frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \right] \right\} = \cos \left\{ \tan^{-1} \left[\frac{\sqrt{3} (5 - 1.2)}{6.2} \right] \right\} \\ &= \cos \left\{ \tan^{-1} (1.0615) \right\} \\ &= 0.6857 \text{ (lagging)} \end{aligned} \quad (14)$$

$$P = \sqrt{3} V_L I_L \cos \phi = 6.2 \text{ kW} = \sqrt{3} \times 440 \times I_L \times 0.6857 \quad (I_L = 11.86 \text{ A})$$

(*) 3- similar impedences are connected in Δ ac a 3 ϕ supply. The 2 wattmeters are connected to measure the Δ p power indicate 12kW & 7kW calculate

1) Power Δ p & 2) power factor of the load

$$\Rightarrow W_1 = 12 \text{ kW} \quad \& \quad W_2 = 7 \text{ kW}$$

$$P_{in} = W_1 + W_2 = 12 + 7 = 19 \text{ kW}$$

$$\cos \phi = \cos \left[\tan^{-1} \left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right) \right] = 0.4099$$

(*) Power is measured in 3 ϕ Balanced load using 2-wattmeters. The line voltage is 400V. & The load & its P.f is so adjusted that the line current is always 10A. Find the readings of the wattmeters when P.f is i) unity 2) 0.866 iii) 0.5 & 4) 0

$$\Rightarrow V_L = 400 \text{ V}, \quad I_L = 10 \text{ A} \quad V_L I_L = 4000$$

The wattmeter reads are

$$W_1 = V_L I_L \cos(30 - \phi) \quad \& \quad W_2 = V_L I_L \cos(30 + \phi)$$

① $\cos \phi = 1 \Rightarrow \phi = 0^\circ$

$$W_1 = 4000 \times \cos(30) = 3464.1 \text{ W}$$

$$W_2 = 4000 \times \cos(30) = 3464.1 \text{ W}$$

② $\cos \phi = 0.866 \quad \phi = 30^\circ$

$$W_1 = 4000 \cos(30 - 30), \quad W_2 = 4000 \cos(30 + 30)$$

$$= 4000$$

$$= 2000 \text{ W}$$

③ $\cos \phi = 0.5, \quad \phi = 60^\circ$

$$W_1 = 4000 \cos(30 - 60) = 3464.1$$

$$W_2 = 4000 \cos(30 + 60) = 0$$


4) $\cos \phi = 0 \quad \phi = 90^\circ$

$$W_1 = 4000 \cos(30 - 90) = 2000 \text{ W}$$

$$W_2 = 4000 \cos(30 + 90) = -2000 \text{ W}$$

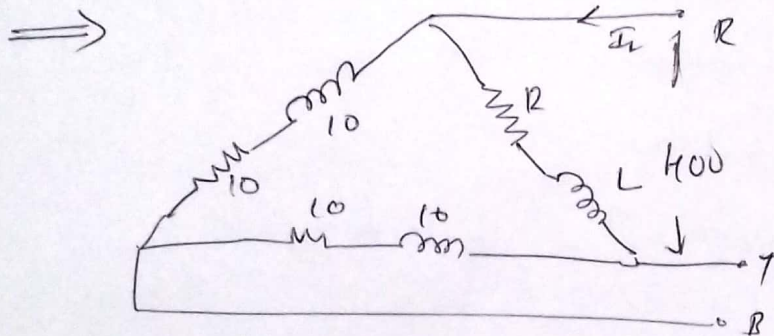(20)

(*) Three identical coils each having $R = 10\Omega$ & inductive reactance of 10Ω are connected in delta to a $400V$, 3ϕ supply. Find the current & reading on the two wattmeters connected to measure power.



$$V_L = V_{ph} = 400V$$

$$Z_{ph} = \sqrt{10^2 + 10^2} = 14.14\Omega$$

$$I_L = \sqrt{3} I_{ph}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{14.14} = 28.29A \Rightarrow I_L = \sqrt{3} \times 28.29 = 49A$$

$$\cos\phi = \frac{R}{Z} = \frac{10}{14.14} = 0.707$$

$$P = \sqrt{3} V_L I_L \cos\phi \Rightarrow \sqrt{3} \times 400 \times 49 \times 0.707 = 24001W$$

$$W_1 + W_2 = 24001W \rightarrow (1)$$

$$P_T = \cos\phi \left\{ \tan^{-1} \left(\frac{\sqrt{3} (W_1 - W_2)}{24001} \right) \right\} \Rightarrow$$

$$0.707 = \cos\phi \left\{ \tan^{-1} \left(\frac{\sqrt{3} (W_1 - W_2)}{24001} \right) \right\}$$

$$\cos^{-1}(0.707) = 45^\circ$$

$$\tan^{-1} \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2}$$

$$W_1 - W_2 = 13856.98W \rightarrow (2)$$

$$W_1 = 18928.99W$$

$$W_2 = 5072.01W$$

(81)

(*) each of the 2-wattmeters connected to measure the i/p to a 3 ϕ ckt reads 20kw. what does each instrument reads when p.f is 0.866 lagging with the total 3 ϕ power remaining unchanged in the altered condition?

$$\Rightarrow W_1 + W_2 = 20 + 20 = 40 \text{ kW} \rightarrow \textcircled{1}$$

$$0.866 = \cos \phi \tan^{-1} \left(\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right)$$

$$W_1 - W_2 = 13.355 \text{ kW} \rightarrow \textcircled{2}$$

$$W_1 = 26.6675 \text{ kW} \quad W_2 = 13.3325 \text{ kW}$$

(*) A 415V 3 ϕ motor has o/p of 80H.P & operates at a power factor of 0.866 with an η of 90%. calculate

① The current in each phase of motor if the motor is connected in Δ

② The readings of the two wattmeters connected in the line to measure the i/p power

$$\Rightarrow \text{motor o/p power} = 80 \times 735.35 = 58828 \text{ W}$$

$$\eta = \frac{\text{o/p}}{\text{i/p}} \quad \text{motor i/p} = \frac{58.82 \text{ kW}}{0.9} = 65.364 \text{ kW}$$

$$W_1 + W_2 = 65.364 \text{ kW} \rightarrow \textcircled{1}$$

$$\cos \phi = 0.866 = 30^\circ \quad \boxed{\phi = 30^\circ}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$65.364 \times 10^3 = \sqrt{3} \times 415 \times I_L \times 0.866$$

$$I_L = 105 \text{ A}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$= 60.62 \text{ A}$$

$$\tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

$$(W_1 - W_2) = 21.788 \text{ W} \rightarrow \textcircled{2}$$

$$\tan(30) = \frac{\sqrt{3}(W_1 - W_2)}{65.364}$$

$$0.577 \times 65.364 = \sqrt{3}(W_1 - W_2)$$

$$\boxed{\begin{matrix} W_1 = 43.57 \text{ kW} \\ W_2 = 21.788 \end{matrix}} \quad \textcircled{23}$$