



**ACS College of Engineering**  
Approved by AICTE New Delhi, Affiliated to VTU, Belagavi  
(A Unit of RajaRajeswari Group of Institutions)



**Department of Electronics and Communication Engineering**

**ANALOG CIRCUITS LABORATORY MANUAL**

**Subject Code: 18ECL48**

**Prepared by**

**Mrs. Aishwaryaa LK**  
**Assistant Professor, Dept. Of ECE**

**Checked By**  
**Dr. H B Bhuvaneswari**  
**HOD, Dept. Of ECE**



**Affiliated to Visvesvaraya Technological University, Belagavi, Karnataka -**

**590018**

**2019-2023**

<b>ANALOG CIRCUITS LABORATORY SEMESTER – III (EC/TC)</b> <b>[As per Choice Based Credit System (CBCS) scheme]</b>			
<b>Laboratory Code</b>	<b>21ECL35</b>	<b>CIE Marks</b>	<b>50</b>
<b>Number of Lecture Hours/Week</b>	<b>02 Hr. Tutorial(Instructions) + 02 Hours Laboratory</b>	<b>SEE Marks</b>	<b>50</b>
<b>RBT Level</b>	<b>L1, L2, L3</b>	<b>Exam Hours</b>	<b>03</b>
<b>CREDITS – 01</b>			
<b>Course objectives:</b> This laboratory course enables students to <ul style="list-style-type: none"> <li>• Understand the electronic circuit schematic and working</li> <li>• Realize and test amplifiers and oscillator circuits for the given specifications</li> <li>• Realize and opamp circuits for the applications such as DAC , implement mathematical functions and precision rectifiers.</li> <li>• Study the static characteristics of SCR and test the RC triggering circuits</li> <li>• Design and test the combinational and sequential logic circuits for their functionalities.</li> <li>• Use the suitable ICs based on the specifications and functions.</li> </ul>			
<b>Experiments</b>			
1. Design and set up the BJT common emitter voltage amplifier with and without feedback and determine the gain- bandwidth product, input and output impedances.			
2. Design and set-up BJT/FET: i) Colpitts Oscillator, and ii) Crystal Oscillator iii) RC phase shift oscillator			
3. Design and setup the circuits using opamp: i) Adder , ii) Integrator, iii) Differentiator and iv) Comparator			
4. Obtain the static characteristics of SCR and test SCR controlled HWR and FWR using RC triggering circuits.			
5. Test the precision rectifiers using opamp: i) Half wave rectifier, ii) full wave rectifier			
6. Design and test Monostable and Astable Multivibrator using 555 Timer.			

**Course Outcomes:** On the completion of this laboratory course, the students will be able to:

- Design analog circuits using BJT/FETs and evaluate their performance characteristics.
- Design analog circuits using OPAMPs for different applications
- Simulate and analyze analog circuits that uses ICs for different electronic applications.

**Conduct of Practical Examination:**

- All laboratory experiments are to be included for practical examination.
- Students are allowed to pick one experiment from the lot.
- Strictly follow the instructions as printed on the cover page of answer script for breakup of marks.
- Change of experiment is allowed only once and Marks allotted to the procedure part to be made zero

**Reference Books:**

1. David A Bell, “Fundamentals of Electronic Devices and Circuits Lab Manual, 5th Edition, 2009, Oxford University Press.

**INDEX**

Sl. No:	Name of the Experiment	Page No:
1.	Design and set up the BJT common emitter voltage amplifier with and without feedback and determinethe gain- bandwidth product, input and output impedances.	4-7
2.	Design and set-up BJT/FET: i) Colpitts Oscillator, and ii) Crystal Oscillator iii) RC phase shift oscillator	
3.	Design and setup the circuits using opamp: i) Adder , ii) Integrator, iii) Differentiator and iv) Comparator	
4.	Obtain the static characteristics of SCR and test SCR controlled HWR and FWR using RC triggering circuits.	
5.	Test the precision rectifiers using opamp: i)Half wave rectifier, ii) full wave rectifier	
6.	Design and test Monostable and Astable Multivibrator using 555 Timer.	

**EXPERIMENT: 1****COMMON EMITTER AMPLIFIER**

**Aim:** Design and set up the BJT common emitter amplifier using voltage divider bias with and without feedback and determine the gain- bandwidth product from its frequency response.

**Components required:** Transistor – SL100, Resistors - 470  $\Omega$ , 1K $\Omega$ , 10K $\Omega$  - 2nos, and 33K $\Omega$ , Capacitors 100 $\mu$ f, 0.22 $\mu$ f and 0.47 $\mu$ f, Power Supply, 10Hz – 3MHz Signal generator, CRO, Connecting wires and Bread board/Spring board with spring terminals.

**Theory:**

Common Emitter Amplifier Configuration, the Emitter of a BJT is common to both the input and output signal.

**Design:** Transistor: **SL100**

Let  $V_{CC} = 12V$ ;  $I_C = 4.5 \text{ mA}$ ;  $V_E = 1.2V$ ;  $V_{CE} = 6V$ ;  $h_{FE} = 100$ .

Given  $V_E = 1.2V$ . Therefore  $R_E = V_E / I_E \Omega$   $V_E / I_C = 266.67\Omega$ ;  $R_E = 270\Omega$

Writing KVL for the Collector loop we get,  $V_{CC} = I_C R_C + V_{CE} + V_E$

$R_C = (V_{CC} - V_{CE} - V_E) / I_C = (12 - 6 - 1.2)V / 4mA = 1.06K \Omega$ ;  $R_C = 1 K \Omega$

$h_{FE} R_E = 10R_2$

Assume  $R_2 = 2.7K\Omega$ ,

$V_B = (V_{CC} \times R_2) / (R_1 + R_2)$


Hence  $R_1 = 14.14 K \Omega$ ;  $R_1 = 15 K \Omega$


Use  $C_{C1} = 0.47\mu F$

Use  $C_{C2} = 0.47\mu F$

Use  $C_E = 47\mu F$

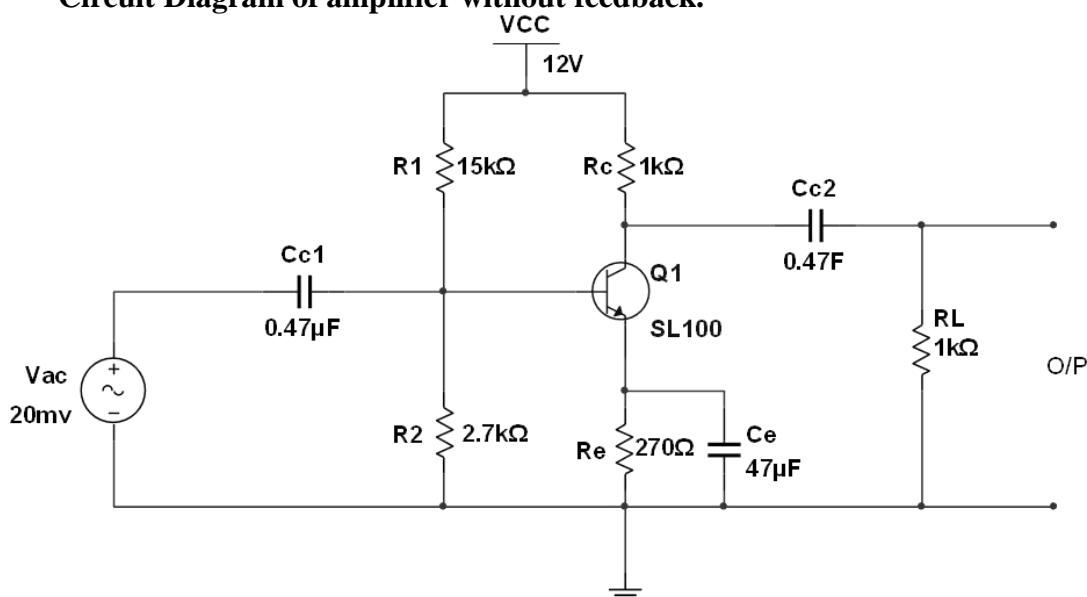**Circuit Diagram of amplifier without feedback.**



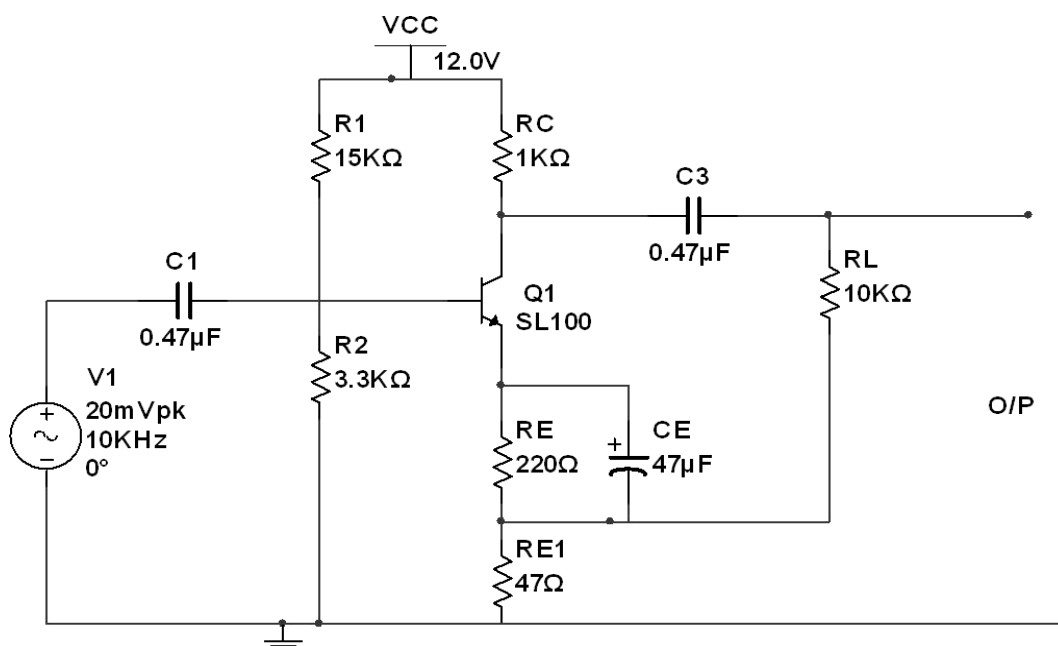**Circuit Diagram of amplifier with feedback.** (Introduce a resistor in the emitter circuit)

**Procedure:** Follow the same procedure for both circuits

After making the connections, switch on the D.C. power supply and check the D.C. conditions without any input signal and record in table below

Parameter	V <sub>RC</sub>	V <sub>CE</sub>	V <sub>E</sub>	I <sub>CQ</sub>	V <sub>BE</sub>
Assumed	4.8V	6 V	1.2V	4.5 mA	0.6 V
Practical					

- Select sine wave input and set the input signal frequency  $\geq 10f_1$  (Say = 10 KHz. This will be a convenient 'Mid – frequency').
- Observe the input wave form and output wave form on a dual channel CRO.
- Adjust the input amplitude such that the output waveform is just undistorted (or in the verge of becoming distorted). Measure the amplitude of the Input Signal now. This amplitude is the Maximum Signal Handling Capacity of your amplifier.
- Decrease the input voltage to a convenient value such that the output is undistorted. Say 20mV. Measure the corresponding o/p voltage. Calculate mid-band gain,  $AM = V_o \text{ (p-p)} / V_{in} \text{ (p-p)}$ .
- Keeping the input voltage constant, go on reducing the frequency until the output voltage reduces to 0.707 times its value at 10 KHz. The frequency at which this happens gives you the Lower Cut-off frequency ( $f_1$ ).
- Keeping the input voltage constant, go on increasing the frequency until the output voltage decreases to 0.707 times its value at 10 KHz. The frequency at which this happens gives you the Upper Cut-off frequency ( $f_2$ ).
- Thus you have pre-determined  $f_1$  and  $f_2$ . Find the amplifier band width,  $BW = f_2 - f_1$
- Determine Gain Bandwidth product (GBW product) which is a Figure of Merit of

your amplifier as  $GBW = AM \times BW$ .

9. Now repeat the experiment by recording values of output voltage versus frequency keeping the input voltage at a constant value convenient to you. You should take at least 5 readings below  $f_1$  and 5 readings above  $f_1$ , at least 5 readings in the mid band, at least 5 readings below  $f_2$  and 5 readings above  $f_2$ .
10. Plot graphs of  $A_V$  versus Frequency,  $f$  and /or  $M$ , dB versus Frequency,  $f$  on a *semi log graph paper*. From the graph determine: Mid –band - gain, Lower and Upper Cut-off frequencies and Band width. Compute the GBW product and verify with answer obtained earlier.

**observation:** Use the tabular column separately for each circuit


$$V_{in(P-P)} = \dots\dots\dots V$$

$$A_V = V_O (P-P) / V_{in} (P-P)$$

$$M = 20 \log (A_V), \text{ dB}$$

Frequency In Hz	100	200	300	350	400	500	600	700	800	1K	2K	3K	5K	8K
$V_O(P-P)$ in Volts														
$A_V$														
M, dB, ( $A_V$ in dB)														
Frequency In Hz	10 K	20K	30K	50 K	100 K	200 K	300 K	400 K	500 K	600 K	700 K	800 K	900 K	1M
$V_O(P-P)$ in Volts														
$A_V$														
M, dB, ( $A_V$ in dB)														

**Expected Graph:**

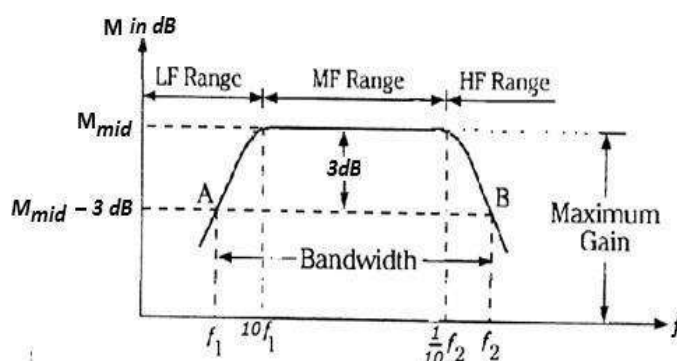

**EXPERIMENT: 2****COLPITTS OSCILLATOR ,CRYSTAL OSCILLATOR and RC PHASE SHIFT OSCILLATOR**

**Aim:** Design and set-up the following oscillators circuits using BJT, and determine the frequency of oscillation.

- i) Colpits Oscillator
- ii) Crystal Oscillator
- iii) RC phase shift oscillators

**Components required:** Transistor SL 100, Resistors 470Ω, 1KΩ 10KΩ and 33 KΩ; Capacitors 0.1μf - 3nos, Discrete inductances 100 μH – 2 nos, Capacitor 470 pF – 2nos, Power supply, CRO, Connecting wires etc.

**Theory:**

**i) Colpits Oscillator:** LC oscillators are generally used as RF oscillators since they generally used to create high frequency oscillations. In Colpitts oscillator an LC tank circuit is used for selection of frequency of oscillation. A voltage divider biased common emitter amplifier is used as amplifier. The amplifier and tank circuit together provides a phase shift of 360 degrees to satisfy Barkhausen criterion.

**Design:**

BJT- Amplifier design is same as given in Common Emitter Amplifier.


**Tank Circuit Design:**  $f = \frac{1}{2\pi\sqrt{LC_{eq}}}$  Where  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$

**Given Oscillation frequency**  $f = 1 \text{ MHz}$

**Assume**  $C_1 = C_2 = 470 \text{ pF}$  ∴  $C_{eq} = 235 \text{ pF} = 2.35 \times 10^{-10} \text{ F}$

**Then,**  $L = \frac{1}{4\pi^2(f^2)C} = 119 \mu\text{H}$

**Use**  $L = 100 \mu\text{H}$ , For this value of L,  $f = 1.04 \text{ MHz}$

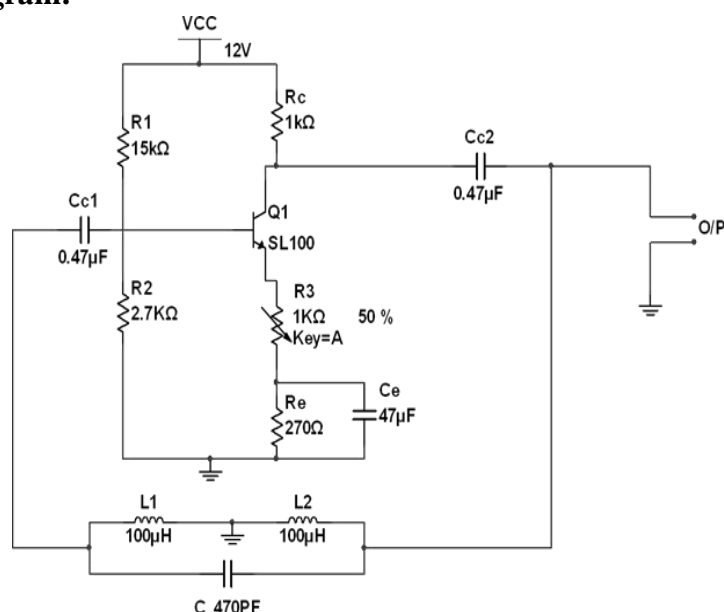**Circuit Diagram:**



**Procedure:**

1. Switch on the Power Supply and check the D.C conditions by removing the coupling capacitor CC1 or CC2.
2. Connect the coupling capacitors and obtain an output waveform on the CRO. If the o/p is distorted adjust 1- K $\Omega$  Potentiometer (R3) to get perfect SINE wave.
3. Measure the period of oscillation and calculate the frequency of oscillation.
4. Compare the measured frequency with re-computed theoretical value for the component values connected.

**Observation**

Parameter	V <sub>RC</sub>	V <sub>CE</sub>	V <sub>E</sub>	I <sub>CQ</sub> = V <sub>RC</sub> / R <sub>C</sub>	V <sub>BE</sub>	V <sub>B</sub>
Assumed	4.8V	6 V	1.2V	4.5 mA	0.6 V	1.8 V
Practical						

**CRYSTAL OSCILLATOR****Theory:**

Crystal oscillators are used in order to get stable sinusoidal signals despite of variations in temperature, humidity, transistor and circuit parameters. A piezo electric crystal is used in this oscillator as resonant tank circuit. Crystal works under the principal of piezo-electric effect. i.e., when an AC signal applied across the crystal, it vibrates at the frequency of the applied voltage. Conversely if the crystal is forced to vibrate it will generate an AC signal. Commonly used crystals are Quartz, Rochelle salt etc.

**Components required:** Transistor SL 100, Crystal – 2MHz, Resistors 470 $\Omega$ , 1K $\Omega$  10K $\Omega$  and 33 K $\Omega$ ; Capacitors 0.1 $\mu$ f - 2nos, Power supply, CRO, Connecting wires etc.

**Design:**

$$\begin{aligned} \text{Let } V_{CC} &= 12\text{V}; I_{CQ} = 4\text{mA}; \\ V_E &= (1/10) V_{CC} \text{ to } (1/5) V_{CC}; \\ V_{CE} &= \underline{6\text{V}}; \end{aligned}$$

$$h_{FE} = 100.$$

To find R<sub>E</sub>: Let us choose V<sub>E</sub> = 2 V

$$\begin{aligned} R_E &= V_E / I_E \approx V_E / I_C = 2\text{ V} / 4\text{ mA} = 500\ \Omega; \text{ let } \quad \mathbf{R_E = 470\ \Omega} \\ V_{CC} &= I_C R_C + V_{CEQ} + V_{EQ} \\ R_C &= (V_{CC} - V_{CEQ} - V_{EQ}) / I_{CQ} = 4.0\text{ V} / 4\text{mA} = 1.0\text{K}\ \Omega; \quad \mathbf{R_C = 1K\ \Omega} \end{aligned}$$

Assume **R2=10kΩ**.

$$V_B = V_E + V_{BE} = 2 + 0.6 = 2.6V$$

$$I_2 = \text{Current through } R_2 = V_B / R_2 = 0.26mA \text{ or } 260\mu A$$

$$\text{The base current } I_B = I_C / h_{FE} = 4mA / 100 = 0.04mA = 40\mu A$$

$$(h_{FE} = \beta_{DC} = 100, \text{ a working value; It varies from 50 to 280 for SL 100}) I_1 =$$

$$\text{Current through } R_1 = I_B + I_2 = 300 \mu A$$


$$V_{R1} = V_{CC} - V_B = 12 - 2.6 = 9.4V$$

$$R_1 = V_{R1} / I_1 = 9.4V / 300 \mu A = 9400 / 300 K\Omega = 31.33K\Omega \quad R_1 = 33K \Omega$$

$$C_E = C_C = 0.1\mu F \text{ (Arbitrary, any value which gives a reactance } < 10 \Omega \text{ at}$$

$$\text{Crystal frequency may be used. reactance of a Capacitor } X_C = (1/2\pi fC); \text{ For } C = 0.1 \mu F, X_C = 0.8\Omega \text{ at } 2 \text{ MHz})$$

### Circuit Diagram

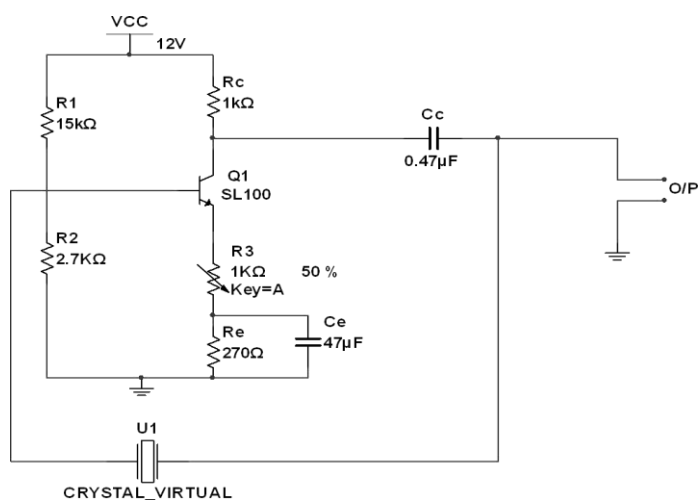

### Procedure:

1. Switch on the Power Supply and before inserting the crystal check the D.C conditions by removing the coupling capacitor CC1 or CC2.
2. Insert the crystal and the coupling capacitors and obtain the output waveform on the CRO. If the o/p is distorted vary 1- KΩ Potentiometer (R3) to get perfect SINE wave.
3. Measure the period of oscillation and calculate the frequency of oscillation.
4. Compare with frequency marked on the crystal

### Observation:

Parameter	VRC	VCE	VE	ICQ = VRC / RC	VBE	VB
Assumed	4.8V	6 V	1.2V	4.5 mA	0.6 V	1.8 V
Practical						

## RC PHASE SHIFT OSCILLATOR

### Theory

A **Phase Shift Oscillator** is an electronic oscillator circuit which produces sine wave output. It can either be designed by using transistor or by using an Op-amp as inverting amplifier. Generally, these phase shift oscillators are used as audio oscillators. In RC phase shift oscillator, 180 degree phase shift is generated by the RC network and another 180 degree is generated by the Op-amp, so the resulting wave is inverted by 360 degree.

Apart from generating the sine wave output they are also used to provide significant control over the phase shifting process

### Circuit diagram

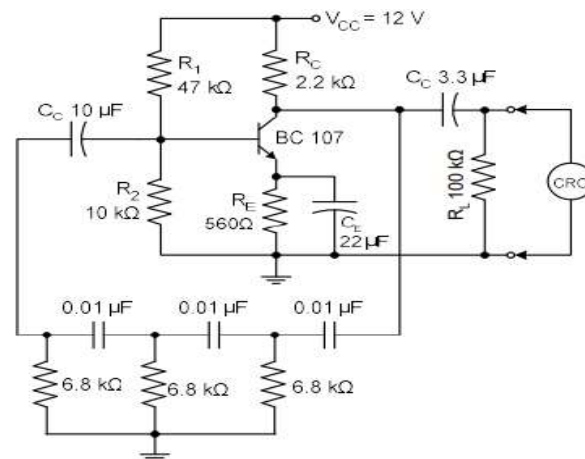


Fig1 g. Circuit Diagram of RC Phase shift Oscillator

### DESIGN

From the transistor data sheet, for BC107,

$$h_{FE} = \beta = 110, I_{C \text{ max}} = 100 \text{ mA}, V_{CE \text{ max}} = 45 \text{ V}$$

Let  $V_{CC} = 12 \text{ V}$ ,  $I_C = 2 \text{ mA}$ . Since the quiescent point is in the middle of the load line for the amplifier,  $V_{CE} = 50\% \text{ of } V_{CC} = 6 \text{ V}$ .

$$V_{RE} = 10\% \text{ of } V_{CC} = 1.2 \text{ V}$$

Assuming  $I_C = I_E$ ,  $V_{RE} = I_C R_E = I_E R_E$

$$1.2 = 2 \times 10^{-3} \times R_E$$

$$R_E = \frac{1.2}{2 \times 10^{-3}} = 600 \Omega \quad \text{Select standard value of resistance } 560 \Omega$$

$$\begin{aligned} \text{Voltage across collector resistance, } V_{RC} &= V_{CC} - V_{CE} - V_{RE} \\ &= 12 - 6 - 1.2 = 4.8 \text{ V} \end{aligned}$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{4.8}{2 \times 10^{-3}} = 2.4 \text{ k}\Omega \quad \text{Select standard value of } 2.2 \text{ k}\Omega$$

$$\text{Base current, } I_B = \frac{I_C}{\beta} = \frac{2 \times 10^{-3}}{110} = 18.2 \mu\text{A}$$

$$\text{Take } I_2 = I_B \quad \text{then } I_1 = 10I_B + I_B = 11I_B$$

$$\text{Base voltage, } V_B = V_{RE} + V_{CE} = 1.2 + 0.6 = 1.8 \text{ V}$$

$$R_2 = \frac{V_B}{I_2} = \frac{1.8}{10 \times 18.2 \times 10^{-6}} = 9.9 \text{ k}\Omega \quad \text{Select standard value of } 10 \text{ k}\Omega$$

$$R_1 = \frac{V_{CC} - V_B}{I_1} = \frac{12 - 1.8}{11 \times 18.2 \times 10^{-6}} = 51 \text{ k}\Omega \quad \text{Select standard value of } 47 \text{ k}\Omega$$

### Design of coupling capacitors $C_{C1}$ and $C_{C2}$

$X_{C1}$  should be less than the input impedance of the transistor. Here,  $R_{in}$  is the series impedance.

$$\text{Then } X_{C1} \leq \frac{R_{in}}{10}$$

$$\text{Here } R_{in} = R_1 \parallel R_2 \parallel h_{FE} r_E = 47 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 110 \times 12.5 \Omega = 1.17 \text{ k}\Omega$$

$$\text{We get } R_{in} = 1.17 \text{ k}\Omega. \quad \text{Then } X_{C1} \leq 117 \Omega$$

$$\text{For a lower cut off frequency of } 200 \text{ Hz, } C_{C1} = \frac{1}{2\pi f X_{C1}} = \frac{1}{2\pi \times 200 \times 117} = 6.8 \mu\text{F}$$

Select standard value of  $10 \mu\text{F}$  for  $C_{C1}$

$$\text{Similarly, } X_{C2} \leq \frac{R_{out}}{10} \quad \text{where } R_{out} = R_C. \quad \text{Then } X_{C2} \leq 220 \Omega$$

$$\text{So, } C_{C2} = \frac{1}{2\pi f X_{C2}} = \frac{1}{2\pi \times 200 \times 220} = 3.6 \mu\text{F}$$

Select standard value of  $3.3 \mu\text{F}$  for  $C_{C2}$

### Design of bypass capacitors $C_E$

To bypass the lowest frequency (say  $200 \text{ Hz}$ ),  $X_{CE}$  should be much less than or equal to the resistance  $R_E$ .

$$X_{CE} \leq \frac{R_E}{10}$$

$$X_{CE} \leq \frac{560}{10} \quad \text{ie. } X_{CE} \leq 56$$

Apply value of  $f$  such that the amplifier has good gain at a lower cutoff frequency of  $200 \text{ Hz}$

$$C_E \geq \frac{1}{2\pi f X_{CE}} = \frac{1}{2\pi \times 200 \times 56} = 14.2 \mu\text{F}$$

Select standard value of  $22 \mu\text{F}$  for  $C_E$

### Design of Feedback network

The circuit consists of an amplifier stage and a feedback network to provide an additional  $180^\circ$  phase shift, approximately depending upon the frequency of operation. The RC phase shift network must provide  $180^\circ$  or an average of  $60^\circ$  phase shift/lag of RC network

$$\text{RC phase shift factor, } k = V_S/V_O$$

For one stage of RC network

$$V_o = I R \quad V_C = I X_C$$

$$\tan \Phi = \frac{V_C}{V_o} = \frac{I X_C}{I R} = \frac{1}{(2\pi f C) R}$$

$$f = \frac{1}{2\pi R C \tan \Phi}$$

If these are three sections, each must give, approximately  $\Phi = 60^\circ$  then  $\tan 60 = \sqrt{3}$

$$f = \frac{1}{2\pi R C \sqrt{3}}$$

This gives the approximate frequency of oscillation of a phase shift with three RC sections.

In the above phase relationship, between voltage and current in the RC network, the additional current  $I$  that flow through  $C$  for the other sections so that  $V_C$  is larger than the value indicated which means that  $f$  is smaller than the value obtained in the above equation. A transfer function analysis of the three-stage network would give a more accurate expression for frequency of oscillation as below.

$$f = \frac{1}{2\pi R C \sqrt{6}}$$

Assume  $f = 1000$  Hz and  $C = 0.01 \mu\text{F}$

$$1000 = \frac{1}{2\pi R \times 0.1 \times 10^{-6} \times \sqrt{6}}$$

$$R = \frac{1}{2\pi \times 1000 \times 0.01 \times 10^{-6} \times \sqrt{6}} = 6.5 \text{ k}\Omega$$

Select nearest standard value of 6.8 k $\Omega$  for  $R$

The three-stage feedback network would have an attenuation of  $\left(\frac{1}{29}\right)$  and to satisfy the Barkhausen criterion for oscillation, the amplifier should have a gain of 29 or more. If the gain is just above 29, a pure sine wave will be generated. If the gain is too high, there may be distortions in the output waveform. The circuit in figure 1 is having gain of more than 29 by default. A quick method to adjust the voltage gain is to adjust the load resistance  $R_L$ .

### Procedure:

1. Switch on the Power Supply and check the D.C conditions by removing the coupling capacitor CC1 or CC2.
2. Connect the coupling capacitors and obtain an output waveform on the CRO. If the o/p is distorted adjust 1- K $\Omega$  Potentiometer (R3) to get perfect SINE wave.
3. Measure the period of oscillation and calculate the frequency of oscillation.
4. Compare the measured frequency with re-computed theoretical value for the component values connected.

### Observation

Parameter	VRC	VCE	VE	ICQ = VRC / RC	VBE	VB
Assumed	4.8V	6 V	1.2V	4.5 mA	0.6 V	1.8 V
Practical						


**Result:** The frequency of

- i. Colpits Oscillator is.....
- ii. Crystal Oscillator is.....
- iii. RC phase shift oscillators is .....

**EXPERIMENT: 3****OPAMP AS AN ADDER, INTEGRATOR, DIFFERENTIATOR and COMPARATOR**

**Aim:** To Design Adder, Integrator , Differentiator and comparator circuits using Op-Amp

**Components:** Op-Amp  $\mu A 741$ , Resistors, Capacitor, Signal Generator, CRO, Fixed Power supply +12V,0,-12V.

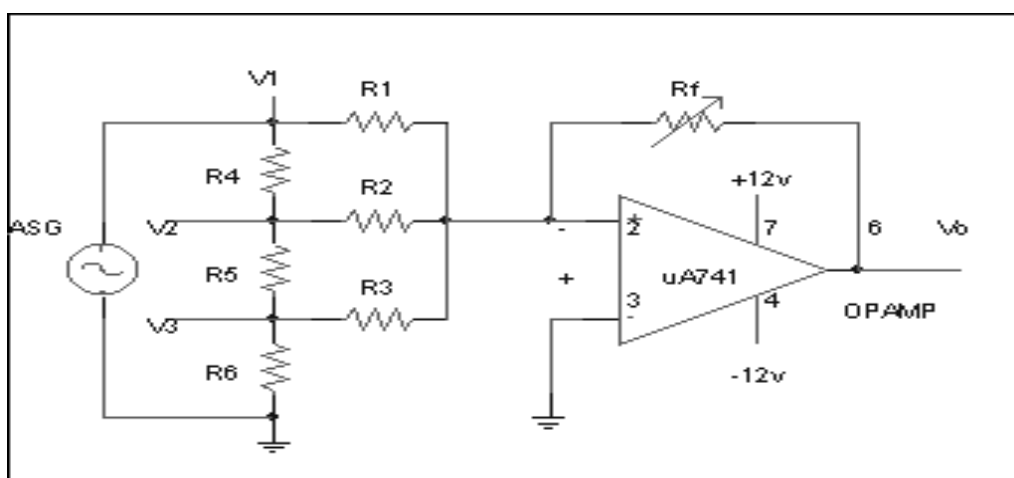**A. Op-Amps as summer( Inverting)****Circuit Diagram:****Design :**

Design a summing amplifier to obtain a output of  $-6V$ . Since inputs are given to Inverting terminal, output is given by,

$$V_{out} = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$

Now,


$$\frac{R_f}{R_1} = \frac{R_f}{R_2} = \frac{R_f}{R_3} = \frac{1k\Omega}{3k\Omega} = \frac{1}{3}$$


$$V_{out} = -\left(\frac{V_1 + V_2 + V_3}{3}\right)$$

**Procedure :**

1. Connections are made as shown in the circuit diagram.

2. With the chosen values of  $R_f$ ,  $R_i$ , and  $R_3$ , provide DC voltages  $V_1$ ,  $V_2$ , and  $V_3$  from VRPS.
3. Measure the output voltage and compare it with the designed value.
4. Repeat the above procedure providing AC sinusoidal signal of frequency 1KHz for  $V_1$ ,  $V_2$  and  $V_3$  and observe the output waveform.

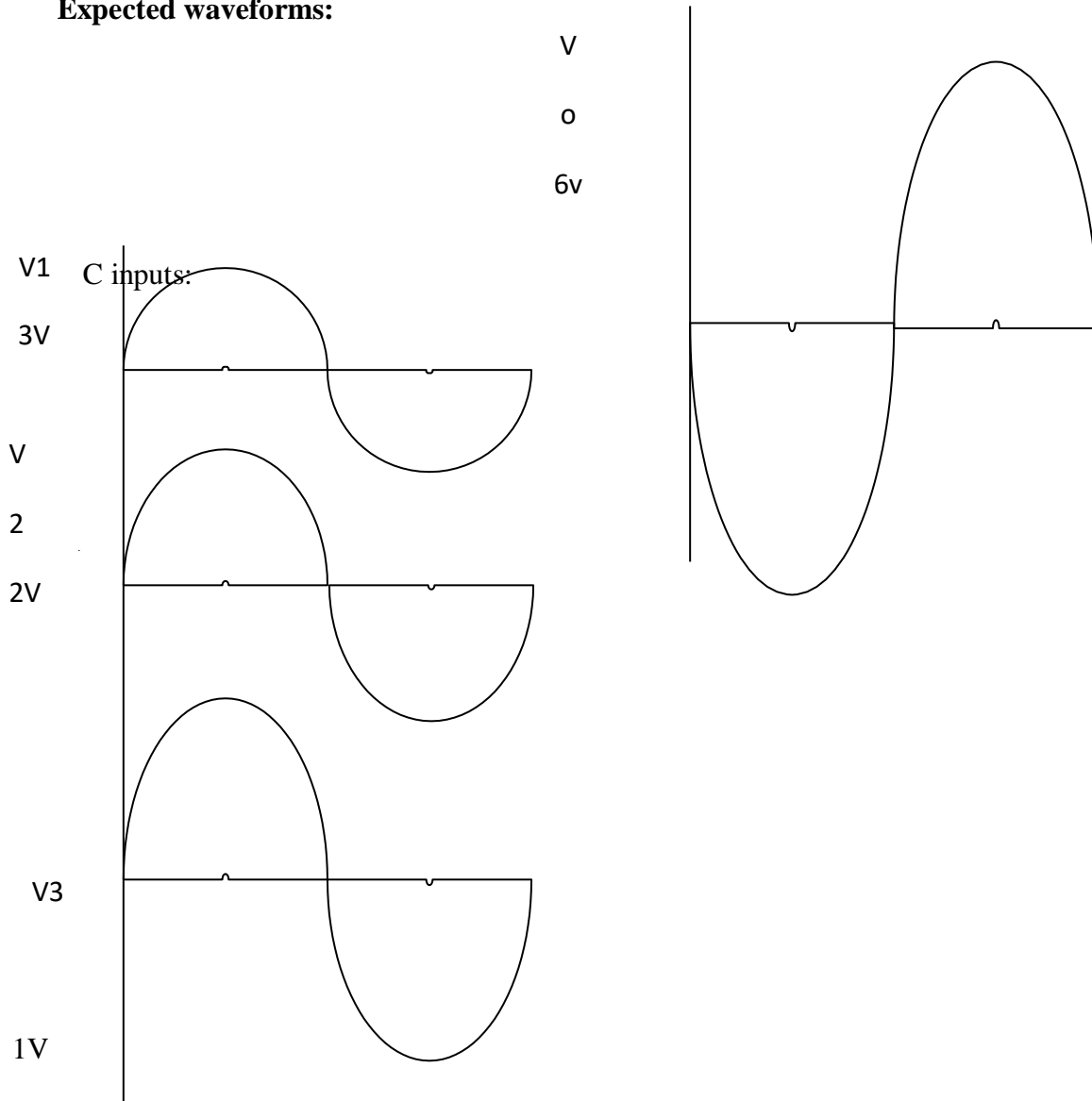**Expected waveforms:**

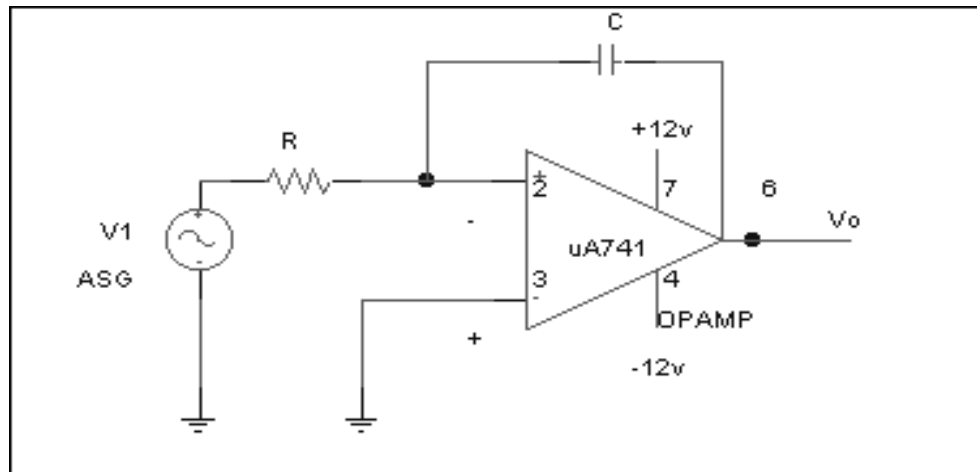**B. Op-amp as an integrator:****Circuit Diagram:****Design :**

Design a integrator circuit for different values of R and C. Since input is given to Inverting terminal, the output of integrator is given by

$$V_o = -\frac{1}{RC} \int V_i dt$$

**Note:** Requirement for integration is  $RC \gg T$ , where T is the time period of input signal.

Consider input square wave of frequency 1 KHz

$$\therefore T = \frac{1}{f} = 1 \text{ ms}$$

Since  $RC \gg T$ , let  $RC = 10 T = 10\text{ms}$



$$\text{For } C = 0.1 \mu\text{f}, R = \frac{10 \times 10^{-3}}{0.1 \times 10^{-6}} = 100\text{K}\Omega$$

Choose,  $R = 100\text{K}\Omega$  and  $C = 0.1 \mu\text{f}$

**Procedure:**

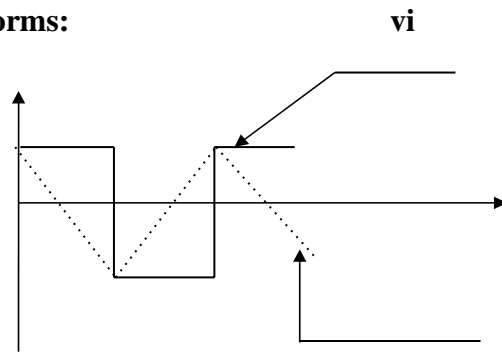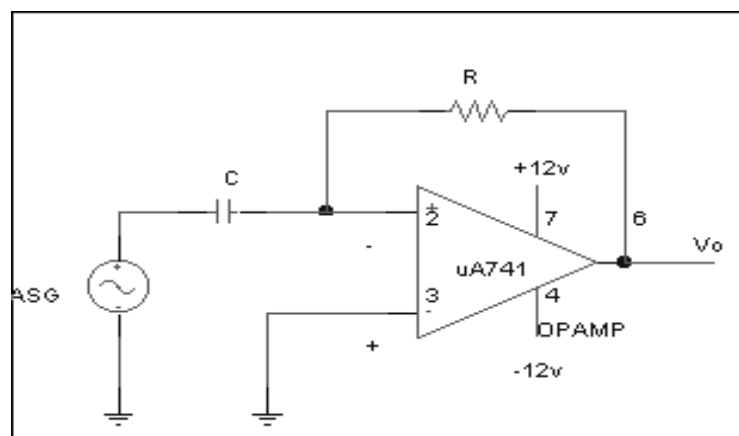1. Connections are made as shown in the circuit diagram.
2. The input square wave signal ( $V_i$ ) is set to 4V(p-p) of 1KHz frequency.
3. For the chosen values of R and C, Observe the output Waveform ( $V_o$ ) on the CRO and verify it with the expected waveforms.
4. Repeat the experiment for different values of R and C ( $RC = 10T$ ,  $RC = T$ ,  $RC=0.1T$ ).



**Expected waveforms:****C. Op-amp as a differentiator:****Circuit Diagram:****Design :**

Design a differentiator circuit for different values of R and C. Since input is given to inverting terminal, the output of differentiator is given by

$$V_o = - \frac{dV_i}{RC dt}$$

Note: Requirement for integration is  $RC \ll T$ , where T is the time period of input signal.

Consider input square wave of frequency 1 KHz

$$T = \frac{1}{f} = 1 \text{ ms}$$

$$\text{Since } RC \ll T, \text{ let } RC = \frac{1}{10} T = 0.1 T$$


for  $C = 0.1 \mu\text{f}$

$$\therefore R = \frac{0.1 \times 10^{-3}}{0.1 \times 10^{-6}} = 1 \text{ K}\Omega$$

Choose,  $R = 1 \text{ K}\Omega$  and  $C = 0.1 \mu\text{f}$


**Procedure :**

1. Connections are made as shown in the circuit diagram.
2. The input square wave signal ( $V_i$ ) is set to 4V(p-p) of 1KHz frequency.
3. For the chosen values of R and C, Observe the output Waveform ( $V_o$ ) on the CRO and verify it with the expected waveforms.
4. Repeat the experiment for triangular waveform.
5. Repeat the experiment for different values of R and C ( $RC = 10T$ ,  $RC = T$ ,  $RC=0.1T$ ).

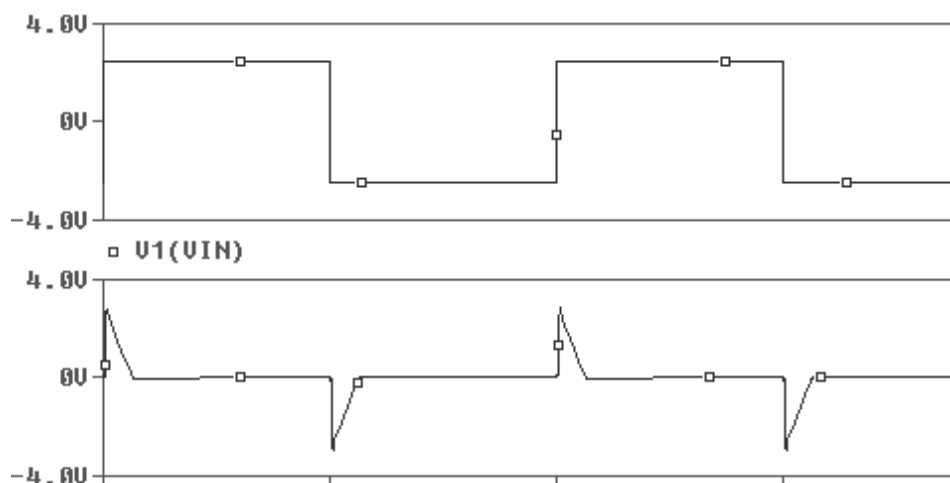**Expected waveforms:**

**Comparator** A voltage comparator is a two-input circuit that compares the voltage at one input to the voltage at the other input. Usually one input is a reference voltage and the other input a time varying signal. If the time varying input is below or above the reference voltage, then the comparator provides a low or high output accordingly (usually the plus or minus power supply voltages, since the op-amp is used in the open loop configuration, a small difference ( $-$ ) makes the output to saturate). For the comparator circuit shown in Figure 1, the output will be at its negative saturation value when the input is greater than the reference and at its positive saturation value when the input is less than the reference. If  $V_r$  is zero, the comparator can be used as a zero-crossing detector. If  $V_r$  is not zero, the comparator can be referred to as a level detector. One problem encountered with the simple comparator is the instability of its output resulting from noise when the input is in the neighborhood of  $V_r$ .
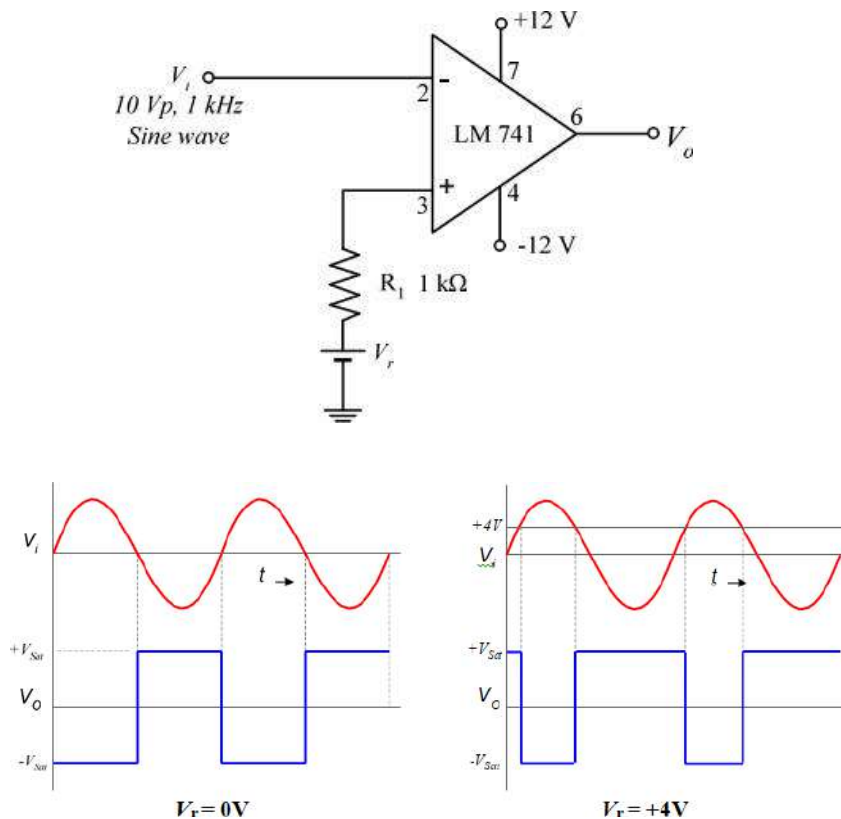
### Circuit Diagram and waveforms of Comparator



#### Procedure

1. Set up circuit as shown in the connection diagram
2. Set the input voltage 20 V peak to peak, 1 kHz in function generator, and apply input signal to the circuit.
3. Observe the output waveform in CRO.
4. Obtain the response for different  $V_r$  (for comparator circuit only).

#### Result

Adder, integrator, differentiator and Comparator circuits were designed and set up. And the output waveform is observed on CRO

**EXPERIMENT: 4****SCR controlled HWR and FWR using RC Triggering circuit**


**AIM:** To study the performance and waveforms of HWR & FWR by using RC triggering circuit


**APPARATUS:**

SL No	Components	Range	Quality
1	DC Power Supply	0-30V	2
2	Resistor	100Ω	1
3	Transformer	230V, 50Hz	1
4	SCR Diode	TY604 BY127	1
5	DC voltmeter	(0-20)V	1
6	DC ammeter	(0-200)mA (0-200)μA	1
7	Connecting wires		



**CIRCUIT DIAGRAM:**

Half wave rectifier:


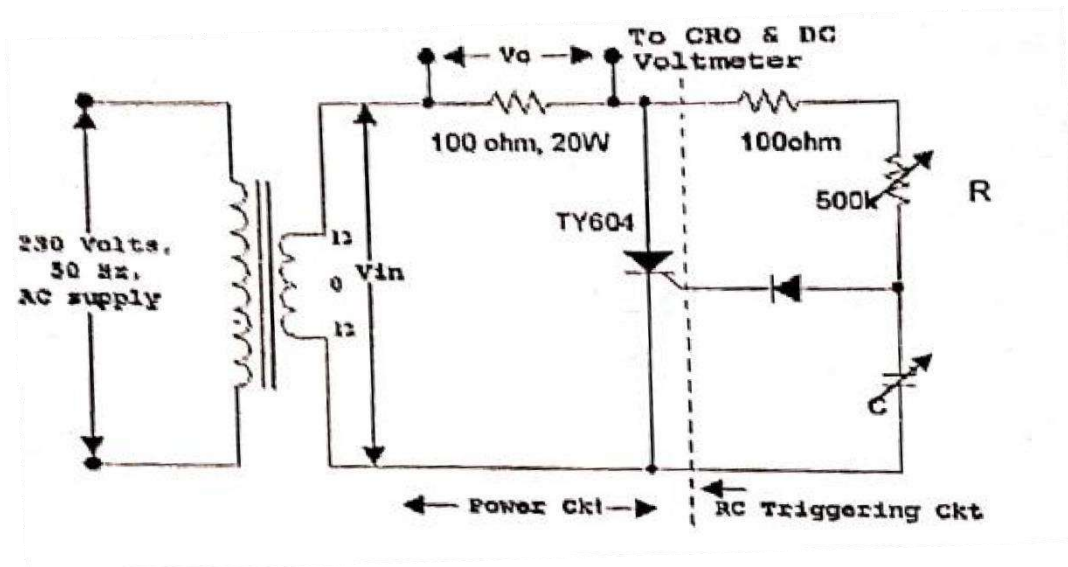


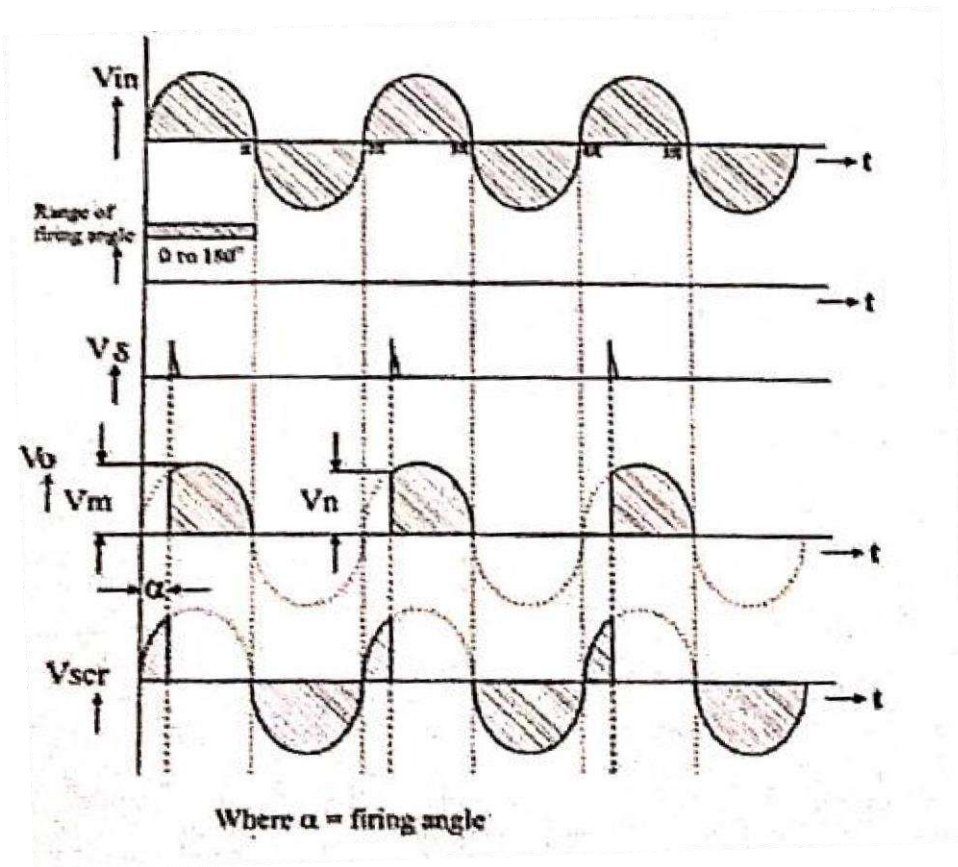**Waveforms:**

Graph:

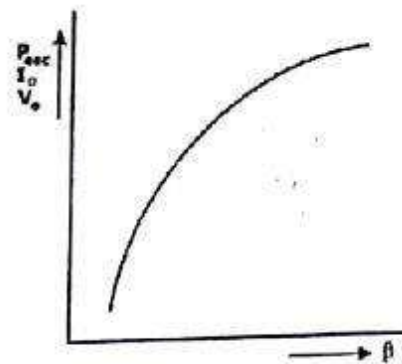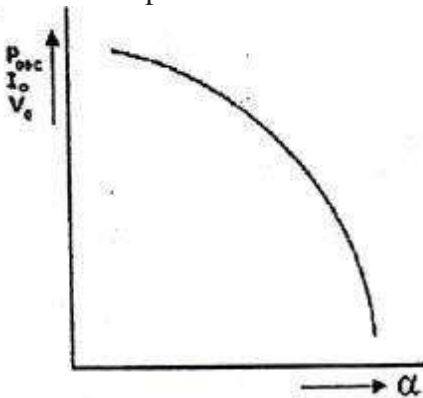

### Full wave rectifier:

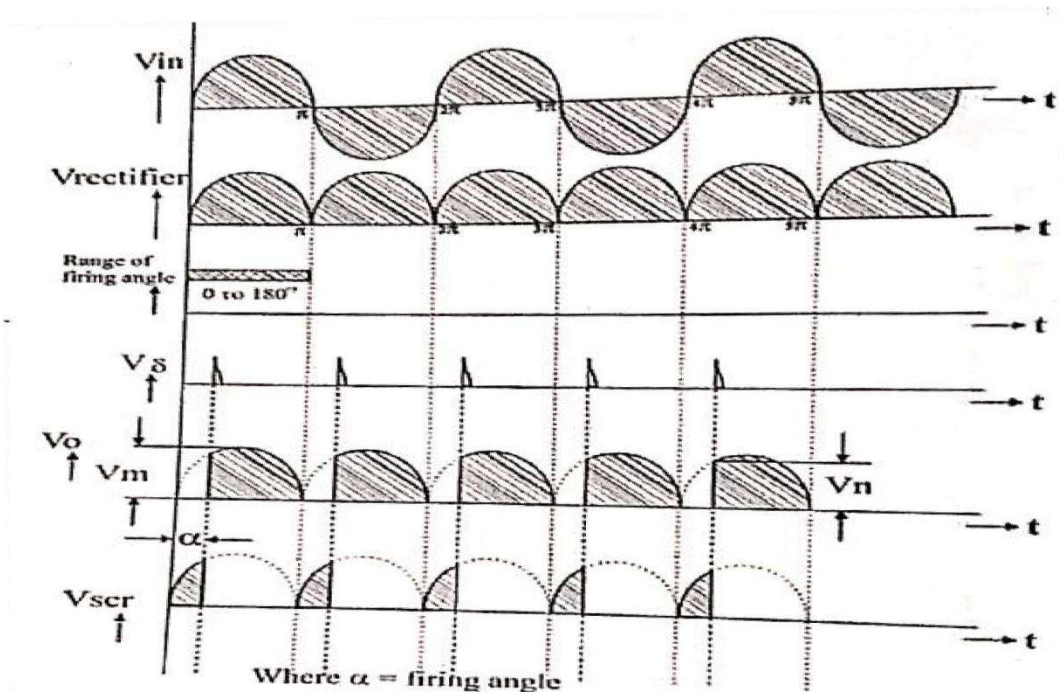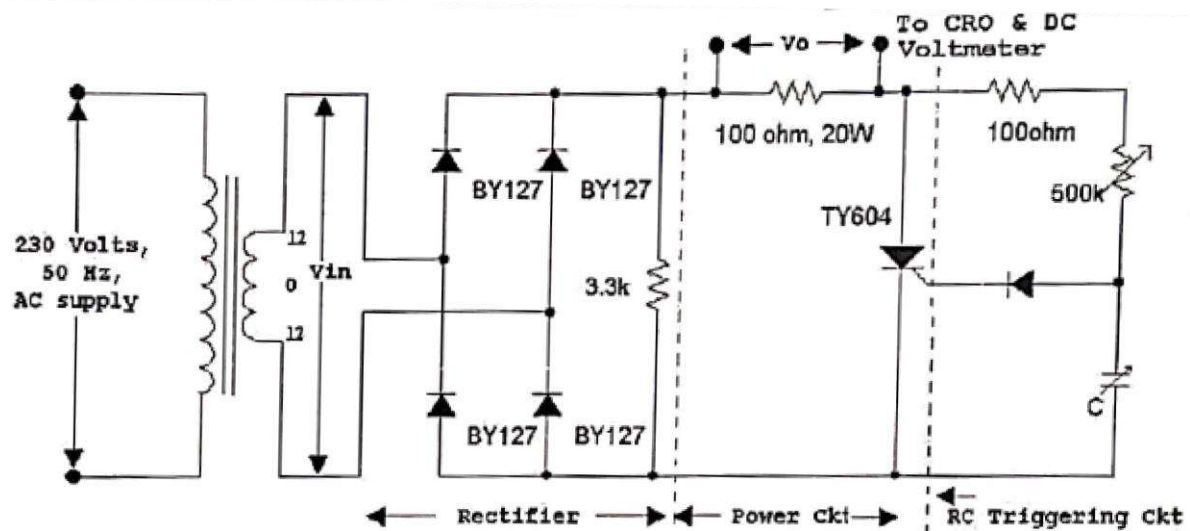

**PROCEDURE:****Half wave rectifier:**

1. Connections are made as shown in the circuit diagram.
2. By varying a resistance R gradually step by step, note down the corresponding values of  $V_n$  &  $V_m$  from CRO and  $V_{o\ dc}$  from the DC voltmeter. The readings are tabulated in the tabular column.
3. If the firing angle ranges from 0 to  $90^\circ$ , then the firing angle  $\alpha$  is calculated by using a formula  $\alpha = \sin^{-1}(V_n/V_m)$  in degrees.
4. The conduction angle  $\beta$  is calculated by using a formula,  $\beta = 180 - \alpha$ .
5. The current and power is calculated by  
 $I_{o\ dc} = (V_{o\ dc}/R)$  in A &  $P_{o\ dc} = V_{o\ dc}^2/R$  in watts respectively.
6. A graph of  $V_o$  v/s  $\alpha$ ,  $V_o$  v/s  $\beta$ ,  $I_o$  v/s  $\alpha$ ,  $I_o$  v/s  $\beta$ ,  $P_{o\ dc}$  v/s  $\alpha$ ,  $P_{o\ dc}$  v/s  $\beta$  to be plotted.
7. Compare practical output voltage with theoretical output voltage,  
 $V_{oth} = V_m(1 + \cos \alpha)/2\pi$  volts where  $V_m = \sqrt{2}V_{rms}$

**Full wave rectifier:**

1. Repeat the above said procedure for full wave rectifier.  
 $V_{oth} = V_m(1 + \cos \alpha)/\pi$  volts where  $V_m = \sqrt{2}V_{rms}$

**TABULAR COLUMN:****Half wave rectifier**

SL No	$V_n$	$V_m$	$\alpha < 90$ degree	$\alpha > 90$ degree	$V_{odc}$	$V_{oth}$
			$\alpha = \sin^{-1}(V_n/V_m)$	$\alpha = 180 - \sin^{-1}(V_n/V_m)$		

**Full wave rectifier**

SL No	$V_n$	$V_m$	$\alpha < 90$ degree	$\alpha > 90$ degree	$V_{odc}$	$V_{oth}$
			$\alpha = \sin^{-1}(V_n/V_m)$	$\alpha = 180 - \sin^{-1}(V_n/V_m)$		

**Result:**

The performance and waveforms of HWR & FWR by using RC triggering circuit is verified


**EXPERIMENT 5****MONOSTABLE AND ASTABLE MULTIVIBRATOR USING 555 TIMER**

**Aim:** To Design of Monostable and Astable Multivibrator using 555 Timer

**Components required:** 555 Timer, Resistor, Capacitor, Power supply +5V, 0, CRO.

**a) Astable Multivibrator (free running oscillator ):**

**Circuit:**

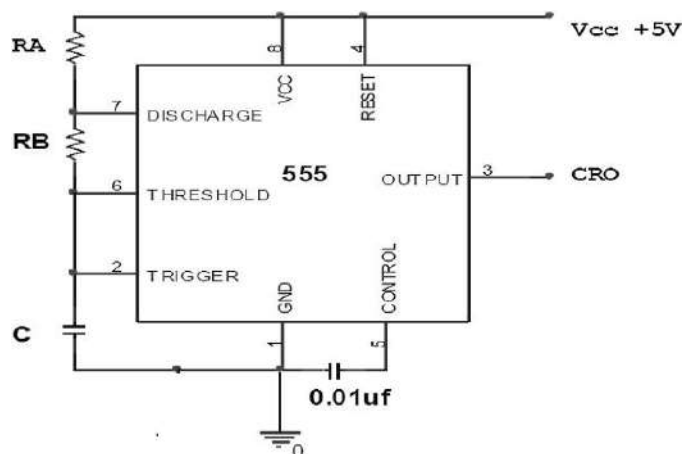

**Design:**

Output time period of oscillations =  $T = T_{on} + T_{off}$

Charging time  $T_{on} = 0.693 (R_A + R_B) C_1$

Discharge time  $T_{off} = 0.693 R_B \cdot C_1$

Duty cycle  $D = \frac{T_{on}}{T_{on} + T_{off}} = \frac{T_{on}}{T} = 0.75$

Let  $T = \frac{1}{f} = 1 \text{ msce},$

**$T_{off} = 0.693 R_B \cdot C_1$**

$0.25 \times 10^{-3} = 0.693 R_B \times 0.1 \times 10^{-6}$

$R_B = 3.6 \text{ K}\Omega$  choose as  **$3.3 \text{ K}\Omega$**

**$T_{on} = 0.693 (R_A + R_B) C_1$**

$0.75 \times 10^{-3} = 0.693 (R_A + 3.3 \text{ K}) \times 0.1 \times 10^{-6}$

**$R_A = 7.2 \text{ K}\Omega$  choose as  $6.8 \text{ K}\Omega$**




Here  $V_{LT}$  = Lower threshold voltage =  $V_{cc}/3 = 1.66V$

$$V_{UT} = \text{Upper threshold voltage} = \frac{2}{3} V_{cc} = \frac{2}{3} \times 5 = 3.33V$$

### Procedure:

1. Connections are made as shown in the circuit diagram
2. Switch on the DC power supply unit
3. Observe the wave form on CRO at pin 3 and measure the o/p pulse amplitude and also measure  $T_{on}$  &  $T_{off}$ .
4. Observe the waveforms across C1 ( $V_c$ ) & measure the max & min voltage levels & verify  $V_{UT}$  &  $V_{LT}$ .
5. Compare the capacitor voltage  $V_c$  with the output waveform  $V_o$  & note that capacitor charges &  $V_c$  rises exponentially when output is high, the capacitor C1 discharges through  $R_B$  & the discharge transistor &  $V_c$  falls exponentially when output is low.
6. Calculate the duty cycle & the output frequency  $f$  & verify with the designed values.

### Waveform:

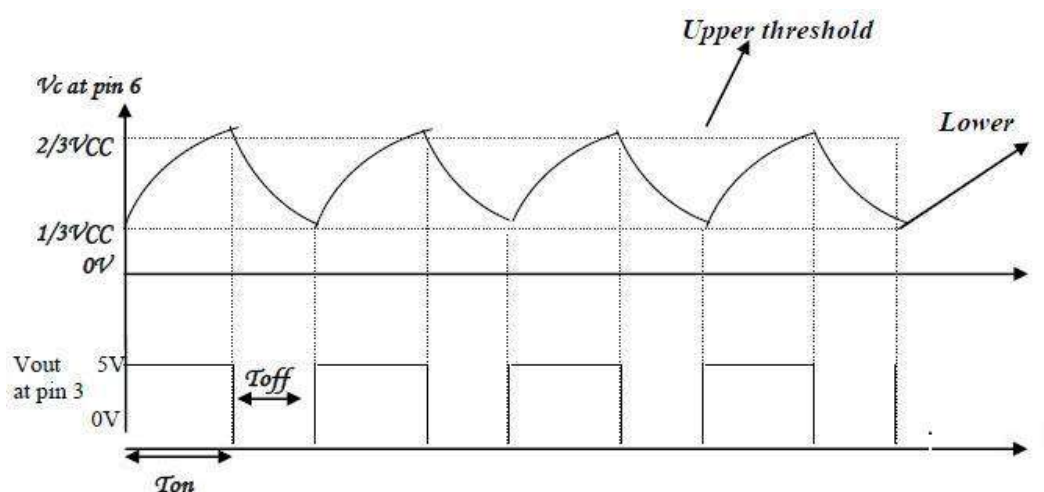


### Tabular Column:

Parameters	Theoretical	Practical
Frequency		
Duty cycle		
$T_{on}$		
$T_{off}$		
$V_{LT} = V_{cc}/3$		
$V_{UT} = \frac{2}{3} V_{cc}$		

**b) Monostable Multivibrator circuit Using 555 Timer.**

**Components required:** Op-Amp  $\mu A$  741, Capacitor, Function Generator , Fixed Powersupply +12V,0,-12V, CRO.

**Circuit:**

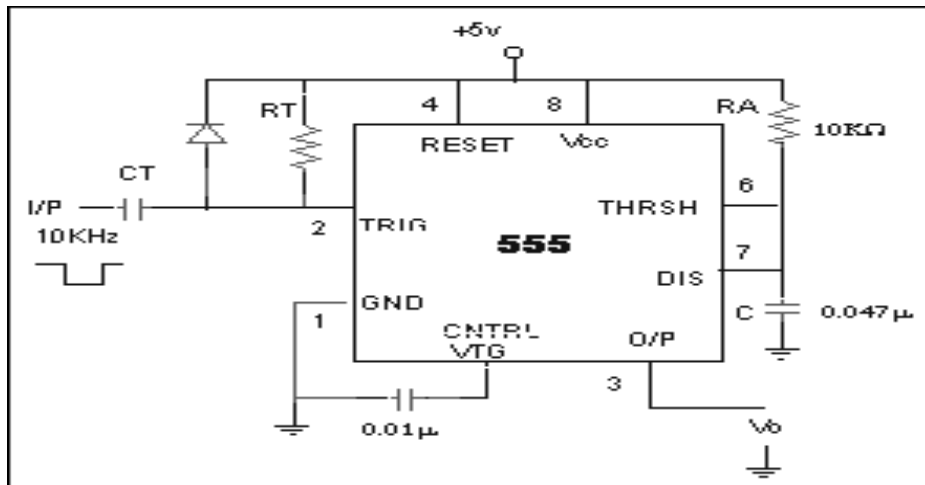

**Design:**

Let output pulse width = Delay time  $t_d$  0.5 msec

Output delay time  $T_d = 1.1 R_A C$


Let  $R_A = 10 \text{ K}\Omega$

$$\therefore C = \frac{T_d}{1.1 R_A} = \frac{0.5 \times 10^{-3}}{1.1 \times 10 \times 10^3}$$

$$= 0.045 \mu\text{F}$$

Choose  $C = 0.047 \mu\text{F}$

Here  $V_{UT}$  = Upper threshold voltage =  $\frac{2}{3} V_{CC}$

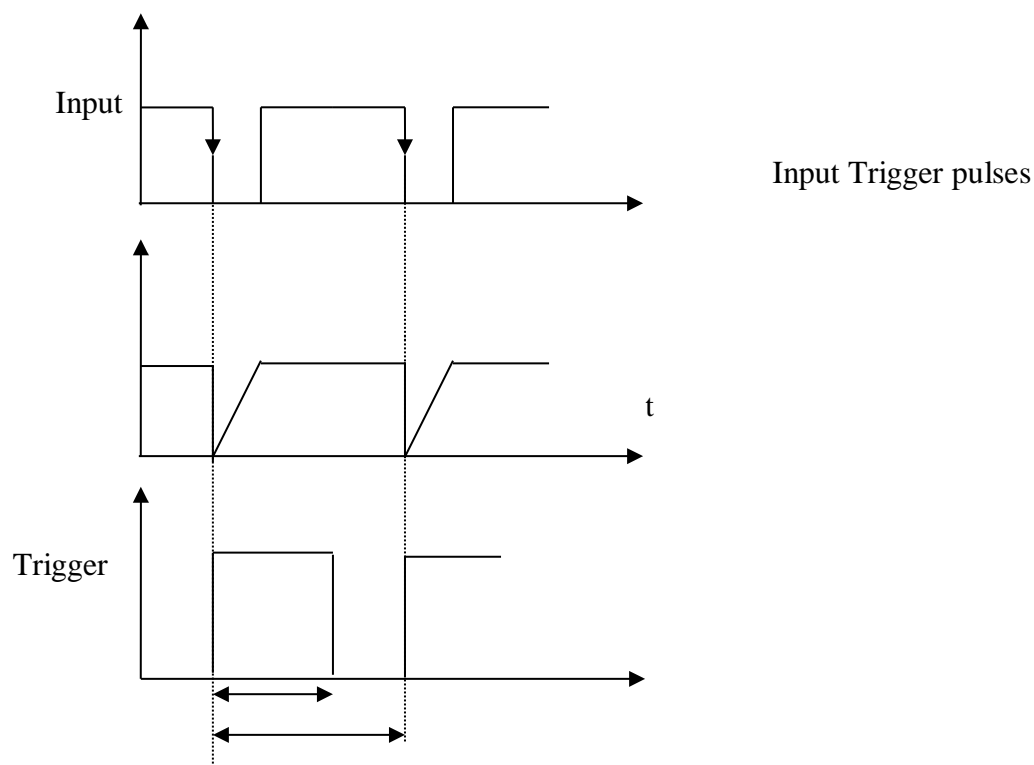**Waveforms:****Procedure:**

1. Connections are made as shown in Figure
2. Switch on the power supply and observe the output waveforms on CRO at pin no 3 and measure the output delay time  $T_d$  and verify with the designed values and also observe the waveforms at pin no 2 – trigger input terminal & at pin no 7, also measure the voltage levels.

**Result:**

Output delay time of monostable and astable vibrators are verified.

## EXPERIMENT 6

### PRECISION HALF WAVE AND FULL WAVE RECTIFIER

**AIM:** To verify precision half wave and full wave rectified using opamp .

#### THEORY:


**Precision Rectifier:** Rectifiers are often called into action to measure signal strength. Rectify an AC signal, pass it through a low-pass filter and the resulting DC level represents some measure of the signal's magnitude. Although the series diode is the classic rectifier, it can't rectify signals smaller than its own forward voltage! But what if your expected amplitude can be as low as 100 mV? Op amps to the rescue! The advantage of op amp circuits lies in their ability to compensate for non-linear devices in the feedback loop. Combining the rectifying action of a diode with the accuracy of an op amp, this circuit creates a precision rectifier.


**Precision Half wave rectifier:** A half wave precision rectifier is implemented using an op amp, and includes the diode in the feedback loop. This effectively cancels the forward voltage drop of the diode, so very low level signals (well below the diode's forward voltage) can still be rectified with minimal error.

**Precision Full Wave Rectifier circuits** accept an ac signal at the input, invert either the negative or the positive half, and delivers both the inverted and noninverted halves at the output, as shown in the Fig




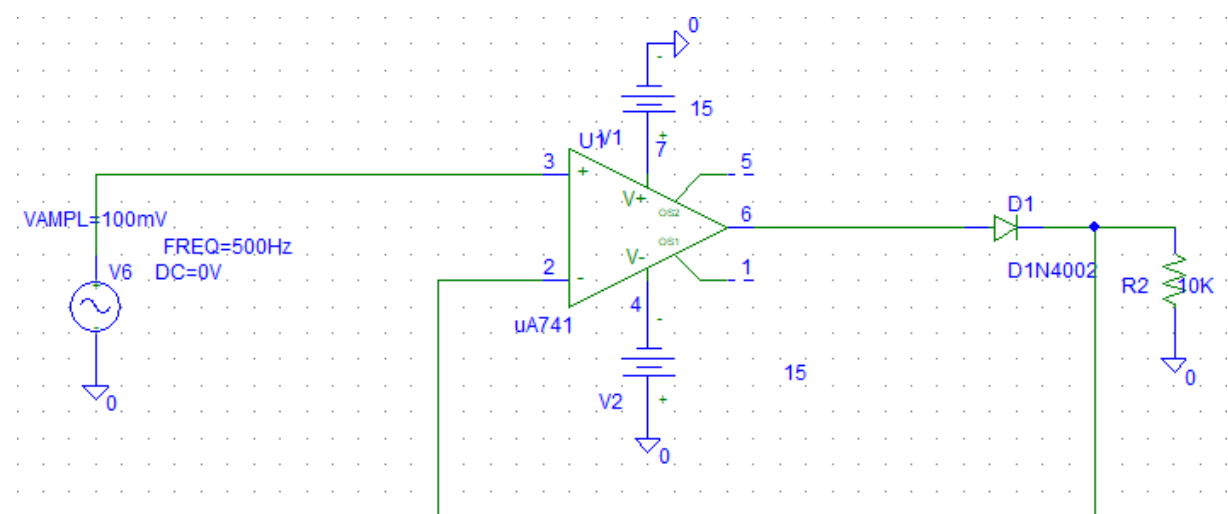
#### SIMULATION CIRCUIT DIAGRAM (Precision HWR)



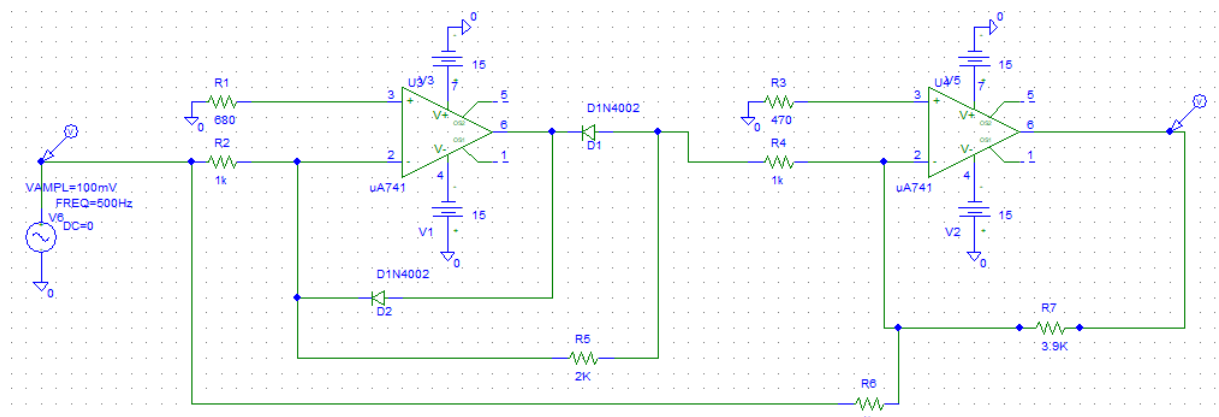**SIMULATION CIRCUIT DIAGRAM (Precision FWR)****Procedure (Same for both HWR & FWR)**

1. Connections are made as shown in the circuit diagram.
2. The input square wave signal ( $V_i$ ) is set to 100mV(p-p) of 500Hz frequency.
3. For the chosen values of R and C, Observe the output Waveform ( $V_o$ ) on the CRO and verify it with the expected waveforms.
4. Repeat the experiment for different values of R and C

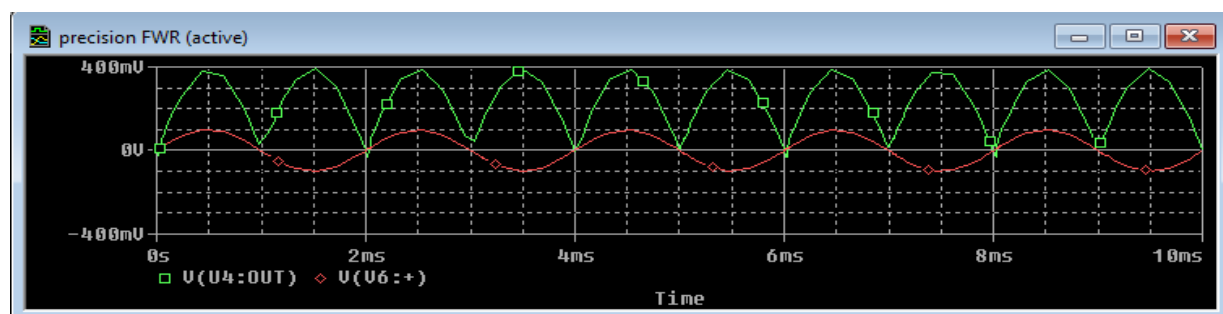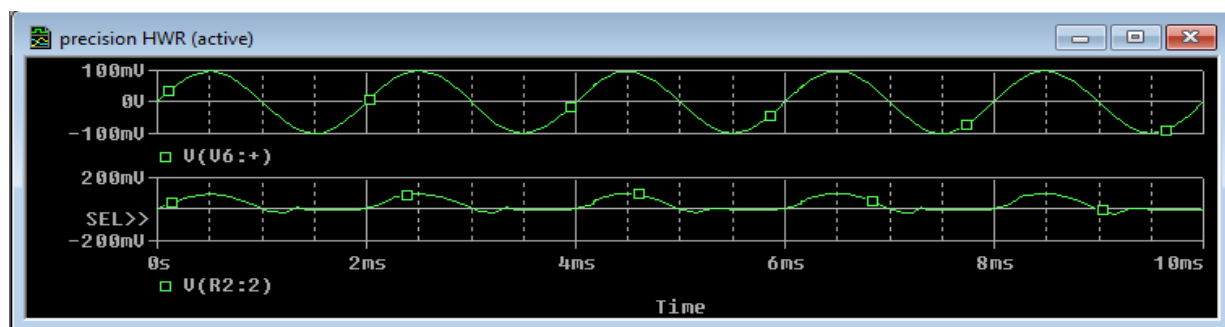**Result:**

Precision half wave and full wave rectified using opamp is verified