



**ACS** College of Engineering  
Approved by AICTE New Delhi, Affiliated to VTU, Belagavi  
(A Unit of RajaRajeswari Group of Institutions)



# Department of Electronics and Communication Engineering

## ELECTRONIC DEVICES AND INSTRUMENTATION LABORATORY MANUAL

**Subject Code: 18ECL37**

**Prepared by**  
**Mrs. Ashwini A M**  
**Assistant Professor, Dept. Of ECE**

**Checked By**  
**Dr. H B Bhuvaneshwari**  
**HOD, Dept. Of ECE**



**Affiliated to Visvesvaraya Technological University,**  
**Belagavi, Karnataka - 590018**

**2019-20**

<b>ELECTRONIC DEVICES AND INSTRUMENTATION LABORATORY</b>			
<b>SEMESTER – III (EC/TC)</b>			
<b>[As per Choice Based Credit System (CBCS) scheme]</b>			
<b>Laboratory Code</b>	<b>18ECL37</b>	<b>CIE Marks</b>	<b>40</b>
<b>Number of Lecture Hours/Week</b>	<b>02 Hr Tutorial (Instructions) + 02 Hours Laboratory</b>	<b>SEE Marks</b>	<b>60</b>
<b>RBT Level</b>	<b>L1, L2, L3</b>	<b>Exam Hours</b>	<b>03</b>
<b>CREDITS – 02</b>			
<p><b>Course objectives:</b> This laboratory course enables students to</p> <ul style="list-style-type: none"> <li>• Understand the circuit schematic and its working</li> <li>• Study the characteristics of different electronic devices</li> <li>• Design and test simple electronic circuits as per the specifications using discrete electronic components.</li> <li>• Familiarize with EDA software which can be used for electronic circuit simulation.</li> </ul>			
<b>Laboratory Experiments</b>			
<b>PART A : Experiments using Discrete components</b>			
1. Conduct experiment to test diode clipping (single/double ended) and clamping circuits (positive/negative)			
2. Half wave rectifier and Full wave rectifier with and without filter and measure the ripple factor			
3. Characteristics of Zener diode and design a Simple Zener voltage regulator determine line and load regulation			
4. Characteristics of LDR and Photo diode and turn on an LED using LDR			
5. Static characteristics of SCR.			
6. SCR Controlled HWR and FWR using RC triggering circuit			
7. Conduct an experiment to measure temperature in terms of current/voltage using a temperature sensor bridge.			
8. Measurement of Resistance using Wheatstone and Kelvin’s bridge.			
PART-B : Simulation using EDA software (EDWinXP, PSpice, MultiSim, Proteus, CircuitLab or any equivalent tool)			
1. Input and Output characteristics of BJT Common emitter configuration and evaluation of parameters.			
2. Transfer and drain characteristics of a JFET and MOSFET.			
3. UJT triggering circuit for Controller Rectifiers.			
4. Design and simulation of Regulated power supply.			

<b>COURSE OUTCOME</b>		
<b>COs</b>	<b>Electronic Devices and Instrumentation Lab (18ECL37)</b>	<b>Bloom's Level</b>
<b>CO1</b>	Understand the characteristics of various electronic devices and measurement of parameters.	<b>L1, L2, L3</b>
<b>CO2</b>	Design and test simple electronic circuits	<b>L1, L2, L3</b>
<b>CO3</b>	Use of circuit simulation software for the implementation and characterization of electronic circuits and devices	<b>L1, L2, L3</b>

## INDEX

<i>Sl. No:</i>	<i>Name of the experiment</i>	<i>Page No:</i>
<b>PART A : Experiments using Discrete components</b>		
<b>1.</b>	Conduct experiment to test diode clipping (single/double ended) and clamping circuits (positive/negative)	
<b>2.</b>	Half wave rectifier and Full wave rectifier with and without filter and measure the ripple factor	
<b>3.</b>	Characteristics of Zener diode and design a Simple Zener voltage regulator determine line and load regulation	
<b>4.</b>	Characteristics of LDR and Photo diode and turn on an LED using LDR	
<b>5.</b>	Static characteristics of SCR.	
<b>6.</b>	SCR Controlled HWR and FWR using RC triggering circuit	
<b>7.</b>	Conduct an experiment to measure temperature in terms of current/voltage using a temperature sensor bridge.	
<b>8.</b>	Measurement of Resistance using Wheatstone and Kelvin's bridge.	
<b>PART-B : Simulation using EDA software</b>		
<b>9.</b>	Input and Output characteristics of BJT Common emitter configuration and evaluation of parameters.	
<b>10.</b>	Transfer and drain characteristics of a JFET and MOSFET.	
<b>11.</b>	UJT triggering circuit for Controller Rectifiers.	
<b>12.</b>	Design and simulation of Regulated power supply.	

# Experiment No.1

## Diode Clipping and Clamping Circuits

**AIM:** To conduct an experiment to test diode clipping (single/double ended) and clamping circuits (positive/negative).

### COMPONENTS REQUIRED:

S.N	Particulars	Type	Range	Quantity
1.	Signal Generator	---	---	01
2.	Regulated Power Supply	---	0-30V	02
3.	Oscilloscope	---	---	01
4.	Bread Board/Spring Board	---	---	01
5.	Diode	IN4007	---	02
6.	Resistor	Carbon	10K $\Omega$	02
7.	Capacitor	Electrolyte	---	01
8.	Connecting wires	Single strand	---	few

### THEORY:

The circuit with which the waveform is shaped by removing (or clipping) a portion of the applied wave is known as a clipping circuit.

Clippers find extensive use in radar, digital and other electronic systems, although several clipping circuit have been developed to change the wave shape, we shall confine our attention to diode clippers. These clippers can remove signal voltages above or below a specified level

The important diode clippers are:

1. Parallel clipper circuits
2. Series clipper circuits

Further it can also be classified into:

1. Positive clippers,
2. Negative clippers
3. Biased clipper
4. Combinational clippers.




A clipping circuit comprises of linear elements like resistors and nonlinear elements like junction diode or transistor, but it does not contain energy storage elements like capacitors.

Clipping circuits are used to select, for purposes of transmission, that part of a signal wave from which lies above or below a certain reference voltage level. There are generally two categories of clippers: series and parallel. The series configuration is defined as one where diode is in series with the load while the parallel variety has the diode in a branch parallel to the load.




A transfer characteristic is the plot of output voltage  $V_o$  vs  $V_i$  that depends upon whether diode is ON or OFF. By the switching action of nonlinear element, definite relationship can be obtained between  $V_o$  and  $V_i$  in practical clipper circuits. The equation connecting  $V_o$  and  $V_i$ , is termed as transfer characteristic equation.

**CIRCUIT DIAGRAM**

**i) Positive Peak Clipping:**

   


**ii) Negative Peak Clipping**

   


**iii) Double Ended Clipping**


**CIRCUIT DIAGRAM:**

 

**Input & Output Waveform**

 

**Transfer Characteristics**

 

**PROCEDURE**

1. Connect the components as shown in circuit diagram.
2. Apply sine wave input signal ( $V_i$ ) at frequency of 1KHz from the signal generator and adjust the peak to peak amplitude 10 Vp-p.
3. Connect the input signal to channel 1, clipped output signal to channel 2 and observe input and output waveforms for different values of  $V_R$  on Oscilloscope.
4. Keep Oscilloscope in X-Y mode and observe the transfer characteristics.
5. Draw the input, output waveform and Transfer characteristics curve on the graph sheet

**TABULAR COLUMN**

**i) Positive Peak Clipping**

SL No.	Theoretical			Practical
	$V_R$	$V_D$	$V_O = V_R + V_D$	$V_O$
1				
2				
3				
4				
5				

**ii) Negative Peak Clipping**

SL No.	Theoretical			Practical
	$V_R$	$V_D$	$V_O=V_R+V_D$	$V_O$
1				
2				
3				
4				
5				

**iii) Double Ended Clipping**

SL No.	Theoretical					Practical	
	$V_D$	$V_{R1}$	$V_{R2}$	$V_{O1}=V_{R1}+V_D$	$V_{O2}=V_{R2}+V_D$	$V_{O1}=V_{R1}+V_D$	$V_{O2}=V_{R2}+V_D$
1							
2							
3							
4							
5							

**CLAMPING CIRCUITS THEORY:**

Sometimes it is necessary to add a DC level to the AC output signal. The circuits which are used to add a DC level as per the requirements to the AC output signal are called Clamper circuit. The capacitor, diode and resistance are the three basic elements of a clamper circuit. The clamper circuits are also called DC Restorer or DC Inverter circuits. Depending upon the whether the positive DC or negative DC shift is introduced in the output waveform, the clampers are classified as,

- Negative Clampers
- Positive Clampers

 
**1. NEGATIVE CLAMPER:**

Fig:1

 


Fig:2

A simple negative clamper which adds a negative level to the AC output is shown in fig.1. It consists of a capacitor C, the ideal diode D and the load resistor  $R_L$ .

During the first positive cycle of the input voltage  $V_i$  the capacitor gets charged through forward biased diode D up to the maximum value  $V_m$  of the input signal  $V_i$ . The capacitor charging is almost instantaneous, which is possible by selecting proper values of C and  $R_L$  in the circuit. The capacitor once charged to  $V_m$ , acts as a battery of voltage  $V_m$  as shown in the fig.2.



Thus when  $V_i = V_m$ , the output voltage  $V_o$  is zero. As input voltage decreases after attaining its maximum value  $V_m$ , the capacitor remains charged to  $V_m$ , and the diode  $D$  becomes reverse biased. And the output voltage  $V_o$  is now given by,

$$V_o = V_i - V_m$$

In the negative half cycle of  $V_i$ , the diode will remain reverse biased. The capacitor starts discharging through the resistance  $R_L$ . As the time constant  $R_L C$  is very large, it can be approximated that the capacitor holds all its charge and remains charged to  $V_m$ , during this period. Hence we can write again that,

$$\begin{aligned} V_o &= V_i - V_m \\ V_o &= -V_m \quad \text{for } V_i = 0 \\ V_o &= 0 \quad \text{for } V_i = V_m \\ V_o &= -2V_m \quad \text{for } V_i = -V_m \end{aligned}$$

## 2. POSITIVE CLAMPER

 


Fig:3

 


Fig:4

By changing the orientation of the diode in the negative clamper, the positive clamper circuit can be achieved. The circuit is shown in fig 3.

During the negative half cycle of the input voltage  $V_i$ , diode  $D$  gets forward biased and almost instantaneously capacitor gets charged equal to the maximum value  $V_m$  of the input signal  $V_i$ .

The capacitor once charged to  $V_m$ , acts as a battery of voltage  $V_m$ , with the polarities as shown in fig. 4.

Thus when  $V_i = V_m$ , the output voltage  $V_o$  is  $2V_m$ . Under steady state conditions we can write,


$$V_o = V_i + V_m$$

In the positive half cycle, the diode  $D$  is reverse biased. The capacitor starts discharging through  $R_L$ . But due to large time constant, it hardly gets discharged during positive half cycle of  $V_i$ . It holds its entire charge. Hence,


$$\begin{aligned} V_o &= V_i + V_m \\ V_o &= V_m \quad \text{for } V_i = 0 \\ V_o &= 2V_m \quad \text{for } V_i = V_m \\ V_o &= 0 \quad \text{for } V_i = -V_m \end{aligned}$$

**CIRCUIT DIAGRAM**

**iv) Positive Clamper:**

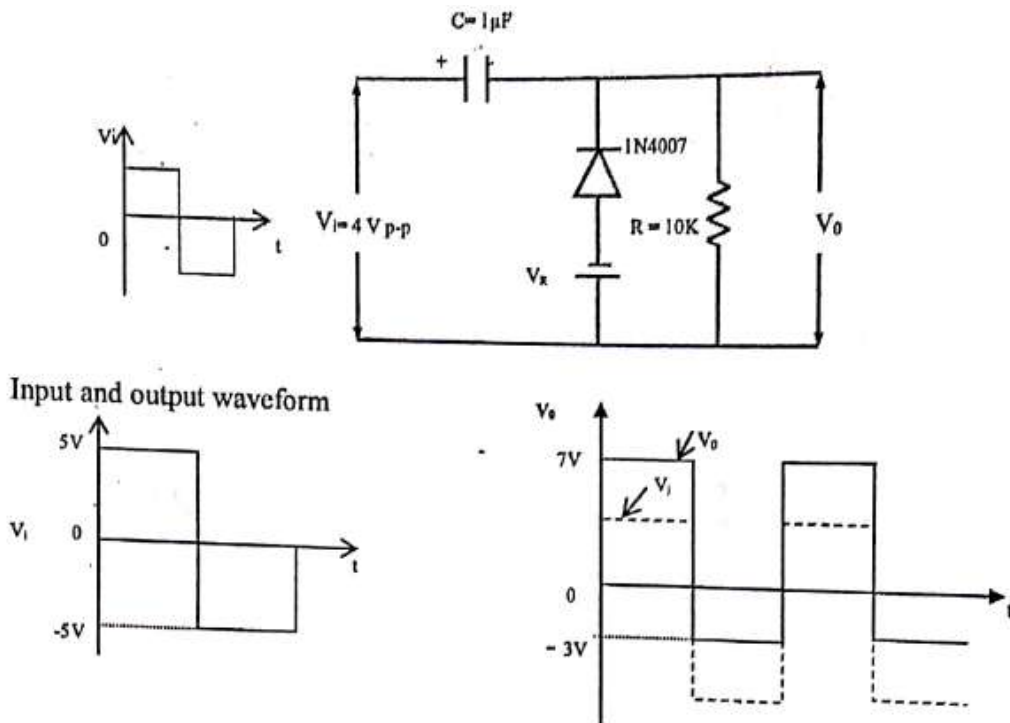

**iv) Negative Clamper:**

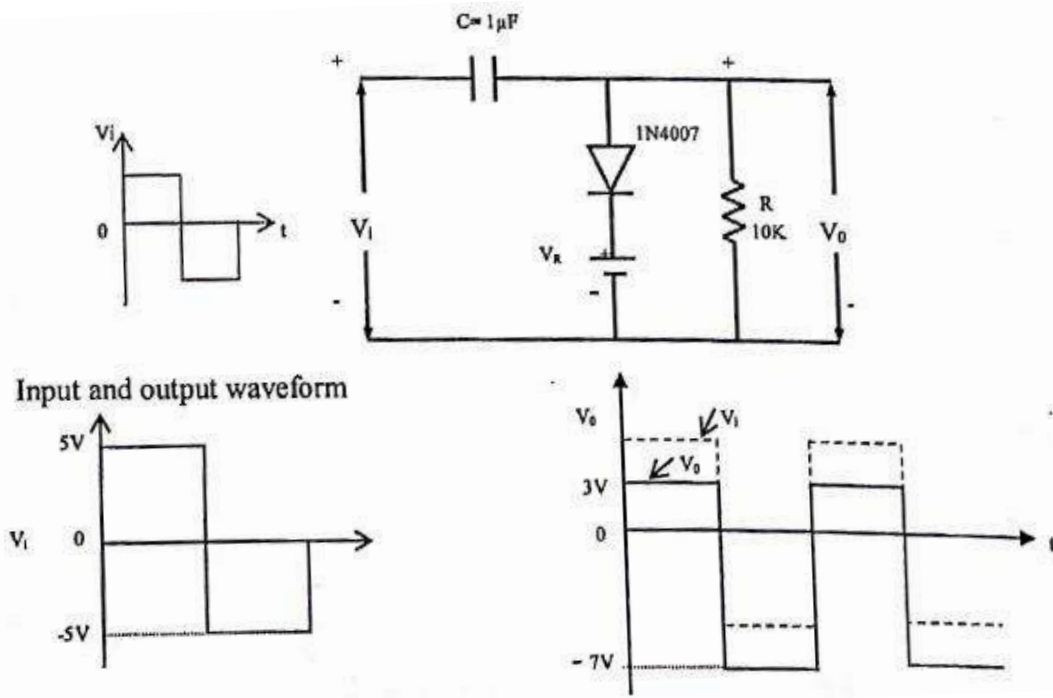

**PROCEDURE:**

1. Connect the components as shown in circuit diagram.
2. Apply sine wave input signal ( $V_i$ ) at frequency of KHz from the signal generator and adjust the peak to peak amplitude  $4V_{p-p}$ .
3. Connect the input signal to channel 1, clamped output signal to channel 2 and observe input and output waveforms for different values of  $V_R$  on Oscilloscope.
4. Draw the input and output waveform on the graph sheet.

**Tabular column****i) Positive Clamper**

SL. NO	Theoretical				Practical	
	$V_R$	$V_D$	$V_{o+} = V_{inp-p} - (V_R + V_D)$	$V_{o-} = -(V_R + V_D)$	$V_{o+}$	$V_{o-}$
1						
2						
3						
4						
5						

**ii) Negative Clamper**

SL. NO	Theoretical				Practical	
	$V_R$	$V_D$	$V_{o+} = (V_R + V_D)$	$V_{o-} = [V_{inp-p} - (V_R + V_D)]$	$V_{o+}$	$V_{o-}$
1						
2						
3						
4						
5						

## Experiment No.2

### Rectifier Circuits

**AIM:** To Design and set up half wave and full wave rectifiers with and without filters and determine ripple factor and efficiency:

#### COMPONENTS REQUIRED:

S.N	Particulars	Type	Range	Quantity
1.	Oscilloscope	---	---	01
2.	Bread Board	---	---	01
3.	Diode	IN4007	---	02
4.	Resistor	Carbon	10K $\Omega$	01
5.	Capacitor	Electrolyte	10 $\mu$ F	01
6.	Transformer		12-0-12Vpp	01
7.	Connecting wires	Single strand	---	few


#### THEORY:

Rectification is the process of converting the alternating quantity (AC) to the unidirectional quantity (DC with pulsation). The transformer is used to step down the voltage from 230V to the desired level. Then, the diode is responsible for the conversion of ac available at the secondary of the transformer into DC with pulsation. Hence, the diode used for this application is also referred as rectifier. The capacitor connected across the load (resistor) is behaving as a filter. Filter is responsible to smooth the pulsating DC into pure DC.



Half wave rectifier is one which converts the ac into pulsating dc during one half of the cycle. It has poor ripple factor, conversion efficiency and voltage regulation. Full wave rectifier is one which converts the ac into pulsating dc during both cycles. For this process two diodes and centre tapped transformer are required. It has better ripple factor, conversion efficiency and voltage regulation compared to the half wave rectifier.

#### CIRCUIT DIAGRAM:


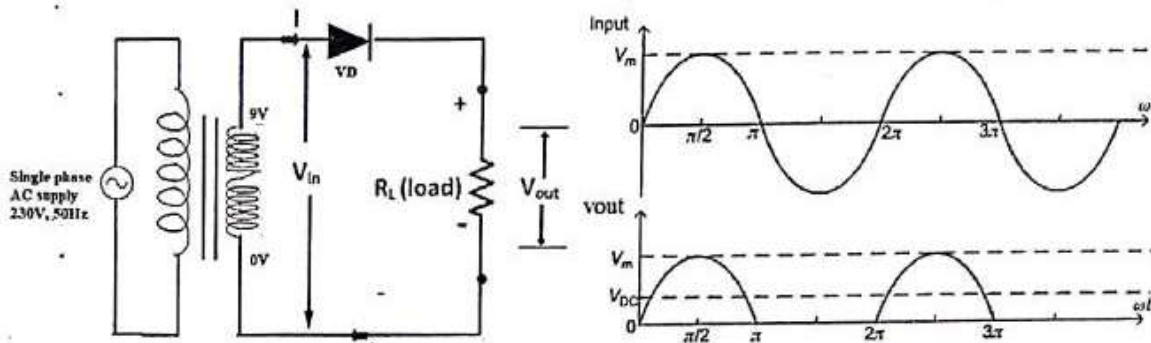
##### Half wave rectifier without filter:





### Half wave rectifier with filter

  

### Full wave rectifier without filter

  
 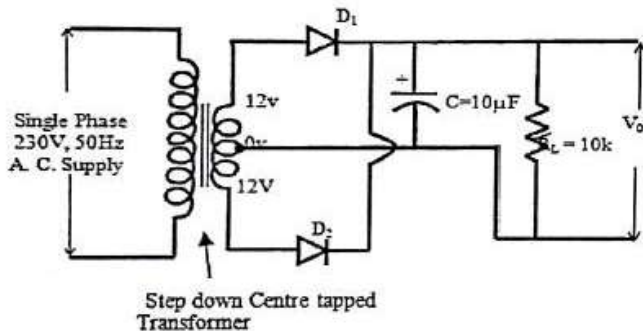
### Full wave rectifier with capacitor –Filter



### PROCEDURE:

1. Connect the components as shown in circuit diagram.
2. Note down the maximum value of output voltage ( $V_m$ ) from the oscilloscope.
3. Calculate  $V_o(\text{dc})$ ,  $V_o(\text{rms})$ ,  $I_o(\text{dc})$  &  $I_o(\text{rms})$
4. Find rectifier efficiency ( $\eta$ ) and ripple factor ( $Y$ ).
5. Connect the capacitor – filter across load resistor  $R_L$  as shown in circuit diagram and calculate ripple factor ( $Y$ ).

**Tabular Column for HWR without filter:**

<b>R Load</b>	<b>Vac</b>	<b>Vdc</b>	<b>Ripple Factor</b>	<b>Efficiency %</b>

**Tabular Column for HWR with filter:**

<b>R Load</b>	<b>Vac</b>	<b>Vdc</b>	<b>Ripple Factor</b>	<b>Efficiency %</b>

**Tabular Column for FWR without filter:**

<b>R Load</b>	<b>Vac</b>	<b>Vdc</b>	<b>Ripple Factor</b>	<b>Efficiency %</b>

**Tabular Column for FWR with filter:**

<b>R Load</b>	<b>Vac</b>	<b>Vdc</b>	<b>Ripple Factor</b>	<b>Efficiency %</b>

## Experiment No. 3

### Zener Diode as Voltage Regulator

**AIM:** To study the Characteristics of Zener diode and design a Simple Zener voltage regulator determine line and load regulation.

#### COMPONENTS REQUIRED:

S.N	Particulars	Type	Range	Quantity
1.	Bread Board	---	---	01
2.	Zener Diodes	(IN4735A)	---	01
3.	Resistor	Carbon	1K $\Omega$ ,3.3K $\Omega$	01
4.	Digital Ammeter	---	0-200 mA	02
5.	Digital Voltmeter	---	0-20V	01
6.	Decade Resistance Box (DRB)	---	---	01
7.	Dual DC Regulated power supply	---	0-30V	01
8.	Connecting wires	Single strand	---	few

#### THEORY:

Zener diodes are a special kind of diode which permits current to flow in the forward direction. And also allow current to flow in the reverse direction when the voltage is above a certain value. This breakdown voltage is known as the Zener voltage.

In the forward bias direction, the zener diode behaves like an ordinary silicon diode. In the reverse bias direction, there is practically no reverse current flow until the breakdown voltage is reached. When this occurs there is a sharp increase in reverse current. Varying amount of reverse current can pass through the diode without damaging it. The breakdown voltage or zener voltage (V) across the diode remains relatively constant. The maximum reverse current is limited, however, by the wattage rating of the diode.

#### Zener Breakdown:

If both p-side and n-side of the diode are heavily doped, depletion region at the junction reduces compared to the width in normal doping. Applying a reverse bias causes a strong electric field get applied across the device. As the reverse bias is increased, the Electric field becomes strong enough to rupture covalent bonds and generate large number of charge carriers. Such sudden increase in the number of charge carriers due to rupture of covalent bonds under the influence of Strong electric field is termed as Zener breakdown.


#### Zener Diode as Voltage Regulator:

The purpose of a voltage regulator is to maintain a constant voltage across a load regardless of variations in the applied input voltage and variations in the load current. Basically there are two types of regulation such as;



- a. **Line Regulation:** This type of regulation, series resistance and load resistance are fixed, only input voltage is changing. Output voltage remains the same as long as the input voltage is maintained above minimum value.
- b. **Load Regulation:** In this type of regulation, Input voltage is fixed and the load resistance is varying, Output voltage remains same, as long as the load resistance is maintained above a minimum value.

## CIRCUIT DIAGRAM

### Forward Characteristics

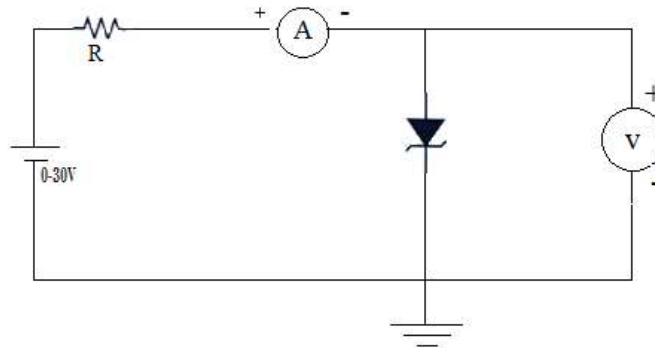

### Reverse Characteristics

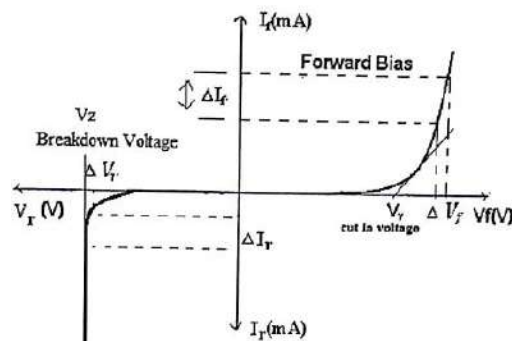 

**Fig: V-I Characteristics of Zener diode under forward and reverse bias conditions**



**PROCEDURE:****Forward Bias:**

1. Connect the circuit as per the circuit diagram
2. Vary the power supply such that readings are taken in a step of 0.1V
3. Note down the corresponding Ammeter reading
4. Plot the graph of  $V_f$  V/s  $I_f$

**Reverse Bias:**


1. Connect the circuit as per the circuit diagram
2. Vary the power supply such that readings are taken in a step of 0.5V
3. Note down the corresponding Ammeter reading
4. Plot the graph of  $V_r$  V/s  $I_r$

**TABULAR COLUMN:****Forward Bias**

SI No	$V_F$	$I_F$

**Reverse Bias**

SI No	$V_R$	$I_R$

 **Zener Diode as Voltage regulator****PROCEDURE:****Zener Diode as Line Regulator (for variations in supply voltage):**

1. Rig up the Circuit as shown
2. For Voltage Regulation, Keep the load Resistance at  $10K\Omega$ , and change the input voltages. Take the readings of O/P Voltmeter ( $V_o = V_z$ ).
3. Now fix the power supply voltage,  $V_i$ , at 10V.
4. Without connecting the load  $R_L$ , note down the No-Load Voltage ( $V_{NL}$ ).

5. Now connect the load ( $R_L$ ) using Decade Resistance Box (DRB) and vary the resistance in steps  $1K\Omega$  from  $1K\Omega$  to  $10K\Omega$  / in steps of  $10 K\Omega$  from  $10K\Omega$  to  $100 K\Omega$  and note the corresponding Zener Current ( $I_Z$ ), Load Current ( $I_L$ ) and Output Voltage ( $V_O$ ) for 10 readings and calculate the percentage regulation.

6. Plot the graph between  $R_L$  and  $V_O$  taking  $R_L$  on X-axis and  $V_O$  on Y-axis.

### TABULAR COLUMN:

#### Line Regulation:

Load Resistance  $R_L =$  \_\_\_\_\_ ( $K\Omega$ )

Unregulated Power Supply $V_S(V)$	Zener Current $I_Z(mA)$	Load Current $I_L(mA)$	Regulated Output Voltage $V_O(V)$

#### Load Regulation:

Input Supply Voltage  $V_S =$  \_\_\_\_\_ Volts

No-load DC Voltage,  $V_{NL} =$  \_\_\_\_\_ Volts

Load Resistance $R_L (K\Omega)$	Zener Current $I_Z(mA)$	Load Current $I_L (mA)$	Regulated Output Voltage $V_O(V)$	% Voltage Regulation

#### Calculations from Graph:

Static forward Resistance  $R_{dc} = V_S/I_S\Omega$

Dynamic Forward Resistance  $r_{ac} = \Delta V_S/\Delta I_S\Omega$

Static Reverse Resistance  $R_{dc} = V_r/I_r\Omega$

Dynamic Reverse Resistance  $r_{ac} = \Delta V_r/\Delta I_r\Omega$

For load regulations, % Voltage Regulation =  $((V_{NL} - V_{FL})/V_{FL}) \times 100$  %

## Experiment No: 4

# CHARACTERISTICS OF LDR AND PHOTO DIODE AND TURN ON AN LED USING LDR

**AIM:** To determine the characteristics of LDR and Photo diode and tun on an LED using LDR

### APPARATUS:

SL No	Components	Range	Quantity
1	Resistors	1K $\Omega$ , 10K $\Omega$ , 100K $\Omega$ , 10% tolerance, 1/2 watt rating	1
2	Photodiode	QSD 2030F	1
3	Phototransistor	BPW77NA	1
4	Regulated power supply	(0-30V), 2A Rating	1
5	Ammeter	(0-30)mA; (0-30) $\mu$ A	1
6	Voltmeter	MC (0-10)V	1
7	LDR	---	1
8	Bread board	---	1
9	Connecting wires	---	Few

### THEORY:


#### LDR

A photoresistor or light dependent resistor or cadmium sulfide (CdS) cell is a resistor whose resistance decreases with increasing incident light intensity. It can also be referred to as a photoconductor. A photoresistor is made of a high resistance semiconductor. If light falling on the device is of high frequency, photons absorbed by the semiconductor gives enough energy to for electrons to jump into the conduction band. The resulting free electron (and its hole partner) conduct electricity, thereby lowering resistance

#### Photodiode

A silicon photodiode is a solid state light detector that consists of a shallow diffused P-N junction with connections provided to the outside world. When the top surface is illuminated, photons of light penetrate into the silicon to a depth determined by the photon energy and are absorbed by the silicon generating electron-hole pairs. The electron-hole pairs are free to diffuse (or wander) throughout the bulk of the photodiode until they recombine. The average time before recombination is the minority carrier lifetime. At the P-N Junction is a region of strong electric field called the depletion region. It is formed by the voltage potential that exists at the P-N junction. Those light generated carriers that wander into contact with this field are swept across the junction. If an external connection is made to both sides of the junction a photo induced current will flow as long as light falls upon the photodiode. In addition to the photocurrent, a voltage is produced across the diode. In effect, the photodiode functions exactly like a solar cell by generating a current and voltage when exposed to light.

**CIRCUIT DIAGRAM:**

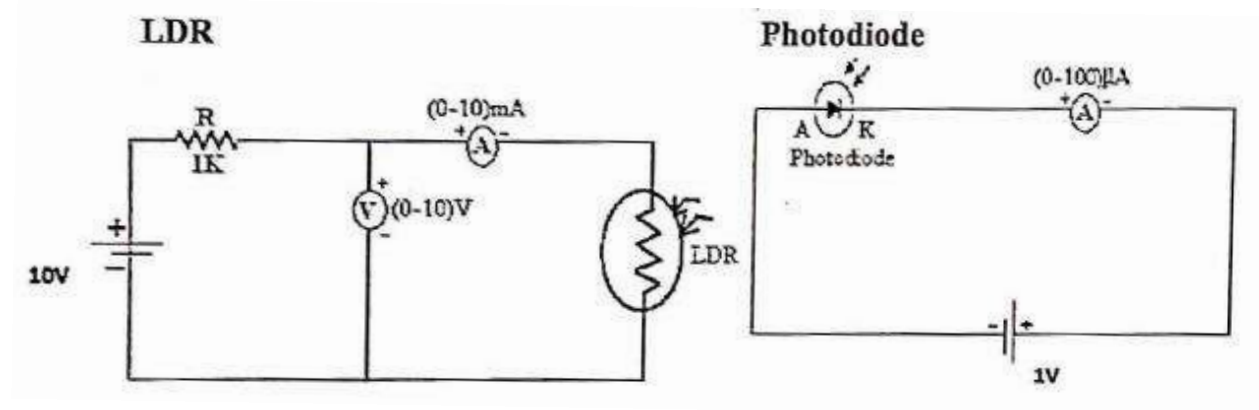

**TABULAR COLUMN**

**LDR**

Distance(cm)	Voltage(V)	Current(mA)	Resistance(KΩ)=V/I

**Photodiode**



SL NO	Without Light		With Light	
	Reverse voltage $V_R$ in V	Reverse current $I_R$ in mA	Reverse voltage $V_R$ in V	Reverse current $I_R$ in mA

**PROCEDURE:****LDR:**

1. Connect circuit as shown in figure
2. Keep light source at a distance and switch it ON, so that it falls on the LDR
3. Note down current and voltage in ammeter and voltmeter.
4. Vary the distance of the light source and note V&I
5. Sketch graph between R as calculated from observed V and I and distance of light source

**Photodiode:**

1. Connect circuit as shown in figure
2. Maintain a known distance between the bulb and photodiode say 5cm
3. Set the bulb voltage, vary the voltage of the diode in steps of 1V and note the diode current  $I_R$ .
4. Repeat above procedure for  $V_L=4V, 6V$ , etc.
5. Plot the graph:  $V_D$   $V_S$   $I_R$  for constant  $V_L$

 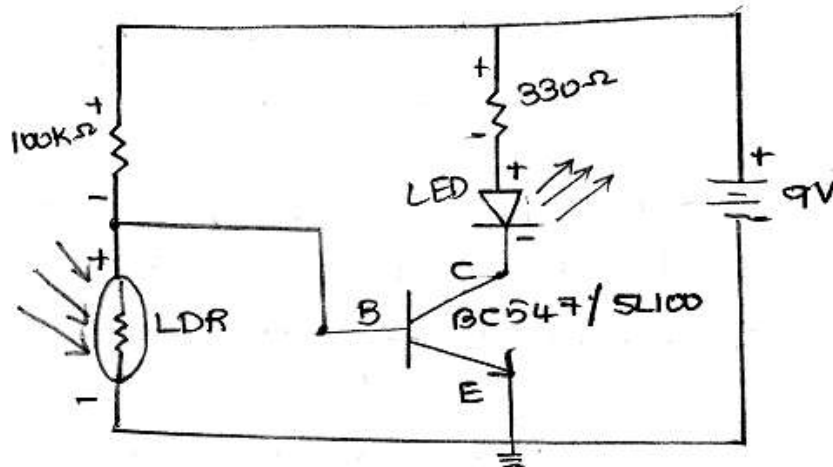**Model Graph:****Circuit to switch ON /OFF an LED using LDR**

## Experiment No. 5

# STATIC CHARACTERISTICS OF SCR


**AIM:** To conduct and plot V-I static characteristics of SCR and determine Latching current and Holding current.

**APPARATUS:**

SLNO	Components	Range	Quantity
1	DC Power Supply	0-30V	2
2	Resistor	100Ω	1
3	SCR	100KΩ	1
4	DC voltmeter	(0-20) V	1
5	DC ammeter	(0-200) mA (0-200)μA	1
6	Connecting wires		Few

 **THEORY:**

It is a four layer semiconductor device being alternate of P-type and N-type silicon. It consists of 3 junctions J1, J2, J3 the J1 and J3 operate in forward direction and J2 operates in reverse direction and three terminals called anode A, cathode K, and a gate G. The operation of SCR can be studied when the gate is open and when the gate is positive with respect to cathode.



Schematic symbol

When gate is open, no voltage is applied at the gate due to reverse bias of the junction J2 no current flows through R2 and hence SCR is at cut off. When anode voltage is increased J2 tends to breakdown.

When the gate positive, with respect to cathode J3 junction is forward biased and J2 is reverse biased. Electrons from N-type material move across Junction J3 towards gate while holes from P-type material moves across junction J3 towards cathode. So gate current starts flowing, anode current increases.

When gate is open, the break over voltage is determined on the minimum forward voltage at which SCR conducts heavily. Now most of the supply voltage appears across the load resistance. The holding current is the maximum anode current when gate being open, when break over occurs.

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. Set both voltage sources to zero volts.

**To find minimum gate current,**

3. Set  $V_{AK}$  from 10 to 15 V. Slowly vary  $V_{AK}$  in steps of 1V. Note down the corresponding  $I_G$  and  $I_{AK}$  values.
4. At some point,  $I_{AK}$  is suddenly increased and  $V_{AK}$  decreases.
5. Note down the minimum gate current required to turn on SCR.
6. Set both voltage sources to zero volts.

**V I Characteristics**


7. Set the minimum gate current in terms of mA
8. Slowly vary  $V_{AK}$ , note down corresponding values of  $I_{AK}$ .
9. Draw the graph  $V_{AK}$  V/S  $I_{AK}$

**To find Latching current**


10. Set  $V_{AK}$  and  $V_{GK}$  in minimal position
11. Switch on power supply vary  $V_{AK}$  and set  $I_G$
12. Slowly vary  $V_{AK}$ , note down the corresponding values of  $I_{AK}$  and simultaneously remove the gate pulse and check the state of SCR (ON/OFF)
13. If the SCR is ON even if gate pulse is removed, then the corresponding current is called latching current.

**To find holding current**

14. Turn on SCR by normal method.
15. Decrease  $V_{AK}$  gradually
16. Note down Anode current at which SCR turns OFF. Corresponding Anode current is the holding

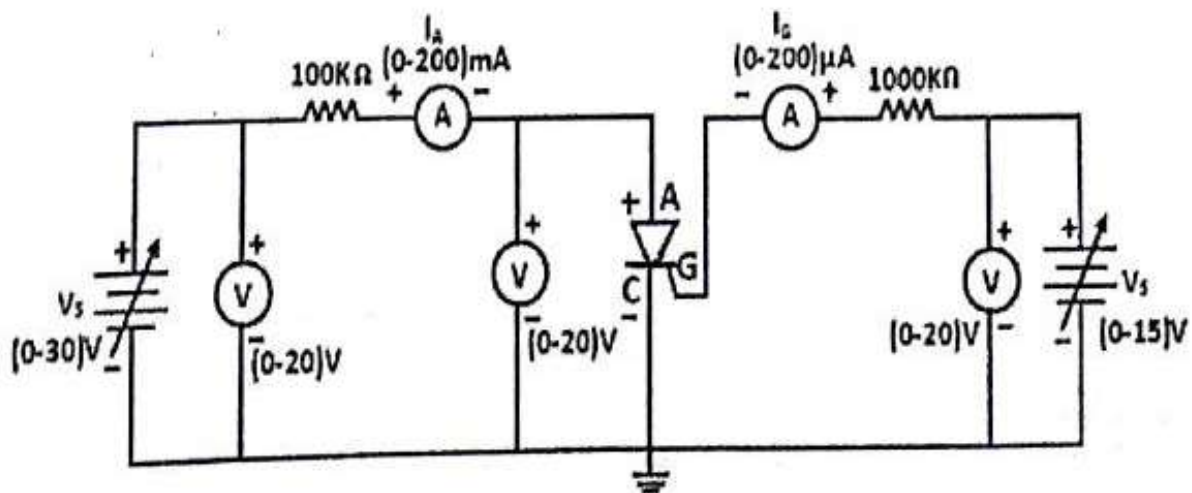**CIRCUIT DIAGRAM:**

**EXPECTED GRAPH:**

 

**TABULAR COLUMN:**

SL NO	Gate current= _____ $\mu\text{A}$		Gate current= _____ $\mu\text{A}$	
	Anode to cathode voltage	Anode current	Anode to cathode voltage	Anode current

**RESULT:**

Static characteristics of SCR is analysed  
 Latching current is .....  
 Holding current is .....



## Experiment No. 6

### SCR controlled HWR and FWR using RC Triggering circuit


**AIM:** To study the performance and waveforms of HWR & FWR by using RC triggering circuit

**APPARATUS:**


SL No	Components	Range	Quality
1	DC Power Supply	0-30V	2
2	Resistor	100Ω	1
3	Transformer	230V, 50Hz	1
4	SCR Diode	TY604 BY127	1
5	DC voltmeter	(0-20)V	1
6	DC ammeter	(0-200)mA (0-200)μA	1
7	Connecting wires		

**CIRCUIT DIAGRAM:**


**Half wave rectifier:**

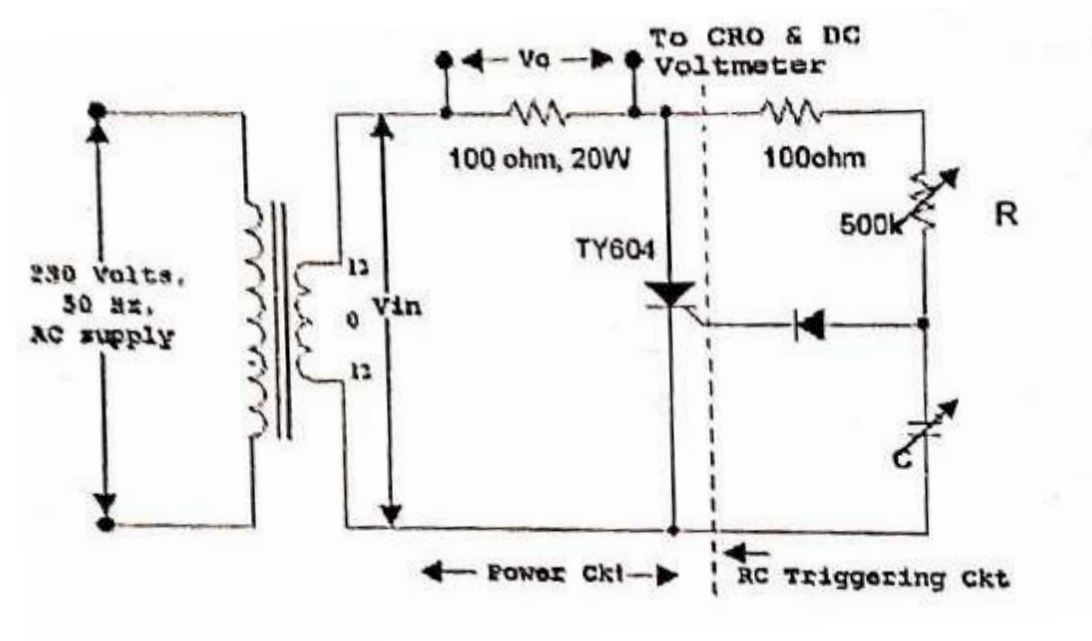



Waveforms:

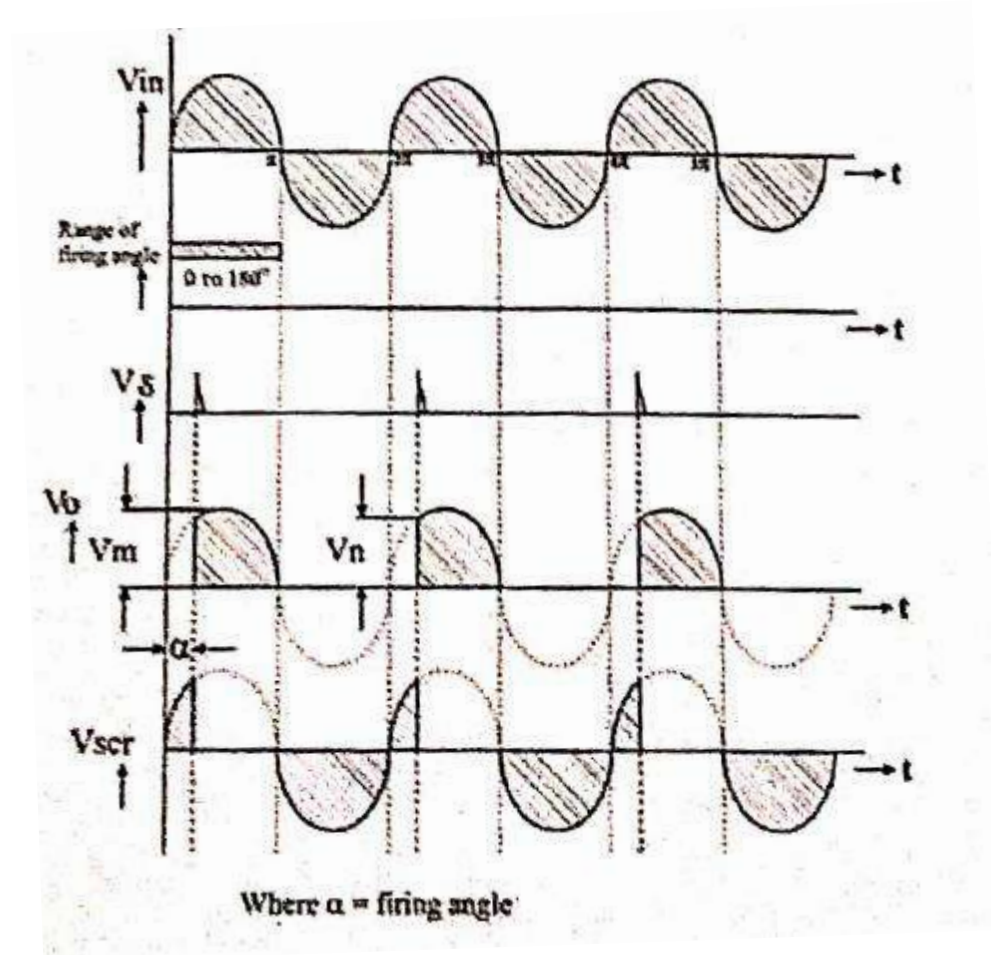

Graph:

 

Full wave rectifier:

 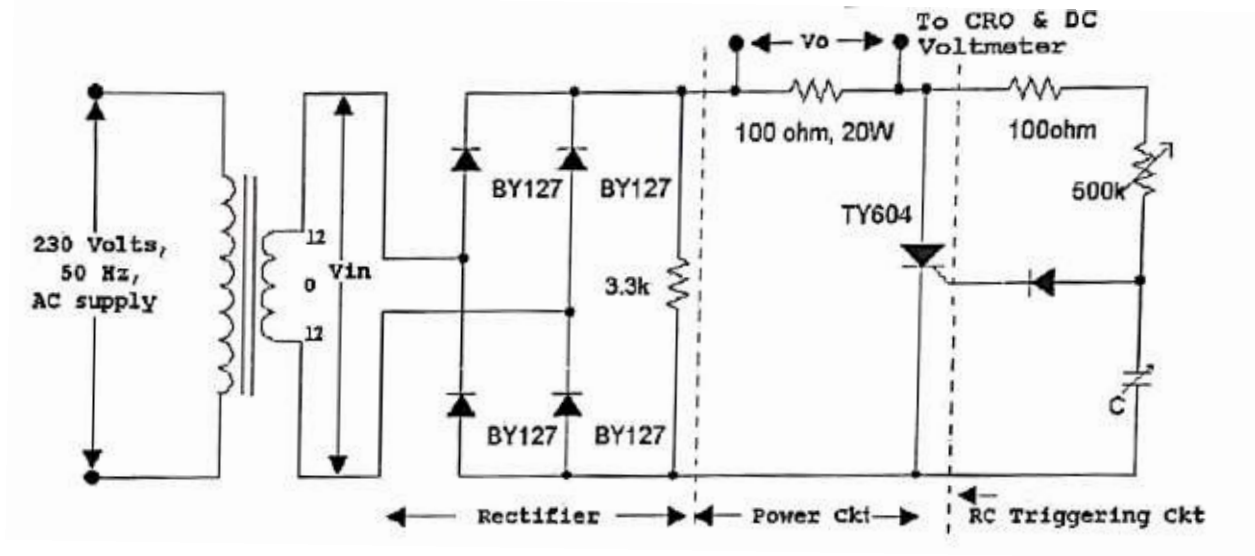

**PROCEDURE:****Half wave rectifier:**

1. Connections are made as shown in the circuit diagram.
2. By varying a resistance R gradually step by step, note down the corresponding values of  $V_n$  &  $V_m$  from CRO and  $V_{o\ dc}$  from the DC voltmeter. The readings are tabulated in the tabular column.
3. If the firing angle ranges from 0 to 90°, then the firing angle  $\alpha$  is calculated by using a formula  $\alpha = \sin^{-1}(V_n/V_m)$  in degrees.
4. The conduction angle  $\beta$  is calculated by using a formula,  $\beta = 180 - \alpha$ .
5. The current and power is calculated by  
 $I_{o\ dc} = (V_{o\ dc}/R)$  in A &  $P_{o\ dc} = V_{o\ dc}^2/R$  in watts respectively.
6. A graph of  $V_o$  v/s  $\alpha$ ,  $V_o$  v/s  $\beta$ ,  $I_o$  v/s  $\alpha$ ,  $I_o$  v/s  $\beta$ ,  $P_{o\ dc}$  v/s  $\alpha$ ,  $P_{o\ dc}$  v/s  $\beta$  to be plotted.
7. Compare practical output voltage with theoretical output voltage,

$$V_{oth} = V_m(1 + \cos \alpha)/2\pi \text{ volts where } V_m = \sqrt{2}V_{rms}$$

**Full wave rectifier:**

1. Repeat the above said procedure for full wave rectifier.

$$V_{oth} = V_m(1 + \cos \alpha)/\pi \text{ volts where } V_m = \sqrt{2}V_{rms}$$

**TABULAR COLUMN:****Half wave rectifier**

SL No	$V_n$	$V_m$	$\alpha < 90$ degree	$\alpha > 90$ degree	$V_{odc}$	$V_{oth}$
			$\alpha = \sin^{-1}(V_n/V_m)$	$\alpha = 180 - \sin^{-1}(V_n/V_m)$		

**Full wave rectifier**

SL No	$V_n$	$V_m$	$\alpha < 90$ degree	$\alpha > 90$ degree	$V_{odc}$	$V_{oth}$
			$\alpha = \sin^{-1}(V_n/V_m)$	$\alpha = 180 - \sin^{-1}(V_n/V_m)$		

## Experiment No. 7


# TEMPERATURE SENSOR BRIDGE CIRCUITS

**AIM:** To implement Wheatstone bridge circuits for temperature measurements using thermistors

### THEORY:
 
#### A. Voltage Dividers

Using resistors  $R_1$  and  $R_T$ , the voltage can be split depending on the ratio between the two resistors.



$$\left. \begin{array}{l} I_{ab} = I_{bc} \\ V_s = V_{ab} + V_{bc} \end{array} \right\} \rightarrow \begin{array}{l} \frac{V_{ab}}{R_1} = \frac{V_{bc}}{R_T} \\ V_s = \frac{R_1}{R_T} V_{bc} + V_{bc} \\ V_{bc} = \frac{R_T}{R_1 + R_T} V_s \end{array}$$

Application: If  $R_T$  is the resistance of a "resistance sensor", e.g. an RTD (resistance temperature detector), a thermistor or a strain gauge, one can measure changes in  $R_T$  by measuring  $V_{bc}$  (with  $V_s$  and  $R_1$  fixed).

#### B. Wheatstone Bridge

Main idea: By adding another (comparator) voltage divider in parallel to that shown in Figure, one could use differential voltage measurements around zero for improved sensitivity in sensor applications, while reducing current flow through component  $R_T$ .

(Note that high electrical currents increase heat in resistors. These effects introduce measurement errors since they are unrelated to the variables being measured).

 


Figure 2: Wheatstone bridge. (M is the voltmeter)

Assuming that very little current flows through the voltmeter, i.e. setting  $I_{fb}=0$ ,

$$\begin{aligned} I_{ab} = I_{bc} &\rightarrow \frac{V_{ab}}{R_1} = \frac{V_{bc}}{R_2} \rightarrow V_{ab} = V_{bc} \frac{R_1}{R_2} \\ I_{df} = I_{fg} &\rightarrow \frac{V_{df}}{R_3} = \frac{V_{fg}}{R_T} \rightarrow V_{df} = V_{fg} \frac{R_3}{R_T} \end{aligned} \quad (2)$$

Summing voltages around each loop.

$$\begin{aligned} V_s &= V_{ab} + V_{bc} \\ V_{ab} &= V_{df} + V_{fb} \rightarrow V_s = V_{ab} + V_{bc} = V_{df} + V_{fg} \\ V_{bc} + V_{fb} &= V_{fg} \end{aligned} \quad (3)$$

Substituting (2) into (3),

$$V_s = V_{bc} \left( 1 + \frac{R_1}{R_2} \right) = V_{fg} \left( 1 + \frac{R_3}{R_T} \right) \quad (4)$$

Applying (4) to the loop containing  $V_{bc}$ ,  $V_{fb}$  and  $V_{fg}$ ,

$$\begin{aligned} V_{fb} &= V_{fg} - V_{bc} \\ &= V_s \left( \frac{1}{1 + \frac{R_3}{R_T}} - \frac{1}{1 + \frac{R_1}{R_2}} \right) \\ &= V_s \left( \frac{R_T}{R_T + R_3} - \frac{R_2}{R_2 + R_1} \right) \end{aligned} \quad (5)$$


The bridge is "balanced" when  $V_{fb}=0$ , i.e. voltage reading in meter M is zero. This occurs when

$$\frac{R_3}{R_T} = \frac{R_1}{R_2}.$$

Since  $R_2$  is a variable resistor, the meter can be zeroed around the nominal value of the variable being sensed. For instance, if the component is an RTD, then the bridge is balanced around a nominal operating temperature  $T_0$ . Voltage readings of  $V_{fb}$  can then monitor temperature changes from  $T_0$ .

$R_1$	4.7 K $\Omega$
$R_2$	10 K $\Omega$ potentiometer
$R_3$	4.7 K $\Omega$
$V_s$	6 V power supply
Thermistor	$\sim 2.80$ K $\Omega$ @ 25 $^\circ$ C

### CIRCUIT DIAGRAM:

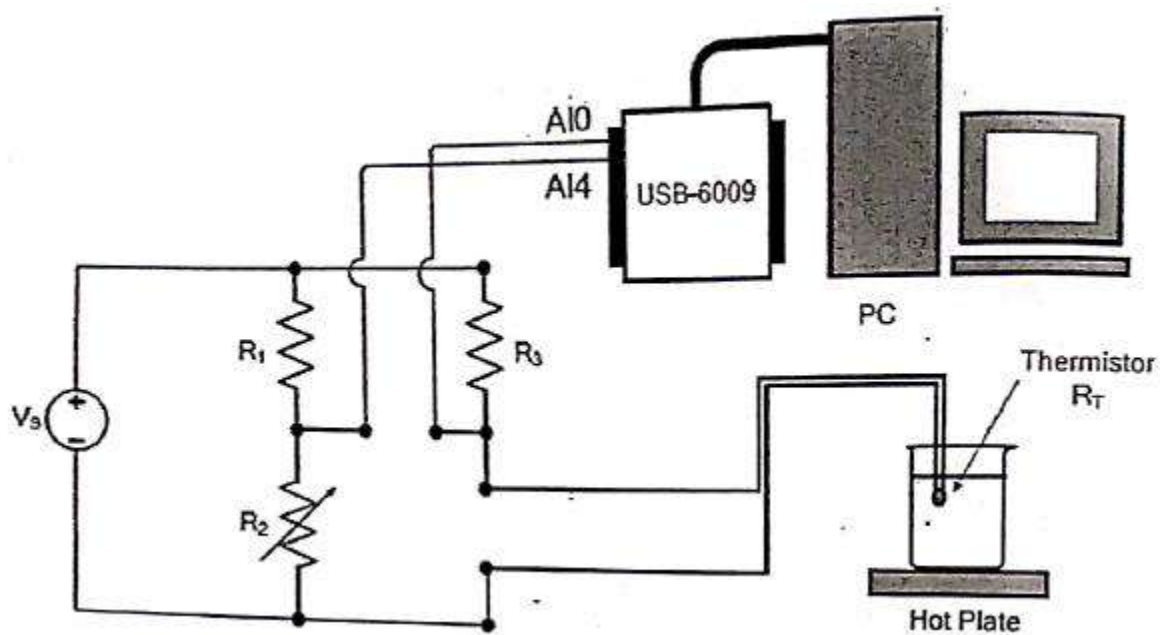

### PROCEDURE:

1. Prepare the setup shown in Figure and the Thermistor VI as well.
2. Note down the voltage readings for different temperature using multi meter.

Temperature ( $^\circ$ C)	Voltage (volts)
30	
35	
40	
45	
50	
55	
60	
65	

## Experiment No. 8

# MEASUREMENT OF RESISTANCE USING WHEATSTONE BRIDGE AND KELVIN'S BRIDGE

**AIM:** To measure the given unknown resistance using Wheatstone bridge Kelvin's bridge.

### APPARATUS:


SL NO	Components	Range	Quality
1	DC Power Supply	---	1
2	Few Resistors	100Ω, 1 K Ω, 10 K Ω	1
3	Galvanometer	---	1
4	Multimeter	---	1

### THEORY:

A wheat stone bridge is an electrical circuit used to measure an unknown resistance by balancing two legs of bridge circuit, one leg of which include the unknown components. Practically the variable resistance is adjusted till the value of galvanometer becomes Zero. At this point , bridge is said to be balanced.

At balanced condition,  $R_1/R_2=R_3/R_x$   
 $R_x= R_2 R_3/ R_1$

### CIRCUIT DIAGRAM:

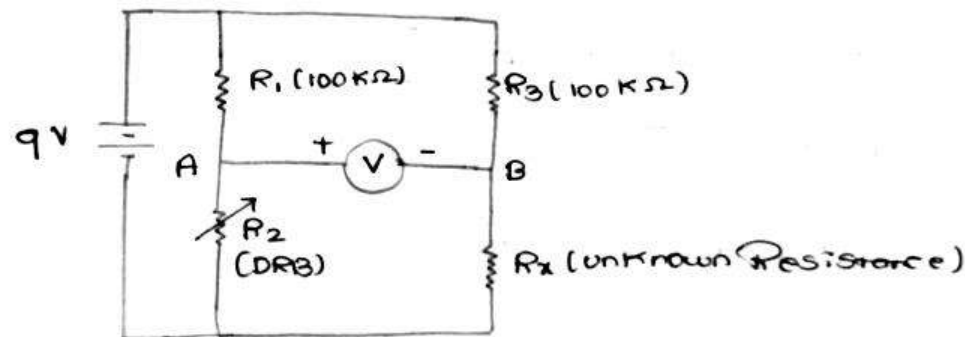

$$\text{Error} = \frac{\text{Actual Value} - \text{obtained Value}}{\text{Actual Value}} \times 100$$

### PROCEDURE:

1. Use 9V battery and take  $R_1 = R_3$
2. Connect the Circuit as Shown
3. The value of DRB is adjusted till the value of voltage displayed on the meter was closed to 0V
4. At some point, the value of decade resistance box is matched to the value of unknown resistance with 5 to 10% of tolerance.



**TABULAR COLUMN:**

SL NO	R <sub>1</sub> (Ω)	R <sub>2</sub> (Ω)	R <sub>3</sub> (Ω)	R <sub>x</sub> (Ω)

 
**KELVIN BRIDGE:****CIRCUIT DIAGRAM:**

Figure: Simplified kelvin Bridge Circuit

A Kelvin Bridge is a measuring instrument used to measure unknown electrical resistors below 1Ω. It is specifically designed to measure resistors that are constructed as four terminal resistors.

The operation of the Kelvin Bridge is very similar to the Wheatstone bridge except that it is complicated by the presence of two additional resistors; Resistors P and Q are connected to the outside potential terminals of the four terminal known or standard resistors S and the unknown resistor R. The resistors S, R, P and Q are essentially a Wheatstone bridge. In this arrangement, the parasitic resistance of the upper part of S and the lower part of R is outside of the potential measuring part of the bridge and therefore are not included in the measurement. However, the link between S and R is included in the potential measurement part of the circuit and therefore can affect the accuracy of the result. To overcome this, a second pair of resistors 'p' and 'q' form a second pair of arms of the bridge (hence 'double bridge') and are connected to the inner potential terminals of S and R. The detector D is connected between the junction of P and Q and the junction of p and q.

The balance equation of this bridge is given by the equation

$$R = \frac{(P/Q) S + qr}{(p+q+r)} \left[ \frac{P}{Q} - \frac{p}{q} \right]$$

As per the design  $P/Q = p/q$ , the value of unknown resistance is,

$$R = (P/Q) S$$

Above equation is the usual working equation for the Kelvin double bridge. It indicates that resistance of connecting lead  $r$  has no effect on the measurement provided that the two sets of ratio arms have equal ratios. The above equation is useful however 85 South error that is introduced in case the ratios are not exactly equal It is indicated that it is desirable to keep as small as possible in order to minimize the errors in case there is a difference between ratios  $P / Q$  and  $p/q$ . In a typical Kelvin bridge, the range of resistance calculated is  $0.1\Omega$  to  $1.0\Omega$ .

**PROCEDURE:**

1. Connections are made as per the connection diagram
2. Connect the unknown resistance at R terminals.
3. Switch ON the unit.
4. Select the range selection switch at the point where the meter reads least possible value of voltage.
5. Vary the potentiometer (S) to obtain null balance
6. Switch OFF the unit and find the resistance using multimeter at S.
7. Tabulate the readings and find the value of unknown resistance using the above formula
8. Repeat the above for different values of unknown resistors.

**TABULAR COLUMN:**

SL NO	P( $\Omega$ )	Q( $\Omega$ )	R( $\Omega$ )	S( $\Omega$ )

## Experiment No.:9

### Characteristics of BJT


**AIM:** To determine the Input and Output characteristics of BJT Common emitter configuration and evaluation of parameters.

**THEORY:** A Bipolar Junction Transistor (BJT) has three terminals connected to three doped semiconductor regions. In an NPN transistor, thin and lightly doped P-type base is sandwiched between a heavily doped N-type emitter and another N-type collector, while in a PNP transistor, a thin and lightly doped N-type base is sandwiched between a heavily doped P-type emitter and another P-type collector.

The output characteristics show the relationship between the collector current ( $I_C$ ) and the collector-emitter voltage ( $V_{CE}$ ) with the varying of base current ( $I_B$ )

The collector current ( $I_C$ ) is mostly affected by the collector voltage ( $V_{CE}$ ) at 1.0V level but this  $I_C$  value is not highly affected above this value. Already we know that the emitter current is the sum of base and collector current. In.  $I_E = I_C + I_B$ . The current flowing through the resistive load ( $R_L$ ) give to the collector current of the transistor The equation for the collector current is given by,

$$I_C = (V_{CC} - V_{CE}) / R_L$$

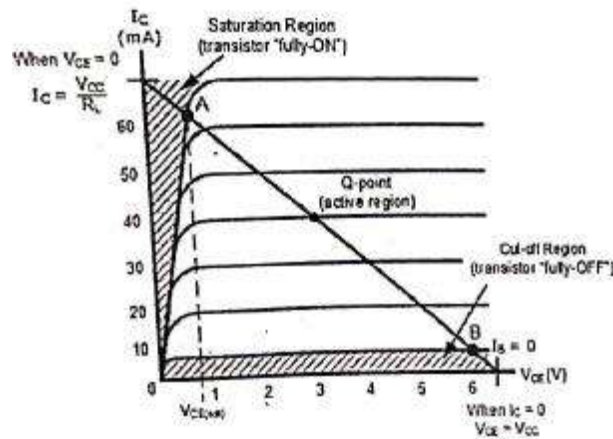


The straight line indicates the 'Dynamic load line' which is connecting the points (where  $V_{CE}=0$ ) and B (where  $I_C = 0$ ). The region along this load line represents the 'active region' of the transistor.

The common emitter configuration characteristics curves are used to calculate the collector current when the collector voltage and base current is given. The load line (red line) is used to determine the Q- point in the graph. The slope of the load line is equal to the reciprocal of the load resistance.

i.e  $-1/R_L$

$$R_{out} = \left. \frac{\Delta V_{CE}}{\Delta I_C} \right|_{I_B = \text{constant}}$$

## Input Characteristics

 

It is the curve between input current  $I_B$  and input voltage  $V_{BE}$  at constant collector-emitter voltage,  $V_{CE}$ . Fig shows the input characteristics of a typical transistor in common-emitter configuration.

This ratio is referred to as common-emitter current gain and is always greater than 1.

$$R_{in} = \left. \frac{\Delta V_{BE}}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$


The current gain in common base configuration  $\alpha$  is

$$\beta = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

related to  $\beta$  as  $\beta = \alpha/(1 - \alpha)$  and  $\alpha = \beta/(1 + \beta)$

The value of  $\alpha$  is always less than unity.

## CIRCUIT DIAGRAM:

 

## PROCEDURE :

### Input Characteristics

1. Construct the circuit as shown in Figure.
2. From the main menu, select Simulate → Analysis → DC Sweep
3. Set the Analysis Parameters tab as follows:
  - Set The Source to be  $V_{BE}$
  - Start value: 0V.
  - Stop value: 5V.
  - Increment: 0.1V
4. Set the nested source to be  $V_{CE}$ 
  - Start value: 0V.
  - Stop value: 20V.
  - Increment: 2V

5. Click the Output tab, select  $V(V_1+:A)$
6. Click Simulate, a grapher window will pop up after simulation is complete, showing the input Characteristics of BJT.

### **Output Characteristics**

1. Construct the circuit as shown in Figure.
2. From the main menu, select Simulate >Analysis >DC Sweep
3. Set the Analysis Parameters tab as follows:
  - Set the Source to be VCE
  - Start value: 0 V
  - Stop value: 20V.
  - Increment: 1V
  - Set the nested source to be VBE
  - Start value: 0V.
  - Stop value: 5V
  - Increment: 0.1V
5. Click Simulate, a graph window will pop up after simulation is complete, showing the output Characteristics of BJT.

### **Result:**

The input and output characteristics of BJT is simulated using PSPICE

# Experiment 10

## Transfer and drain characteristics of a JFET and MOSFET

**AIM:** To plot the characteristics of JFET and MOSFET and to calculate its parameter.

### THEORY:

The JFET is a unipolar device because its operation depends only on one type of carriers. JFET has high input impedance unlike BJT.

The JFET are two types N-channel JFET and P-channel JFET, An N-channel JFET is an N-type silicon bar with a P-type semiconductor embedded on both sides of the bar, The P-type semiconductor forms the gate and the ends of the N-type bar are source and drain. The P-type region are internally shorted. The gate of an N-channel JFET is connected to positive potential with respect to the source.

### *Drain dynamic resistance $r_d$*

The drain dynamic resistance is defined as the ratio of change in drain to source voltage to the change in drain current, when gate to source voltage remain constant.

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} \text{ constant}}$$

### *Mutual Conductance*

The mutual conductance is defined as the ratio of change in drain current to the change in gate to source voltage, when drain to source voltage remains constant

$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS} \text{ constant}}$$


### *Amplification factor*

It is defined as the ratio of change in drain to source voltage to the change in gate to source voltage when drain current remains constant.

$$\mu = \left. \frac{\Delta V_{DS}}{\Delta V_{GS}} \right|_{I_D \text{ constant}}$$

Where  $\mu$ ,  $g_m$  and  $r_d$  are related to each other as  $\mu = g_m \times r_d$

## SIMULATION CIRCUIT DIAGRAM

 

## MOSFET


In a MOSFET, current flows from the drain terminal to the source terminal through semiconductor channel. The resistance of the channel, and therefore its ability to conduct current, is controlled by a voltage applied to a third terminal denoted as the gate. MOSFET can be either an n-channel type or a p-channel type. In an n-channel MOSFET a positive voltage is applied to the drain terminal for operation while in a p-channel MOSFET a negative voltage is applied to the drain terminal for operation. A D-channel and p-channel type MOSFET may be one of two modes; enhancement mode or depletion mode. The enhancement mode MOSFET is normally (in cut-off and conducting no current) when no voltage is applied to the gate and is "on" (in saturation and conduction current) when a voltage greater than the gate-to source threshold is applied to the gate. The depletion mode MOSFET normally "on" (in saturation and conduction current) when no voltage is applied to the gate and is "off" (in cut-off and not conducting current) when a voltage more negative than the gate-to-source threshold is applied to the gate

### Transfer Characteristics:

In most MOSFET applications, an input signal is the gate voltage  $V_G$  and the output is the drain current  $I_D$ . The ability of MOSFET to amplify the signal is given by the output/input ratio: the trans conductance,  $g_m = dI_D/dV_{GS}$  with  $V_{DS}$  constant

### Drain Characteristics:

MOSFET operates in three operation mode, Cut-off when  $V_{GS} < V_t$ , Linear mode when  $V_{GS} > V_{th}$  and  $V_{DS} < (V_{GS} - V_{th})$  and Saturation when  $V_{GS} > V_{th}$  and  $V_{DS} \geq (V_{GS} - V_{th})$ . Pinch off occurs when  $V_{DS} = V_{Sat} = V_{GS} - V_{th}$ . The drain resistance,  $R_d = dV_{DS}/dI_D$  with  $V_{GS}$  constant

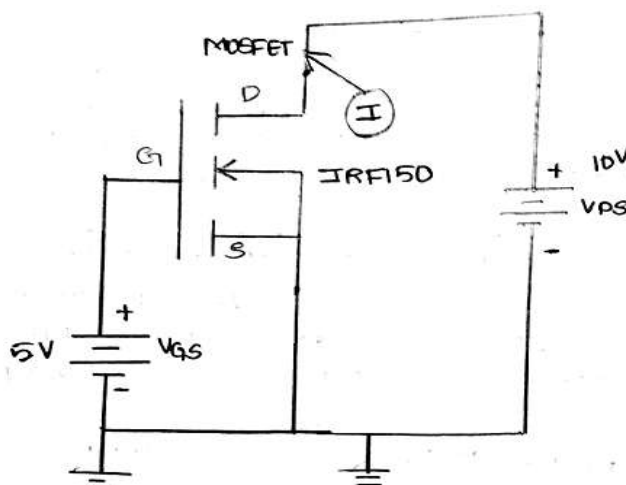**SIMULATION CIRCUIT DIAGRAM****PROCEDURE:****Transfer Characteristics**

1. Construct the circuit as shown in Figure.
2. From the main menu, select Simulate → Analysis → DC Sweep
3. Set the Analysis Parameters tab as follows:
  - Set the Source to be VGS (put all -ve value for JFET and +ve for MOSFET)
  - Start value: 0V.
  - Stop value: 5V.
  - Increment: 1V
4. Set the nested Source to be VDS
  - Start value: 0V.
  - Stop value: 20V.
  - Increment: 5V
5. Click Simulate, a graph window will pop up after simulation is complete, shows the transfer Characteristics of JFET/MOSFET.

**Drain Characteristics**

1. Construct the circuit as shown in Figure
2. From the main menu, select Simulate → Analysis → DC Sweep
3. Set the Analysis Parameters tab as follows
  - Set the Source to be VDS
  - Start value: 0V
  - Stop value: 20V.
  - Increment: 5V
4. Set the nested Source to be VGS
  - Start value: 0V.
  - Stop value: 5V.
  - Increment: 1V
5. Click Simulate, a graph window will pop up after simulation is complete, showing the drain Characteristics of JFET/MOSFET

**Result :** Transfer and drain characteristics of JFET and MOSFET are simulated.




## Experiment 11

### UJT triggering circuit for Controlled Rectifiers

**AIM:** Design and setup UJT triggering circuit for a single-phase half wave Controlled Rectifiers.
 
#### THEORY:

A un-junction transistor (UJT) is an electronic semiconductor device that has only one junction. The UJT has three terminals: an emitter (E) and two bases (B1 and B2). The base is formed by lightly doped n-type bar of silicon. Two ohmic contacts B1 and B2 are attached at its ends. The emitter is of p-type and it is heavily doped. The resistance between B1 and B2, when the emitter is open-circuit is called interbase resistance.



When the voltage across the capacitor reaches the UJT triggering voltage, the UJT turns ON. At this instant, the capacitor discharges through emitter (E), base (B1) and primary of pulse transformer. A pulse is produced at the primary, as well as at the secondary's of the transformer.


When the capacitor discharges to a voltage called valley voltage the UJT turns-off and capacitor charges again and the whole process repeats itself. The charging of the capacitor can be varied by varying the value of resistance R and therefore the firing angle can be controlled from 0 to 180 Degrees.

Then we can see that the un-junction oscillator continually switches "ON" and "OFF" without any feedback. The frequency of operation of the oscillator is directly affected by the value of the charging resistance R1, in series with the capacitor C1 and the value of  $\eta$ . The output pulse shape generated from the Base (B1) terminal is that of a saw-tooth waveform and to regulate the time period, you only have to change the  $\Omega$  value of resistance, R1 since it sets the RC time constant for charging the capacitor.

The time period, T of the saw-toothed waveform will be given as the charging time plus the discharging time of the capacitor. As the discharge time  $t_1$ , it is generally very short in comparison to the larger RC charging time,  $t_2$  the time period of oscillation is more or less equivalent to  $T \approx t_2$ . The frequency of oscillation is therefore given by  $f = 1/T$ .

**PROCEDURE:**

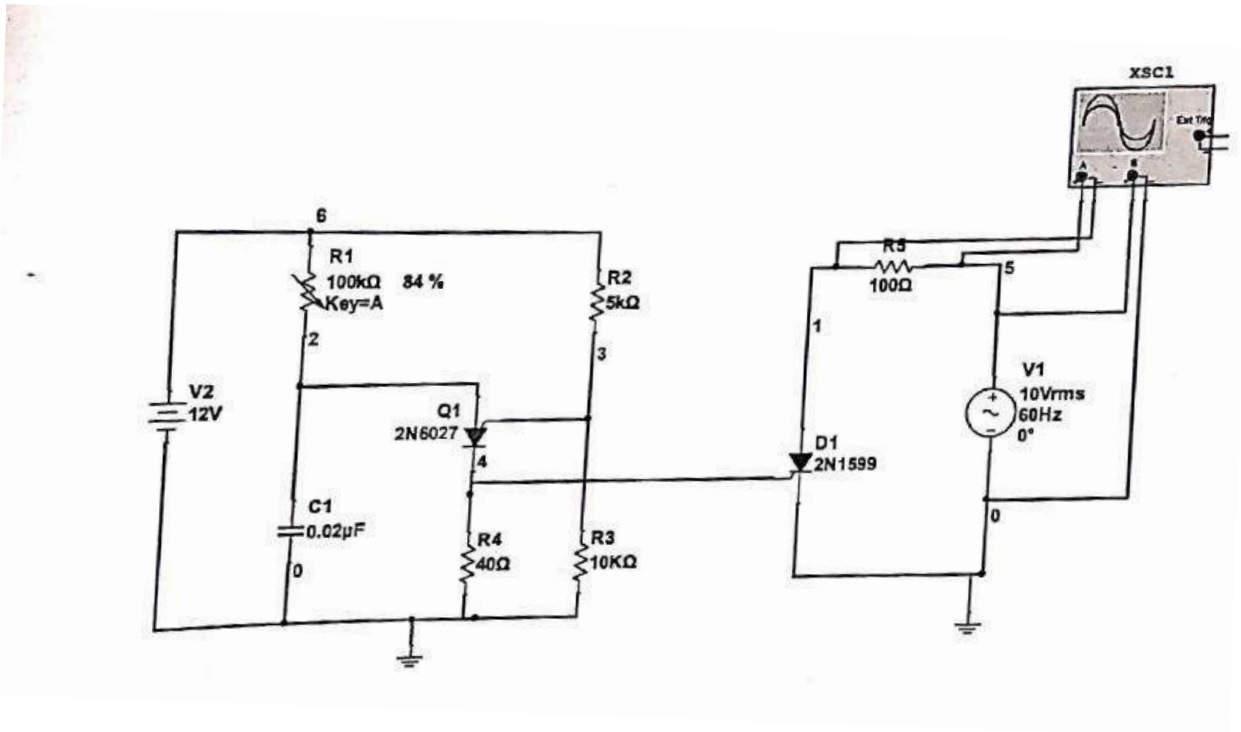1. Construct the circuit diagram as shown in figure
2. Run the simulation and observe the waveform at different firing angle by varying R1 resistor.



## Experiment 12


### Regulated power supply



**AIM:** Design and simulation of Regulated power supply.

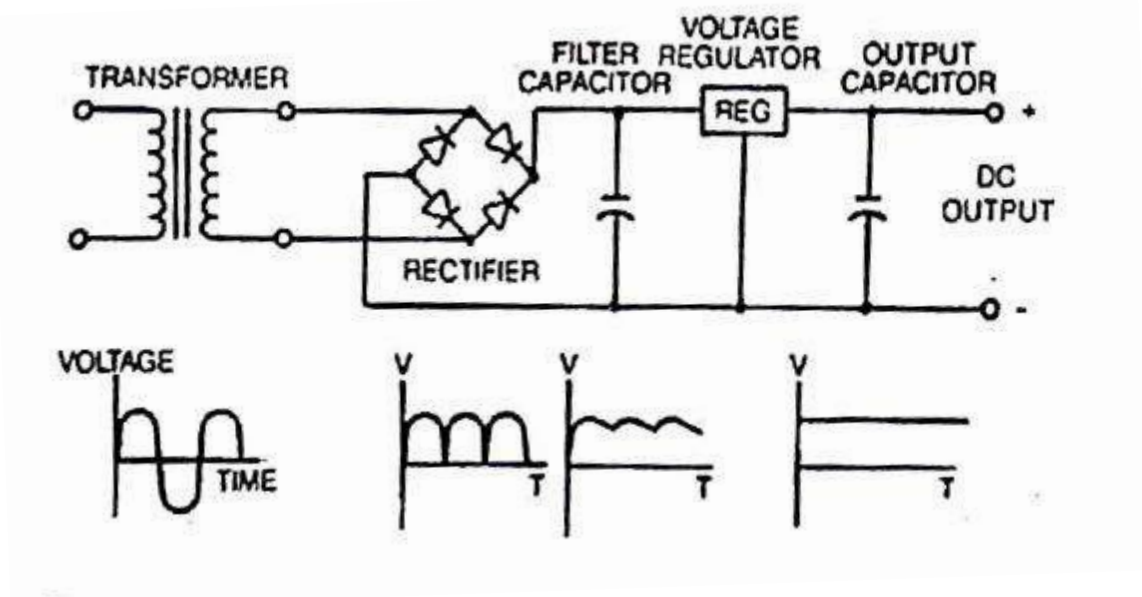**THEORY:**

Regulated power supply is an electronic circuit that is designed to provide a constant dc voltage of predetermined value across load terminals irrespective of ac mains fluctuations or load variations.

Regulated linear power supplies are same as the unregulated linear power supply except that a 3-terminal regulator is used in place of the bleeder resistor. Bleeder Resistor is also known as a power supply drain resistor. It is connected across the filter capacitors to drain their stored charge so that the power system supply is not dangerous. The main aim of this supply is to provide the required level of DC power to the load. A regulated power supply generally consists of a step-down transformer, rectifier circuit, and filter circuit and some voltage device connected to the input. Here the basic circuit diagram for Regulated Linear Power Supply given below.



 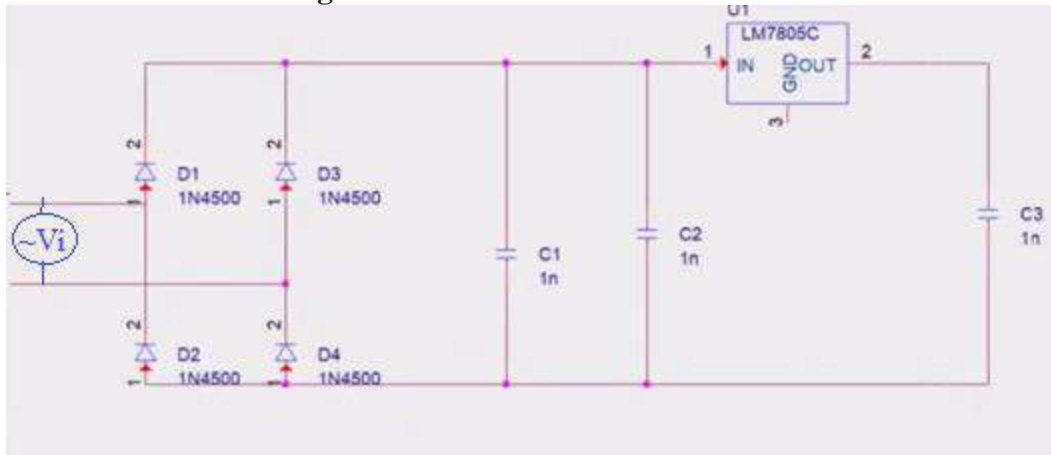**Simulation Circuit Diagram:****PROCEDURE:**

1. Rig up the circuit in PSICE as shown in figure.
2. Go to Analysis> transient> print step: 10ms  
End step:100ms  
 $V_{OFF}=0\text{ V}$   
 $V_{amp}=10\text{ V}$   
Frequency=50Hz

3. Click Simulate, a graph window will pop up after simulation is complete, showing the regulated output.